


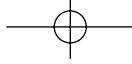
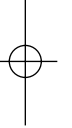


Index

COPYRIGHTED MATERIAL

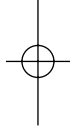

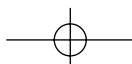

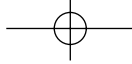

Index

A

AC (alternating current), 22
 circuits
 capacitors, 154–156, 165–167
 inductor, 156–158
 inductors, 190–197
 resistors, 152–154
 diodes in AC circuits, 347–358
 ripple, 359
 signal, capacitor, 187
 signals, 152
 capacitors passing, 166
 sine waves and, 147
 AC reactance of an inductor, 156
 algebraic formula for Ohm's law, 3
 alternative base switching, 131–137
 ammeter, 41
 amperes
 microampere, 11
 milliampere, 11
 amplifiers
 analyzing, 271–275
 common base amplifier, 298
 common collector amplifier, 265
 common emitter amplifier, 296–297
 feedback, 294
 input resistance, 265
 JFET as, 275–284

 lowest frequency passed, 273
 operational amplifier, 284–288
 output resistance, 265
 parallel inductor and capacitor,
 299
 resonant load, 299
 stability, 252–256
 tuned load, 299
 two-stage, 264
 voltage gain, 249
 anode, 36
 forward biased diode, 38
 voltage, 38
 Armstrong method, 304
 Armstrong oscillator, 316
 attenuation, 181
 f_r , 218

B

β (beta), 84–85
 finding of transistor, 87–97
 band of frequencies, 221
 band-reject filter, 222
 bandpass filter, 221
 bandwidth of circuits, 221
 calculating, 223
 base-collector diode, 75
 current flow, 79

- base current
 - collector current, 84
 - flow, 110
 - need for, 110
 - base-emitter diode, 75
 - current flow, 80
 - voltage drop, 111
 - base-emitter junction, current flow
 - from supply voltage to, 115
 - batteries, 2, 3
 - voltage, 13
 - biasing, 243, 256–265
 - bipolar junction transistors. *See* BJT (bipolar junction transistors)
 - bipolar transistors, 71
 - BJT (bipolar junction transistors), 71
 - terminals, 97
 - Boysen, Earl, 378
 - break down of diode, 57
 - BW, 221
- C**
- capacitors
 - AC, 22
 - AC circuits, 154–156
 - capacitor charging graph, 24
 - DC circuit, 22–28
 - DC signal, 187
 - emitter bypass capacitor, 261
 - and inductor in series, 208–218
 - level of opposition, 168
 - passing AC signals, 166
 - reactance, 155, 166
 - resistors and, 186–190
 - in series, 167–174
 - voltage, 24, 181
 - cascading transistor amplifiers, 264
 - cathode, 36
 - voltage, 38
 - center tap, 332
 - characteristic curve of a diode, 41
 - chemically generating electric current, 2
 - circuits
 - bandwidth, 221
 - calculating, 223
 - breaking, 20
 - completing, 20
 - RLC, 208
 - time constant, 23
 - transistors, soldering, 72
 - coils, 236
 - number of turns, 333
 - oscillators, 317
 - reversed, 331
 - transformers, 329–330
 - collector, current flow to base, 116
 - collector current
 - base current and, 84
 - calculating, 110
 - collector-emitter voltage, 89
 - collector voltage, ON transistor, 109
 - Colpitts method, 304
 - Colpitts oscillator circuit, 308–313
 - feedback connections, 310
 - common base amplifier, 298
 - oscillators and, 301
 - common collector amplifier, 265
 - common emitter amplifier, 296–297
 - oscillators and, 301
 - communications circuits, transformers
 - in, 338–343
 - conventional current flow, 3
 - current
 - closed switches, 20
 - definition, 2
 - KCL (Kirchhoff's current law), 19
 - open switches, 20
 - current divider, 17–20
 - current flow, 1–4, 3
 - direction, 81
 - magnetic field and, 234
 - current gain, 84
 - formula, 85
 - currents, small currents, 11–12
 - cutoff point, 246
 - cutoff voltage, 140

D

DC circuit, capacitors in,
22–28

DC (direct current), 1
level, 358–373
pre-test, 30–33
pulsating, diodes in AC circuits,
347–358
pure, 359
resistance, 156
signal, capacitor, 187
smoothing pulsating, 358–373

diode
in AC circuits, 347–358
forward biased, 38
perfect diode, 39
reverse biased, 39

diode junction, 36

diodes, 35
backward in circuit, 55
base-collector diode, 75
base-emitter diode, 75
break down, 57
experiment, 40–45
germanium, 36
power dissipated, 51
silicon, 36
V-I curve, 41
perfect diode, 56
zener diode, 58–65

direction of current flow, 81

doping, 36

dry-labbing, 40

E

efficiency of transformer, 337

electric current
definition, 2
generating, 2
chemically, 2
electrochemical reaction, 2
magnetically, 2
photovoltaic generation of
electrons, 2

piezoelectrical, 3
thermal generation, 2

electrochemical reaction, 2

electron flow, 3

Electronics Projects For Dummies,
378

emitter bypass capacitor, 261

emitter follower, 265–271
output impedance, 265

emitter voltage, ON transistor, 109

exponential curve, 25

F

f_3 , signal output voltage, 218

f_4 , signal output voltage, 218

feedback, 304–308
Armstrong method, 304
Colpitts method, 304
feedback resistor, 287
Hartley method, 304
negative, 294–295
positive, 295–296
voltage, calculating, 307

formulas, for power, 8–9

forward biased diode, 38
closed switches and, 40

forward transfer admittance, 280

f_r , attenuation, 218

frequencies
band of, 221
blocked by circuit, 219
range of, 221

frequency response graphs, half
power frequencies, 219

fuel cells, 2

full-wave rectifier, 355

function generator, 148

G

gain
accurate amounts, 262
op-amp, 287

general resonance curve, 229

generators, 2, 148
function generator, 148

422 Index ■ G–M

germanium, diodes, 36
graph of resistance, 12–14

H

half power frequencies, 219
half power points, 219
half-wave rectifier, 352
Hartley method, 304
Hartley oscillator, 314–315
high pass filter experiment, 174–180
high Q circuit, 227
Hill, Winfield, 378
holes, 2, 36
Horowitz, Paul, 378

I

I_B , 80
 calculating, 112–113
 value, 111
 I_C , 80
 load current, 108
IC (integrated circuit), 284
 op-amps, 285
 I_{DSS} (saturation current), 139
impedance
 calculating, 169
 inductor and capacitor, calculating,
 215
 internal impedance, 299
in phase, 331
inductor
 AC circuits, 156–158
 and capacitor in series, 208–218
 sine waves, 191
 voltage divider, 190
input resistance, 249
internal impedance, 299

J

JFET common source amplifier, 278
JFET (junction field effect transistors),
 71, 97, 241
 as amplifier, 275–284
 amplifying AC signals, 276

 biasing circuit, 275
 experiment, 138–142
 forward transfer admittance, 280
 gate voltage, 99
 N-channel, 97
 operating, 99
 P-channel, 97, 99
 semiconductor material, 97
 switches, 137
 terminals, 97
 transconductance and, 280
junction field effect transistors. *See*
 JFET (junction field effect
 transistors)

K

KCL (Kirchhoff's current law), 19
 KVL and, 19
kilohm, 11
knee region, 44
knee voltage, 45, 46
KVL (Kirchhoff's voltage law), 16
 KCL and, 19

L

LC circuit, 301
level DC, 358–373
limiting voltage, 45
line, 338
load, R_C , 108
load current, calculating, 110
load line, 245
load resistance, 249
low power carbon composition
 resistors, 10
low Q circuit, 228

M

magnet field, current flow and, 234
magnetically generating electric
 current, 2
mechanical switches, 20
 voltage drop, 40
megohm, 12

metal oxide silicon field effect transistors. *See* MOSFET
 microampere, 11
 milliampere, 11
 MOSFET (metal oxide silicon field effect transistors), 71
 Muir, Nancy, 378

N

N-channel JFET, 97
 N type region, 36
 negative feedback, 294–295
 nonlinear regions, 246
 notch filter, 222
 NPN transistor, 75–76, 82

O

OFF transistor
 characteristics, 96
 resistor, 115
 resistor values, 116
 Ohm's law, 4–6
 ON transistor
 collector voltage, 109
 turning on, 108–114
 op-amp (operational amplifier), 241, 284–288
 gain, 287
 operational amplifier, 284–288
 oscillators, 233–236, 293–303
 amplifier, 293
 Armstrong oscillator, 316
 coil, 317
 Colpitts oscillator circuit, 308–313
 components, 293
 design, 316–320
 external input, 308
 feedback connections, 293
 Hartley oscillator, 314–315
 sine wave and, 235
 troubleshooting, 320–325
 out of phase, 331
 output impedance, 265
 output signal, peak-to-peak value, 265

output voltage
 attenuated, 172
 calculating, 168
 determining, 229
 resonant frequency and, 214
 waveform
 lagging, 182
 leading, 182

P

P type region, 36
 peak (p) voltage, 150
 peak-to-peak (pp) voltage, 150
 perfect diode, 39
 V-I curve, 55
 phase
 in, 331
 out of, 331
 phase shift, RL circuit, 197–198
 phasor diagram, 184
 photovoltaic generation of electrons, 2
 piezoelectrical generation of electric current, 3
 PIV (peak inverse voltage), 57
 PN junction, 36
 direction of flow, 36
 PNP transistor, 75–76, 80, 82
 positive feedback, 295–296
 power, 8–10
 formula for, 8–9
 watts and, 8
 power ratings, 10
 power supply circuits, 347
 (peak-to-peak) voltage, D
 150
 primary time measurement, sine waves, 151
 PRV (peak reverse voltage), 57

Q

Q, 219
 calculating, 224
 high Q circuit, 227
 low Q circuit, 228

424 Index ■ R-S

R

R_1 , biasing and, 257
 radio bandwidth, 222
 range of frequencies, 221
 R_B , 82
 calculating, 111–112, 113
 current values, 108
 turning transistor ON, 108
 voltage drop, 111
 R_C , 84
 turning transistor ON, 108
 RC circuit, phase shift, 180–186
 R_E , biasing and, 257
 reactance, 154
 capacitors, 166
 rectification, 352
 full-wave rectifier, 355
 half-wave rectifier, 352
 rectifier, 35
 resistance, 154
 calculating total, 169
 graph of resistance, 12–14
 resistors
 AC circuits, 152–154
 capacitors and, 186–190
 low power carbon composition, 10
 OFF transistor, 115
 in parallel, 7–8
 power ratings, 10
 in series, 6–7
 in series, 167–174
 values, OFF transistor, 116
 resonance, 158–160
 resonant circuits
 capacitor and inductor in series,
 208–218
 half power frequencies, 219
 output curve, 218–232
 resonant frequency, net reactance of
 inductor and capacitor and, 214
 reverse biased diode, 39
 open switches and, 40
 R_F (feedback resistor), 287

R_{IN} (input resistance), 249
 RL circuit, phase shift, 197–198
 R_L (load resistance), 249
 RLC circuit, 208
 impedance, calculating, 209
 reactance, calculating, 209
 rms (root mean square) voltage, 150
 root mean square (rms) voltage, 150

S

saturation, 94, 140
 saturation current (I_{DSS}), 139
 saturation point, 246
 semiconductor, 35
 series
 capacitors in, 167–174
 resistors in, 167–174
 silicon
 diodes, 36
 transistor, 111
 sine wave, 147
 cycle, 148, 151
 duration, 151
 inductor, 191
 as input, 167
 oscillation and, 235
 as output, 167
 p voltage, 150
 pp voltage, 150
 primary time measurement, 151
 producing, 148
 rms voltage, 150
 signals, primary coils, 330
 zero axis, 149
 single pole double throw switch, 20
 single pole single throw switch, 20
 small currents, 11–12
 smoothing pulsating DC, 358–373
 solar cells, 2
 switches, 20–22
 alternative base switching, 131–137
 closed, 20
 controlling, 136

JFET, 137
 mechanical, 20
 open, 20
 current flow, 114
 terminal voltage, 114
 remote operation, 136
 single pole double throw, 20
 single pole single throw, 20
 speed, 136
 transistors as, 117–126
 three-transistor switch, 127–131


T

television bandwidth, 222
The Art of Electronics, 378
 thermal generation of electrical
 current, 2
 three-transistor switch, 127–131
 threshold voltage, 45
 time constant of circuit, 23
 total capacitance, 28
 transconductance, 280
 transformers
 alternating currents, 330
 coils, 329–330
 in communications circuits,
 338–343
 efficiency, 337
 output voltage, 333
 transistor, 71
 base-collector diode, 75
 base-emitter diode, 75
 cases, 72
 current gain, 85
 experiment, 87–97
 lead designations, 72
 leads, 73
 no collector current, 95
 NPN, 75–76
 OFF
 characteristics, 96
 resistor, 115
 resistor values, 116

P region thickness, 74
 packages, 72
 PNP, 75–76
 silicon, 111
 soldering to circuit, 72, 73
 switching, alternative base
 switching, 131–137
 turning OFF, 114–117
 turning ON, 108–114
 used as switches, 117–126
 three-transistor switch, 127–131
 voltage, between collector and
 emitter, 246
 transistor action, 79
 transistor amplifiers, 242–250
 cascading, 264
 emitter follower, 265–271
 experiment, 251–252
 gain, 249
 stability, 252–256
 two-stage amplifier, 264

V

V-I curve, 41
 perfect diode, 56
 V_{ce} , 89
 V_{CE} , 246
 voltage
 capacitors, 24, 181
 cutoff, 140
 knee voltage, 45, 46
 KVL (Kirchhoff's voltage law), 16
 limiting voltage, 45
 PIV (peak inverse voltage), 57
 PRV (peak reverse voltage), 57
 threshold voltage, 45
 voltage divider, 14–17
 capacitor in series, 168
 inductors, 190
 output voltage calculation,
 168
 resistor in series, 168
 Zener effect, 58

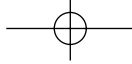**426 Index ■ V-Z**

voltage gain, 249
voltmeter, 41
 V_{out} , 170
plotting on graph, 214
resonance frequency,
 217
 V_z , 219

W

watts, 8
waveforms, oscillators, 233

Z

zener diode, 58–65
Zener effect, 58

