

Index

- AC circuits, 255, 256, 259, 261, 265, 275, 519
- AC-excited first-order circuits, 136, 138
- AC-excited RL circuit, 151
- Active filter, 333, 364
- Allpass filter (APF), 357
- Ampere's right-hand rule, 224, 225
- Autotransformers, 241

- Balanced three-phase load, 302
- Balanced three-phase voltages, 299, 300
- Bandpass filter (BPF), 322, 323, 325, 327, 329, 336, 337, 356, 363
- Bandstop filter (BSF), 329, 331, 338, 363
- Bipolar junction transistor (BJT), 13, 494, 504, 508
- Bridge balance condition, 273, 274
- Bridge circuit, 267, 273, 292, 440
- Bridged-T network, 363

- Capacitor, 8, 113, 477
 - characteristics of, 111
 - continuity rule of, 114
 - memory/inertia of, 114
 - series-parallel combination, 115, 116
 - standard values of, 476, 477
 - voltages, 114, 116
- Cascade connection, 416
- Circuit analysis, 373, 380, 521
- Circuit elements, 5, 25
- Circuit models, 438
- Complementary metal oxide semiconductor (CMOS), 165
- CRC circuit, 144, 146
- Current divider, 37, 38
- Current gain, 38, 423
 - parameters, 428
- Current magnification ratio, 326
- Current-controlled current source (CCCS), 10, 81, 296, 433, 438
- Current-controlled voltage source (CCVS), 10, 274, 297, 438

- Cutoff frequency, 320, 321, 333

- Damped frequency, 180, 196
- DC-excited RC circuits, 123
- Differential equation solver, 469
- Digital-to-analog converter (DAC), 102
- Discrete inductors, 478
- Discrete resistors, 476
- Double integrator, 219
- Driving-point impedances, 411
- Dual in-line package (DIP), 11

- Edison General Electric Company, 223
- Electric circuits, 1, 21, 514
- Electric energy, 3
 - storage elements, 111
- Electric power, 3, 320
- Electric shock, 310
- Electromotive force (emf), 2, 224, 297, 302
- Equivalent circuit, 64, 101, 102, 164
- Equivalent models, 228

- Faraday's law, 6, 224
- Fast Fourier transform (FFT), 373
- Feedback amplifier (s), 430, 433
 - series-parallel (shunt), 431
 - series-series, 431
- Final value theorem, 457
- First-order circuit, 111, 125, 126, 138, 152, 516
 - analysis of, 120
- First-order filter, 356
- First-order OP Amp circuits, 138, 140
 - analysis of, 138
- Fourier series, 373, 380, 387
 - complex exponential form, 374
 - magnitude-and-phase form, 374, 394
 - series representation, 373, 374, 380, 381, 392
 - sine-and-phase form, 374, 393
 - trigonometric form, 374

- Fourier series-with-phasor method, 390
- Fourier spectrum, 380, 397
- Free-wheeling diode, 112, 148
- Frequency response, 319
- Frequency scaling, 338
- Frequency selective circuit, 319, 520
- Full-wave rectified cosine wave, 380, 385

- Ground fault interrupter (GFI), 311

- Half-power frequency, 320
- Half-wave rectified cosine wave, 378, 380
- Half-wave rectifier, 161
- High-order Butterworth lowpass filter (LPF), 367
- High-order Chebyshev I bandpass filter (BPF), 370
- Highpass filter (HPF), 321, 335, 336
- Highpass notch (HPN), 357, 358, 362
- Highpass notch filter (HPNF), 357, 358
- Howland circuit, 107, 108
- Hybrid parameters, 402

- Inductors, 1, 8, 112, 115
 - characteristics of, 111
 - series-parallel combination of, 115
 - standard values of, 476, 478
- Ideal transformer, 237, 238, 240
- Impedance matching, 255, 284
- Integrated circuit (IC), 11
- Inverse Laplace transform, 122, 178, 179, 181–189, 191, 192, 194, 195, 248, 249, 457, 458
- Inverting RC integrator, 138

- Junction field-effect transistor (JFET), 13

- Kirchhoff's current law (KCL), 1, 13, 15, 205
- Kirchhoff's voltage law (KVL), 13, 16

- Laplace transform method, 177, 181, 256, 260, 261, 387, 390, 393
 - circuit analysis, 117
 - for first-order differential equation, 118
- Left-half plane (LHP), 211, 212, 457
- Lenz's law, 224, 226, 227
- Linear systems, 208
- Linear time-invariant (LTI) circuit, 256
- Linear time-invariant (LTI) system, 177, 207–211, 256, 451, 456
- Linear transformer, 240
- Load flow calculation, 285
- Lowpass filter (LPF), 319, 320, 322, 328, 333, 334
 - performance of, 398
- Lowpass notch (LPN), 362
- Lowpass notch filter (LPNF), 357, 358
- LRL circuits, 144

- Magnetic reluctance, 7, 223
- Magnetically coupled circuits, 223, 518
- Magnetomotive force (mmf), 6, 223, 237
- Magnitude scaling, 338
- MATLAB, 149, 511
 - command window, 155, 181, 186, 468, 511
 - routine, 343, 350
- Maximum power transfer, 283, 284, 286, 296
 - simulation for, 286
- Mesh (loop) analysis, 48, 56, 64
- Metal-oxide semiconductor field-effect transistor (MOSFET), 13
- Miller integrator, 138
- Multiple feedback (MFB) circuit, 353

- Network variables, 1
- Node circuit, 198
- Norton equivalent circuits, 63, 64
- Nonlinear equation solver, 155, 157, 285, 468
- Nonlinear resistor circuits, 83
 - load line analysis of, 82
- Nonsinusoidal periodic signal, 393, 394
 - distortion factor of, 393
 - power factor of, 393
 - power of, 393
 - RMS value of, 393

- Ohm's law, 5, 27
- One-shot method, 64
- OP Amp circuit, 13, 77, 78, 79, 91, 106
- Open/short-circuit tests, 294

- Parallel (shunt) connection, 414, 415
- Parallel feedback amplifier, 432
- Parallel resonance, 326, 327
- Parallel RLC circuit, 181, 192, 193, 196, 197, 215, 278, 326, 332
- Parallel-parallel feedback amplifier, 95
- Partial differentiation, 456
- Positive feedback path, 13, 78, 138, 140
- Power conservation law, 277, 281
- Power factor compensation, 279
- Power factor (PF) correction, 279, 295

- RC circuit, 149
- RC debouncer, 163
- RC OP Amp circuits, 169
- Real-world capacitors, 115
- Real-world inductors, 115
- Reciprocal network, 412
- Rectangular-wave generator, 142, 167

- Resistors circuits, 35, 515
 - parallel combination of, 36
 - series combination of, 35
 - standard values of, 476
- RLC circuit, 181, 187, 214
- Root mean square (RMS), 255, 256, 393, 509
 - phasor, 256, 257, 270
 - value, 393
- Sallen–Key circuits, 334, 353
- Sawtooth function, 395, 396
- Second-order active BPF, 334, 336, 337
- Second-order active HPF, 334
- Second-order active LPF, 334
- Second-order bandpass filter (s), 355, 356
- Second-order circuits, 177, 181, 517
 - OP Amp circuit, 219, 203, 222
- Self-inductance, 223
- Series connection, 413
- Series CR circuit, 321
- Series LR circuit, 319
 - RC circuit, 156, 166, 320
 - RLC circuit, 322, 329
- Series resonance, 322
- Source transformation method, 43, 47, 50, 52, 55, 56
- Spark arcing, 112
- Square-wave generator, 140, 174
- Supermesh method, 50, 51, 54, 56
- Supernode method, 42, 46, 56
- Tellegen’s theorem, 27, 28
- Thevenin equivalent circuit, 63, 65, 202, 229
 - equivalent impedance, 424
- Test current source method, 66
- Test voltage source method, 66
- Three-phase AC circuits, 299, 520
 - power system, 304, 306
- Total harmonic distortion (THD), 384, 394, 503
- Transformation method, 56
- Transistor, 13, 82
 - circuits, 81, 495
- Two-integrator biquad circuits, 362
- Two-mesh circuit, 198
- Two-port networks, 401, 406, 430, 441, 521
 - interconnection of, 413
 - reciprocity of, 411
- Triangular-wave generator, 142, 167
- Undamped resonant frequency, 180
- Virtually parallel capacitors, 164
- Voltage divider, 37
- Voltage drop, 2
- Voltage follower, 76
- Voltage magnification ratio, 324
- Voltage-controlled current source (VCCS), 10
- Voltage-controlled voltage source (VCVS), 9
- Voltage–current relationship (VCR), 1, 119
 - equations, 41, 48
- Wien bridge oscillator, 221

