

Index

- ABCD parameter, 402
- AC (alternating current), 10
- AC admittance, 262
- AC-excited first-order circuit, 136
- AC impedance, 261–262
- AC steady-state response, 260
- AC sweep analysis, 498, 508
- active element, 9
- active filter, 336–340
- active power, 275, 394
- admittance, 41, 120, 262
- admittance parameter, 401
- admittance triangle, 264–265
- all-pass filter, 358
- Ampere’s right-hand rule, 225
- analog computer, 169
- analog filter design, 341–354
- analogy, 205
- a -parameter, 402, 438
- apparent power, 277, 394
- arc, 112, 188, 190
- astable, 143
- autotransformer, 241–242
- average power, 275, 394

- balanced, 299–300, 302, 305
- bandpass filter (BPF), 323, 336, 344, 370
- bandstop filter (BSF), 330, 337, 345
- bandwidth, 320, 324, 331
- bias point, 493, 504
- biquad circuit, 362
- bistable multivibrator, 80
- bode(), 357, 366
- Bode diagram, 357
- bouncing, 163
- b -parameter, 402, 438
- Branch, 14, 18
- bridge balance condition, 274
- bridge circuit, 65, 267, 274, 292, 363, 440
- butter(), 342–344, 368
- Butterworth filter, 343, 347

- capacitance, 7–8, 116–117
- capacitance multiplier, 171
- capacitive, 264, 265
- capacitive reactance, 264
- capacitor, 7–8, 113, 116–117, 262
- Capture (CIS) window, 481
- cascade, 343, 369
- cascade connection, 416, 448
- causal, 212
- CCCS (current-controlled current source), 9–10
- CCVS (current-controlled voltage source), 9–10
- center frequency, 323, 324, 330
- characteristic equation, 178, 182
- characteristic root, 178
- charge conservation, 114, 147, 148
- cheby1(), 342, 344
- cheby2(), 342, 345
- Chebyshev filter, 342, 244, 245, 370
- closed-loop gain, 74, 75, 435
- coefficient of coupling, 225, 236
- complex power, 277
- conductance, 5, 36
- continuity rule of capacitor voltage, 114, 124
- continuity rule of inductor current, 111–112, 121, 252
- controlled source, 9
- controlling variable, 9
- convolution, 210, 455
- convolution property, 210, 452, 455
- coupled coils, 225–236, 243–254
- coupling, 225, 236
- CRC circuit, 146
- critically damped, 178, 179, 184, 194
- CtFS_trigonometric(), 380
- current, 2
- current divider, 38, 97
- current gain, 82, 241, 243, 423, 425
- current magnification ratio, 326
- current source, 9
- current transformer, 252
- Cursor, 490

- cutoff frequency, 320, 321, 322
 cutset, 15, 18
- DAC, *see* Digital-to-Analog converter
 damped frequency, 180
 damping constant, 180
 damping ratio, 180
 DC (direct current), 10
 DC path to ground, 485
 DC sensitivity analysis, 504
 DC steady state, 113, 114, 115
 DC sweep analysis, 494
 deactivation (removal) of sources, 21
 debounce, 95, 163
 degenerate circuit, 144
 Δ (delta)-Y (Π -T) conversion, 40, 266
 dependent source, 9
 design_combiner(), 104
 destabilization effect of positive feedback, 80
 diff(), 473
 difference amplifier, 91, 102, 103
 differential equation, 459, 469, 472
 differential input voltage, 11
 differentiation property, 122, 184, 452–454
 differentiator, 139, 170
 Digital-to-Analog converter (DAC), 102
 distortion factor, 394
 dot convention, 226
 driving-point impedance, 411
 dsolve(), 175, 472
 dual circuit, 206
 duality, 206
 dy_conversion(), 266
 dynamic resistance, 85–86
- effective value, 256, 393
 electric field energy (of capacitor), 8, 147
 electric potential, 2
 electric power, 3
 electric shock, 310
 electromotive force (emf), 2
 ellip(), 342, 346
 emf, *see* electromotive force
 equivalent, 21–22
- 555 timer/oscillator, 152–155, 173
 Faraday's law, 6, 224
 feedback amplifier, 430–434
 filter, 319
 filter design, 341, 343, 367, 370
 final state, 113, 114, 115
 final value theorem, 452, 457
 first-order circuit, 111
 first-order OP Amp circuit, 138–143
 flux, 6, 225
- flux linkage, 6, 224–225
 flux linkage conservation, 112, 145, 148, 252
 forced response, 124
 Fourier_analysis(), 384–385, 399
 Fourier analysis using Pspice, 381–384, 501
 Fourier series, 373–375
 Fourier series and Laplace transform, 387–390
 free-wheeling diode, 149
 frequency response, 211–212, 263, 319, 338–341, 347, 379
 frequency response scaling, 338
 frequency scaling, 338
 frequency selective circuit, 319
 fsolve(), 157, 162, 174, 175, 468
 full-wave rectified cosine wave, 385
 fundamental frequency, 373
- geometric series, 474
 GFI, *see* ground fault interrupter g -parameter, 402, 438
 ground fault interrupter (GFI), 311–313
 ground (node), 40, 484, 485
 grounding, 310–312
- half-power frequency, *see* cutoff frequency
 half-wave rectified cosine wave, 378
 half-wave rectifier, 161
 half-wave (symmetric), 375
 highpass filter (HPF), 321, 335, 336, 346
 highpass notch filter (HPNF), 358
 Howland circuit, 107
 h -parameter, 402, 438
 hybrid parameter, 402
 hysteresis characteristic, 80
- ideal OP Amp, 12
 ideal source, 10
 ideal transformer, 237–239
 ilaplace(), 187, 234, 459–460
 ilaplace_my(), 249, 446
 immittance parameter, 401
 impedance, 49, 120, 262
 impedance angle, 265
 impedance matching, 283–284, 296, 444, 448
 impedance parameter, 401
 impedance scaling (transformation), 238
 impedance transformation (scaling), 238
 impedance triangle, 263, 265
 impulse function, 453
 impulse response, 207–210
 independent source, 9
 inductance, 6–7, 116, 224
 inductance emulator, 172
 inductive, 264, 265
 inductive reactance, 264
 inductor, 6–7, 111, 115–116, 261–262

- initial state, 113, 114, 115
- initial transient bias point, 493
- initial value theorem, 452, 456
- in phase, 265, 323
- input impedance, 11, 77, 82, 422, 424, 425
- input resistance, 82, 100
- input resistance of OP Amp, 12
- instantaneous power, 275, 303
- int(), 473
- integration property, 452, 454
- integrator, 138–139, 169, 170, 219
- inverse Laplace transform, 457–460
- inverse matrix, 462–463
- inverse phasor transform, 259
- inverting OP Amp circuit, 72–73
- inverting positive-feedback OP Amp, 78–79

- jacob(), 469

- KCL (Kirchhoff's current law), 15–16, 27–30, 40, 75–76
- KCL equation, 18
- Kerwin-Huelsman-Newcomb (KHN) circuit, 362
- KVL (Kirchhoff's voltage law) 16–17, 27–30, 48
- KVL equation, 18

- ladder network, 27, 87
- lagging PF, 278
- Laplace transform, 118, 260, 390, 451–460
- Laplace transform table, 452
- LC tank, 327
- leading PF, 278
- Lenz's law, 224
- limit on output current of OP Amp, 109
- limit on output voltage of OP Amp, 109
- linear, 5, 8, 71, 208
- linear region, 11
- linear time-invariant, 208–209
- linear transformer, 240
- line voltage, 301
- load current controller, 107
- load flow, 285
- loading effect, 38, 77, 81–82
- load line analysis, 82–86, 110
- loop, 14–18
- loop analysis, *see* mesh analysis
- lowpass filter (LPF), 320, 334, 336
- lowpass notch filter (LPNF), 358
- LRL circuit, 144–145

- magnetically coupled, 225–236, 243–254
- magnetic field energy (of inductor), 7, 145
- magnetic reluctance, 7, 223
- magnetomotive force (mmf), 6, 223
- magnitude scaling, 338

- marginally stable, 181
- Marker, 486
- maximum output voltage of OP Amp, 11, 78–80
- maximum power transfer, 283–284, 296
- mesh, 14, 17
- mesh (loop) analysis, 48–56
- mesh equation, 49
- mesh impedance matrix, 49
- MFB (multiple feedback) circuit, 335–337, 353
- Millman's theorem, 98
- missing DC path to ground, 504
- mmf, *see* magnetomotive force
- multi-scale ammeter, 96
- multi-scale voltmeter, 96
- mutual inductance, 225–230, 246

- natural frequency, 125
- natural response, 124–125
- negative feedback, 12–13, 73–75, 138–143
- negative resistance, 108
- netlist file, 493
- neutral, 301
- neutrally stable, 181
- newtons(), 157, 469
- node, 14, 18
- node admittance matrix, 41
- node analysis, 40–48, 56
- node equation, 41
- non-inverting OP Amp circuit, 74–75
- non-inverting positive-feedback OP Amp, 79–80
- nonlinear equation, 468
- nonlinear resistor circuit, 82–86, 110
- nonlinear RL circuit, 175
- Norton equivalent, 63–64
- notch frequency, 330

- OP Amp (operational amplifier), 10–12, 77–78
- OP Amp circuit, 72–80, 91–94, 138–143, 168–174, 204, 333–340
- open-loop gain, 11–12, 435
- operating point, 83–86, 175, 493
- output impedance, 11, 77, 78, 82, 424, 429
- output resistance, 82, 100
- output resistance of OP Amp, 12
- overdamped, 178, 183

- parallel_comb(), 36, 266
- parallel, 25, 116, 117, 343, 369, 414, 432
- parallel(-parallel) connection, 414, 432
- parallel combination of capacitors, 117
- parallel combination of inductors, 116
- parallel combination of resistors, 36–37, 95
- parallel duplication of voltage source, 19, 22
- parallel resonance, 326, 327
- parallel RLC circuit, 192, 197, 215, 264, 326, 332

- parallel-series, 415, 433
- PARAMETERS, 287–288, 500–501
- parameter conversion, 406–410
- Parametric Sweep, 287–288, 500–501
- Passband, 324, 341
- passive element, 5
- passive sign convention, 4
- peak frequency, 323, 326
- periodic switching, 165
- permeability, 7, 223
- permeance, 6–7, 223, 237
- PF_correction(), 282
- PF (power factor) correction, 279–282, 295
- phase, 256, 466
- phase lag, 265
- phase lead, 265
- phase voltage, 301
- phasor, 256
- phasor diagram, 263–264, 280, 293, 301, 303
- phasor method, *see* phasor transform
- phasor transform, 259–260
- II(pi)-equivalent, 229
- port condition, 401, 416, 444
- port_conversion(), 410, 419, 439, 449
- port current requirement, *see* port condition
- port_property(), 427, 439, 449
- positive feedback, 13, 78–80, 95, 140–143
- potential, 2
- power, 3, 228, 275–278, 303, 394
- power conservation, 277
- power factor (PF), 278–286, 302–303, 394
- power factor (PF) angle, 265, 278
- power transmission, 240, 317
- power triangle, 277–278
- practical analysis rule of OP Amp circuit, 76
- practical source, 10
- Property Editor spreadsheet, 94, 152, 237, 288, 484, 497, 500
- pulse response, 208
- quality factor, 324, 326, 331
- RC circuit, 123, 134, 150, 156, 160, 164–167, 381
- RC OP Amp circuit, 139, 169, 173
- reactance, 262, 263
- reactive power, 276
- real power, 275
- reciprocal, 412
- rectangular (or square) wave, 142, 376, 381
- rectangular wave generator, 140–143, 167–168, 174
- reference direction, 4
- reference node, 40
- reference polarity, 3
- reflected impedance, 239, 297
- rejection frequency, 330
- relative winding direction, 226, 230, 235
- relaxation oscillator, 143
- relay, 159
- removal (deactivation) of sources, 21
- residue(), 458–460
- resistance, 5, 35
- resistivity, 5, 25
- resistor, 5, 119, 261
- resonance, 325, 326, 329
- resonance condition, 329
- resonant frequency, 323, 326
- RL circuit, 121, 134, 152, 156, 159, 166, 173, 176
- rms (root-mean-square), 256, 393
- Sallen-Key circuit, 334, 353
- saturation output voltage of OP Amp, 11, 78, 108, 220, 291
- saturation (nonlinear) region, 11
- saw-tooth function, 395
- Schmitt trigger, 80, 94–95, 163
- s-domain (transformed) equivalent, 119–120
- second-order active filter, 334–338
- second-order circuit, 177
- second-order OP Amp circuit, 204, 213, 222
- selectivity, 324, 331
- self inductance, 224
- sequential switching, 133, 166–167
- series, 25, 116, 117, 414
- series combination of capacitors, 117
- series combination of inductors, 116
- series combination of resistors, 36–37, 95
- series duplication of current source, 20, 23
- series-parallel, 415, 431
- series resonance, 325
- series RLC circuit, 181, 187, 214, 263, 323, 330
- series(-series), 414, 432
- simulation profile, 486–487
- Simulation Settings dialog box, 237, 288, 487–488
- singular circuit, 144
- SKIPBP, 236, 248, 250
- solve(), 472
- source transformation, 21–24, 31
- source transformation method, 43, 45, 47, 52, 55, 56
- square wave, *see* rectangular wave
- stable, 180–181, 212
- stabilization effect of negative feedback, 12
- standard values of capacitors, 477
- standard values of inductors, 478
- standard values of resistors, 476
- state equation, 470
- static resistance, 85–86
- steady-state response, 125, 211–212
- step function, 451
- step response, 327
- stopband, 331, 341

- summing amplifier, 91
- supermesh, 14, 17
- supermesh method, 50, 51, 54
- supernode, 14, 16
- supernode method, 42, 44, 46, 59, 61
- superposition principle, 71, 208
- susceptance, 262, 264
- symbolic computation, 471
- symmetrical, 412

- 3dB frequency, 320, 326, 331
- Tellegen's theorem, 28
- T-equivalent, 229, 245, 248, 250
- tf2par_s(), 349
- tf2sos(), 344
- THD, *see* total harmonic distortion
- Thevenin equivalent, 63–70, 99–102, 203, 239, 270, 273, 424
- three-phase power, 303–308
- time constant, 125–128, 180, 321
- time differentiation property, 452, 454
- time-invariant, 208
- time shifting property, 452, 455
- total harmonic distortion (THD), 394
- Tow-Thomas circuit, 362
- Trace, 490
- transfer function, 178, 205, 207, 210
- transfer function analysis, 504
- transfer impedance, 411
- transformed (*s*-domain) equivalent, 119–120
- transformer, 237–243, 246, 284, 294
- transient response, 125
- transmission loss, 280
- transmission parameter, 402
- tree, 18
- triangular wave, 376, 399
- triangular wave generator, 140–143, 167–168
- trigonometric formulas, 474
- tuning, 339
- two-port network, 401, 420
- two-port network property, 427

- undamped, 186, 195
- undamped resonant frequency, 180, 181

- underdamped, 179, 185
- unit impulse function, 453
- units, 1
- unit step function, 451
- unbalanced three-phase power system, 314
- unstable, 143, 180, 181

- VA (Volt-Ampere), 277
- VAC (AC voltage source), 483
- VAR (Volt-Ampere Reactive), 277
- VCCS (voltage-controlled current source), 9–10
- VCR (voltage-current relationship), 41, 48
- VCVS (voltage-controlled voltage source), 9–10
- virtual ground, 73
- virtual open principle, 13, 76
- virtual short principle, 12–13, 76
- voltage, 2
- voltage divider, 37, 88, 97
- voltage follower, 76–77
- voltage gain, 81, 241, 243, 423, 425
- voltage magnification ratio, 324
- voltage source, 9
- voltage-to-current converter, 107
- VPULSE, 382, 484
- VPWL, 484
- VSIN, 483, 484

- War of Currents, 223
- wC_for_PF_correction(), 282
- Wien bridge oscillator, 221
- window defroster, 90

- y*-parameter, 401, 438
- yd_conversion(), 266
- Y- Δ (T-II) conversion, 40, 266
- Y- Δ /Y connection, 307
- y_d(), 316
- y_dy(), 307, 314
- Y-Y connection, 304
- y_y(), 305, 314

- zero-input response, 124
- zero-state response, 124
- z*-parameter, 401, 438

