

Contents

PREFACE *xi*

**CHAPTER 1 INTRODUCTION TO DATA CONVERSION
AND PROCESSING** **1**

CHAPTER 2 BASIC SAMPLING CIRCUITS **7**

2.1 General Considerations **7**

2.2 Performance Metrics **11**

2.3 Sampling Switches **13**

2.3.1 MOS Switches **14**

2.3.2 Diode Switches **19**

2.3.3 Comparison of MOS and Diode Switches **23**

2.3.4 Improvements in MOS Switch Performance **24**

References **27**

CHAPTER 3 SAMPLE-AND-HOLD ARCHITECTURES **29**

3.1 Conventional Open-Loop Architecture **29**

3.2 Conventional Closed-Loop Architecture **31**

3.3 Open-Loop Architecture with Miller Capacitance **33**

3.4	Multiplexed-Input Architectures	35
3.5	Recycling Architecture	39
3.6	Switched-Capacitor Architecture	40
3.7	Current-Mode Architecture	42
	References	43
CHAPTER 4	BASIC PRINCIPLES OF DIGITAL-TO-ANALOG CONVERSION	45
4.1	General Considerations	45
4.2	Performance Metrics	47
4.3	Reference Multiplication and Division	49
4.3.1	Voltage Division	50
4.3.2	Current Division	55
4.3.3	Charge Division	63
4.4	Switching and Logical Functions in DACs	70
4.4.1	Switching Functions in Resistor-Ladder DACs	70
4.4.2	Switching Functions in Current-Steering DACs	72
4.4.3	Switching Functions in Capacitor DACs	74
4.4.4	Binary-to-Thermometer Code Conversion	76
	References	77
CHAPTER 5	DIGITAL-TO-ANALOG CONVERTER ARCHITECTURES	79
5.1	Resistor-Ladder DAC Architectures	79
5.1.1	Ladder Architecture with Switched Subdivider	79
5.1.2	Intermeshed Ladder Architectures	82
5.2	Current-Steering Architectures	84
5.2.1	R - $2R$ -Network Based Architectures	84
5.2.2	Segmented Architectures	90
	References	94
CHAPTER 6	ANALOG-TO-DIGITAL CONVERTER ARCHITECTURES	96
6.1	General Considerations	96
6.2	Performance Metrics	99
6.3	Flash Architectures	101
6.3.1	Reference Ladder DC and AC Bowing	103
6.3.2	Nonlinear Input Capacitance	106

6.3.3	Kickback Noise	107
6.3.4	Sparkles in Thermometer Code	108
6.3.5	Metastability	110
6.3.6	Slew-Dependent Sampling Point	112
6.3.7	Clock Jitter and Dispersion	112
6.3.8	Gray Encoding	114
6.4	Two-Step Architectures	116
6.4.1	Effect of Nonidealities	121
6.4.2	Two-Step Recycling Architecture	124
6.4.3	Two-Step Subranging Architecture	125
6.5	Interpolative and Folding Architectures	126
6.5.1	Interpolation	127
6.5.2	Folding Architectures	132
6.5.3	Folding with Interpolation	136
6.6	Pipelined Architectures	140
6.7	Successive Approximation Architectures	143
6.8	Interleaved Architectures	147
	References	149

CHAPTER 7 BUILDING BLOCKS OF DATA CONVERSION SYSTEMS 153

7.1	Amplifiers	153
7.1.1	Open-Loop Amplifiers	153
7.1.2	Closed-Loop Amplifiers	160
7.1.3	Operational Amplifiers	164
7.1.4	Gain Boosting Techniques	171
7.1.5	Common-Mode Feedback	172
7.2	Comparators	177
7.2.1	Bipolar Comparators	181
7.2.2	CMOS Comparators	188
7.2.3	BiCMOS Comparators	191
	References	195

CHAPTER 8 PRECISION TECHNIQUES 198

8.1	Comparator Offset Cancellation	198
8.1.1	Input Offset Storage	199
8.1.2	Output Offset Storage	201
8.1.3	Multistage Offset Storage	202
8.1.4	Comparators Using Offset-Cancelled Latches	206
8.2	Op Amp Offset Cancellation	208

- 8.3 Calibration Techniques **211**
 - 8.3.1 DAC Calibration Techniques **211**
 - 8.3.2 ADC Calibration Techniques **218**
- 8.4 Range Overlap and Digital Correction **224**
 - References **229**

CHAPTER 9 TESTING AND CHARACTERIZATION 232

- 9.1 General Considerations **232**
- 9.2 Sampling Circuits **234**
- 9.3 D/A Converters **239**
- 9.4 A/D Converters **239**
 - 9.4.1 Static Testing **239**
 - 9.4.2 Dynamic Testing **241**

INDEX 252