

Contents

| | |
|---|-------------|
| List of Contributors | xv |
| Preface | xvii |
| 1 Overview | 1 |
| <i>I. A. Glover, S. R. Pennock and P. R. Shepherd</i> | |
| 1.1 Introduction | 1 |
| 1.2 RF Devices | 2 |
| 1.3 Signal Transmission and Network Methods | 4 |
| 1.4 Amplifiers | 5 |
| 1.5 Mixers | 6 |
| 1.6 Filters | 7 |
| 1.7 Oscillators and Frequency Synthesisers | 7 |
| 2 RF Devices: Characteristics and Modelling | 9 |
| <i>A. Suarez and T. Fernandez</i> | |
| 2.1 Introduction | 9 |
| 2.2 Semiconductor Properties | 10 |
| 2.2.1 Intrinsic Semiconductors | 10 |
| 2.2.2 Doped Semiconductors | 13 |
| 2.2.2.1 N-type doping | 13 |
| 2.2.2.2 P-type doping | 14 |
| 2.2.3 Band Model for Semiconductors | 14 |
| 2.2.4 Carrier Continuity Equation | 17 |
| 2.3 P-N Junction | 18 |
| 2.3.1 Thermal Equilibrium | 18 |
| 2.3.2 Reverse Bias | 21 |
| 2.3.3 Forward Bias | 23 |
| 2.3.4 Diode Model | 24 |
| 2.3.5 Manufacturing | 25 |
| 2.3.6 Applications of P-N Diodes at Microwave Frequencies | 26 |
| 2.3.6.1 Amplitude modulators | 28 |
| 2.3.6.2 Phase shifters | 29 |
| 2.3.6.3 Frequency multipliers | 30 |
| 2.4 The Schottky Diode | 32 |
| 2.4.1 Thermal Equilibrium | 32 |
| 2.4.2 Reverse Bias | 34 |

| | | |
|-------|--|----|
| 2.4.3 | <i>Forward Bias</i> | 35 |
| 2.4.4 | <i>Electric Model</i> | 36 |
| 2.4.5 | <i>Manufacturing</i> | 37 |
| 2.4.6 | <i>Applications</i> | 37 |
| | 2.4.6.1 Detectors | 38 |
| | 2.4.6.2 Mixers | 39 |
| 2.5 | PIN Diodes | 40 |
| | 2.5.1 <i>Thermal Equilibrium</i> | 40 |
| | 2.5.2 <i>Reverse Bias</i> | 40 |
| | 2.5.3 <i>Forward Bias</i> | 41 |
| | 2.5.4 <i>Equivalent Circuit</i> | 43 |
| | 2.5.5 <i>Manufacturing</i> | 44 |
| | 2.5.6 <i>Applications</i> | 45 |
| | 2.5.6.1 Switching | 45 |
| | 2.5.6.2 Phase shifting | 47 |
| | 2.5.6.3 Variable attenuation | 50 |
| | 2.5.6.4 Power limiting | 50 |
| 2.6 | Step-Recovery Diodes | 51 |
| 2.7 | Gunn Diodes | 52 |
| | 2.7.1 <i>Self-Oscillations</i> | 54 |
| | 2.7.2 <i>Operating Modes</i> | 55 |
| | 2.7.2.1 Accumulation layer mode | 56 |
| | 2.7.2.2 Transit-time dipole layer mode | 56 |
| | 2.7.2.3 Quenched dipole layer mode | 56 |
| | 2.7.2.4 Limited-space-charge accumulation (LSA) mode | 57 |
| | 2.7.3 <i>Equivalent Circuit</i> | 57 |
| | 2.7.4 <i>Applications</i> | 58 |
| | 2.7.4.1 Negative resistance amplifiers | 58 |
| | 2.7.4.2 Oscillators | 59 |
| 2.8 | IMPATT Diodes | 59 |
| | 2.8.1 <i>Doping Profiles</i> | 60 |
| | 2.8.2 <i>Principle of Operation</i> | 60 |
| | 2.8.3 <i>Device Equations</i> | 62 |
| | 2.8.4 <i>Equivalent Circuit</i> | 63 |
| 2.9 | Transistors | 65 |
| | 2.9.1 <i>Some Preliminary Comments on Transistor Modelling</i> | 65 |
| | 2.9.1.1 Model types | 65 |
| | 2.9.1.2 Small and large signal behaviour | 65 |
| | 2.9.2 <i>GaAs MESFETs</i> | 66 |
| | 2.9.2.1 Current-voltage characteristics | 68 |
| | 2.9.2.2 Capacitance-voltage characteristics | 70 |
| | 2.9.2.3 Small signal equivalent circuit | 71 |
| | 2.9.2.4 Large signal equivalent circuit | 74 |
| | 2.9.2.5 Curtice model | 74 |
| | 2.9.3 <i>HEMTs</i> | 75 |
| | 2.9.3.1 Current-voltage characteristics | 76 |
| | 2.9.3.2 Capacitance-voltage characteristics | 78 |
| | 2.9.3.3 Small signal equivalent circuit | 78 |
| | 2.9.3.4 Large signal equivalent circuit | 78 |

| | | |
|----------|---|-----------|
| 2.9.4 | <i>HBTs</i> | 80 |
| 2.9.4.1 | Current-voltage characteristics | 84 |
| 2.9.4.2 | Capacitance-voltage characteristics | 84 |
| 2.9.4.3 | Small signal equivalent circuit | 86 |
| 2.9.4.4 | Large signal equivalent circuit | 87 |
| 2.10 | Problems | 88 |
| | References | 89 |
| 3 | Signal Transmission, Network Methods and Impedance Matching | 91 |
| | <i>N. J. McEwan, T. C. Edwards, D. Dernikas and I. A. Glover</i> | |
| 3.1 | Introduction | 91 |
| 3.2 | Transmission Lines: General Considerations | 92 |
| 3.2.1 | <i>Structural Classification</i> | 92 |
| 3.2.2 | <i>Mode Classes</i> | 94 |
| 3.3 | The Two-Conductor Transmission Line: Revision of Distributed Circuit Theory | 95 |
| 3.3.1 | <i>The Differential Equations and Wave Solutions</i> | 96 |
| 3.3.2 | <i>Characteristic Impedance</i> | 98 |
| 3.4 | Loss, Dispersion, Phase and Group Velocity | 99 |
| 3.4.1 | <i>Phase Velocity</i> | 100 |
| 3.4.2 | <i>Loss</i> | 100 |
| 3.4.3 | <i>Dispersion</i> | 101 |
| 3.4.4 | <i>Group Velocity</i> | 102 |
| 3.4.5 | <i>Frequency Dependence of Line Parameters</i> | 105 |
| 3.4.5.1 | Frequency dependence of G | 108 |
| 3.4.6 | <i>High Frequency Operation</i> | 109 |
| 3.4.6.1 | Lossless approximation | 111 |
| 3.4.6.2 | The telegrapher's equation and the wave equation | 111 |
| 3.5 | Field Theory Method for Ideal TEM Case | 113 |
| 3.5.1 | <i>Principles of Electromagnetism: Revision</i> | 114 |
| 3.5.2 | <i>The TEM Line</i> | 117 |
| 3.5.3 | <i>The Static Solutions</i> | 117 |
| 3.5.4 | <i>Validity of the Time Varying Solution</i> | 119 |
| 3.5.5 | <i>Features of the TEM Mode</i> | 121 |
| 3.5.5.1 | A useful relationship | 122 |
| 3.5.6 | <i>Picturing the Wave Physically</i> | 123 |
| 3.6 | Microstrip | 126 |
| 3.6.1 | <i>Quasi-TEM Mode and Quasi-Static Parameters</i> | 128 |
| 3.6.1.1 | Fields and static TEM design parameters | 128 |
| 3.6.1.2 | Design aims | 129 |
| 3.6.1.3 | Calculation of microstrip physical width | 130 |
| 3.6.2 | <i>Dispersion and its Accommodation in Design Approaches</i> | 132 |
| 3.6.3 | <i>Frequency Limitations: Surface Waves and Transverse Resonance</i> | 135 |
| 3.6.4 | <i>Loss Mechanisms</i> | 137 |
| 3.6.5 | <i>Discontinuity Models</i> | 139 |
| 3.6.5.1 | The foreshortened open end | 139 |
| 3.6.5.2 | Microstrip vias | 141 |
| 3.6.5.3 | Mitred bends | 142 |
| 3.6.5.4 | The microstrip T-junction | 142 |

| | | |
|----------|---|------------|
| 3.6.6 | <i>Introduction to Filter Construction Using Microstrip</i> | 145 |
| 3.6.6.1 | Microstrip low-pass filters | 145 |
| 3.6.6.2 | Example of low-pass filter design | 148 |
| 3.7 | Coupled Microstrip Lines | 148 |
| 3.7.1 | <i>Theory Using Even and Odd Modes</i> | 150 |
| 3.7.1.1 | Determination of coupled region physical length | 156 |
| 3.7.1.2 | Frequency response of the coupled region | 157 |
| 3.7.1.3 | Coupler directivity | 158 |
| 3.7.1.4 | Coupler compensation by means of lumped capacitors | 159 |
| 3.7.2 | <i>Special Couplers: Lange Couplers, Hybrids and Branch-Line Directional Couplers</i> | 161 |
| 3.8 | Network Methods | 163 |
| 3.8.1 | <i>Revision of z, y, h and ABCD Matrices</i> | 164 |
| 3.8.2 | <i>Definition of Scattering Parameters</i> | 166 |
| 3.8.3 | <i>S-Parameters for One- and Two-Port Networks</i> | 168 |
| 3.8.4 | <i>Advantages of S-Parameters</i> | 171 |
| 3.8.5 | <i>Conversion of S-Parameters into Z-Parameters</i> | 171 |
| 3.8.6 | <i>Non-Equal Complex Source and Load Impedance</i> | 174 |
| 3.9 | Impedance Matching | 176 |
| 3.9.1 | <i>The Smith Chart</i> | 176 |
| 3.9.2 | <i>Matching Using the Smith Chart</i> | 182 |
| 3.9.2.1 | Lumped element matching | 182 |
| 3.9.2.2 | Distributed element matching | 187 |
| 3.9.2.3 | Single stub matching | 187 |
| 3.9.2.4 | Double stub matching | 189 |
| 3.9.3 | <i>Introduction to Broadband Matching</i> | 191 |
| 3.9.4 | <i>Matching Using the Quarter Wavelength Line Transformer</i> | 194 |
| 3.9.5 | <i>Matching Using the Single Section Transformer</i> | 194 |
| 3.10 | Network Analysers | 195 |
| 3.10.1 | <i>Principle of Operation</i> | 196 |
| 3.10.1.1 | The signal source | 197 |
| 3.10.1.2 | The two-port test set | 197 |
| 3.10.1.3 | The receiver | 198 |
| 3.10.2 | <i>Calibration Kits and Principles of Error Correction</i> | 198 |
| 3.10.3 | <i>Transistor Mountings</i> | 202 |
| 3.10.4 | <i>Calibration Approaches</i> | 206 |
| 3.11 | Summary | 207 |
| | References | 208 |
| 4 | Amplifier Design | 209 |
| | <i>N. J. McEwan and D. Dernikas</i> | |
| 4.1 | Introduction | 209 |
| 4.2 | Amplifier Gain Definitions | 209 |
| 4.2.1 | <i>The Transducer Gain</i> | 211 |
| 4.2.2 | <i>The Available Power Gain</i> | 212 |
| 4.2.3 | <i>The Operating Power Gain</i> | 213 |
| 4.2.4 | <i>Is There a Fourth Definition?</i> | 213 |
| 4.2.5 | <i>The Maximum Power Transfer Theorem</i> | 213 |
| 4.2.6 | <i>Effect of Load on Input Impedance</i> | 216 |
| 4.2.7 | <i>The Expression for Transducer Gain</i> | 218 |

| | | |
|---------|---|-----|
| 4.2.8 | <i>The Origin of Circle Mappings</i> | 221 |
| 4.2.9 | <i>Gain Circles</i> | 222 |
| 4.3 | Stability | 223 |
| 4.3.1 | <i>Oscillation Conditions</i> | 224 |
| 4.3.2 | <i>Production of Negative Resistance</i> | 227 |
| 4.3.3 | <i>Conditional and Unconditional Stability</i> | 228 |
| 4.3.4 | <i>Stability Circles</i> | 229 |
| 4.3.5 | <i>Numerical Tests for Stability</i> | 230 |
| 4.3.6 | <i>Gain Circles and Further Gain Definitions</i> | 231 |
| 4.3.7 | <i>Design Strategies</i> | 237 |
| 4.4 | Broadband Amplifier Design | 239 |
| 4.4.1 | <i>Compensated Matching Example</i> | 240 |
| 4.4.2 | <i>Fano's Limits</i> | 241 |
| 4.4.3 | <i>Negative Feedback</i> | 243 |
| 4.4.4 | <i>Balanced Amplifiers</i> | 244 |
| 4.4.4.1 | Principle of operation | 245 |
| 4.4.4.2 | Comments | 245 |
| 4.4.4.3 | Balanced amplifier advantages | 246 |
| 4.4.4.4 | Balanced amplifier disadvantages | 246 |
| 4.5 | Low Noise Amplifier Design | 246 |
| 4.5.1 | <i>Revision of Thermal Noise</i> | 246 |
| 4.5.2 | <i>Noise Temperature and Noise Figure</i> | 248 |
| 4.5.3 | <i>Two-Port Noise as a Four Parameter System</i> | 250 |
| 4.5.4 | <i>The Dependence on Source Impedance</i> | 251 |
| 4.5.5 | <i>Noise Figures Circles</i> | 254 |
| 4.5.6 | <i>Minimum Noise Design</i> | 255 |
| 4.6 | Practical Circuit Considerations | 256 |
| 4.6.1 | <i>High Frequencies Components</i> | 256 |
| 4.6.1.1 | Resistors | 256 |
| 4.6.1.2 | Capacitors | 259 |
| 4.6.1.3 | Capacitor types | 261 |
| 4.6.1.4 | Inductors | 263 |
| 4.6.2 | <i>Small Signal Amplifier Design</i> | 267 |
| 4.6.2.1 | Low-noise amplifier design using CAD software | 268 |
| 4.6.2.2 | Example | 269 |
| 4.6.3 | <i>Design of DC Biasing Circuit for Microwave Bipolar Transistors</i> | 272 |
| 4.6.3.1 | Passive biasing circuits | 272 |
| 4.6.3.2 | Active biasing circuits | 274 |
| 4.6.4 | <i>Design of Biasing Circuits for GaAs FET Transistors</i> | 277 |
| 4.6.4.1 | Passive biasing circuits | 277 |
| 4.6.4.2 | Active biasing circuits | 279 |
| 4.6.5 | <i>Introduction of the Biasing Circuit</i> | 279 |
| 4.6.5.1 | Implementation of the RFC in the bias network | 282 |
| 4.6.5.2 | Low frequency stability | 287 |
| 4.6.5.3 | Source grounding techniques | 288 |
| 4.7 | Computer Aided Design (CAD) | 290 |
| 4.7.1 | <i>The RF CAD Approach</i> | 291 |
| 4.7.2 | <i>Modelling</i> | 293 |
| 4.7.3 | <i>Analysis</i> | 296 |
| 4.7.3.1 | Linear frequency domain analysis | 296 |

| | | |
|-------------|--|------------|
| 4.7.3.2 | Non-linear time domain transient analysis | 297 |
| 4.7.3.3 | Non-linear convolution analysis | 297 |
| 4.7.3.4 | Harmonic balance analysis | 297 |
| 4.7.3.5 | Electromagnetic analysis | 298 |
| 4.7.3.6 | Planar electromagnetic simulation | 298 |
| 4.7.4 | <i>Optimisation</i> | 298 |
| 4.7.4.1 | Optimisation search methods | 299 |
| 4.7.4.2 | Error function formulation | 300 |
| 4.7.5 | <i>Further Features of RF CAD Tools</i> | 302 |
| 4.7.5.1 | Schematic capture of circuits | 302 |
| 4.7.5.2 | Layout-based design | 302 |
| 4.7.5.3 | Statistical design of RF circuits | 303 |
| Appendix I | | 306 |
| Appendix II | | 306 |
| References | | 310 |
| 5 | Mixers: Theory and Design | 311 |
| | <i>L. de la Fuente and A. Tazon</i> | |
| 5.1 | Introduction | 311 |
| 5.2 | General Properties | 311 |
| 5.3 | Devices for Mixers | 313 |
| 5.3.1 | <i>The Schottky-Barrier Diode</i> | 313 |
| 5.3.1.1 | Non-linear equivalent circuit | 313 |
| 5.3.1.2 | Linear equivalent circuit at an operating point | 314 |
| 5.3.1.3 | Experimental characterization of Schottky diodes | 317 |
| 5.3.2 | <i>Bipolar Transistors</i> | 319 |
| 5.3.3 | <i>Field-Effect Transistors</i> | 321 |
| 5.4 | Non-Linear Analysis | 322 |
| 5.4.1 | <i>Intermodulation Products</i> | 323 |
| 5.4.2 | <i>Application to the Schottky-Barrier Diode</i> | 327 |
| 5.4.3 | <i>Intermodulation Power</i> | 327 |
| 5.4.4 | <i>Linear Approximation</i> | 329 |
| 5.5 | Diode Mixer Theory | 331 |
| 5.5.1 | <i>Linear Analysis: Conversion Matrices</i> | 332 |
| 5.5.1.1 | Conversion matrix of a non-linear resistance/conductance | 333 |
| 5.5.1.2 | Conversion matrix of a non-linear capacitance | 335 |
| 5.5.1.3 | Conversion matrix of a linear resistance | 336 |
| 5.5.1.4 | Conversion matrix of the complete diode | 337 |
| 5.5.1.5 | Conversion matrix of a mixer circuit | 337 |
| 5.5.1.6 | Conversion gain and input/output impedances | 338 |
| 5.5.2 | <i>Large Signal Analysis: Harmonic Balance Simulation</i> | 339 |
| 5.6 | FET Mixers | 341 |
| 5.6.1 | <i>Single-Ended FET Mixers</i> | 341 |
| 5.6.1.1 | Simplified analysis of a single-gate FET mixer | 341 |
| 5.6.1.2 | Large-signal and small-signal analysis of single-gate FET mixers | 343 |
| 5.6.1.3 | Other topologies | 346 |
| 5.7 | Double-Gate FET Mixers | 349 |
| 5.7.1 | <i>IF Amplifier</i> | 354 |
| 5.7.2 | <i>Final Design</i> | 355 |
| 5.7.3 | <i>Mixer Measurements</i> | 356 |

| | | |
|----------|--|------------|
| 5.8 | Single-Balanced FET Mixers | 358 |
| 5.9 | Double-Balanced FET Mixers | 359 |
| 5.10 | Harmonic Mixers | 360 |
| | 5.10.1 <i>Single-Device Harmonic Mixers</i> | 362 |
| | 5.10.2 <i>Balanced Harmonic Mixers</i> | 362 |
| 5.11 | Monolithic Mixers | 364 |
| | 5.11.1 <i>Characteristics of Monolithic Medium</i> | 365 |
| | 5.11.2 <i>Devices</i> | 366 |
| | 5.11.3 <i>Single-Device FET Mixers</i> | 366 |
| | 5.11.4 <i>Single-Balanced FET Mixers</i> | 368 |
| | 5.11.5 <i>Double-Balanced FET Mixers</i> | 370 |
| | Appendix I | 375 |
| | Appendix II | 375 |
| | References | 376 |
| 6 | Filters | 379 |
| | <i>A. Mediavilla</i> | |
| 6.1 | Introduction | 379 |
| 6.2 | Filter Fundamentals | 379 |
| | 6.2.1 <i>Two-Port Network Definitions</i> | 379 |
| | 6.2.2 <i>Filter Description</i> | 381 |
| | 6.2.3 <i>Filter Implementation</i> | 383 |
| | 6.2.4 <i>The Low Pass Prototype Filter</i> | 383 |
| | 6.2.5 <i>The Filter Design Process</i> | 384 |
| | 6.2.5.1 <i>Filter simulation</i> | 384 |
| 6.3 | Mathematical Filter Responses | 385 |
| | 6.3.1 <i>The Butterworth Response</i> | 385 |
| | 6.3.2 <i>The Chebyshev Response</i> | 386 |
| | 6.3.3 <i>The Bessel Response</i> | 390 |
| | 6.3.4 <i>The Elliptic Response</i> | 390 |
| 6.4 | Low Pass Prototype Filter Design | 393 |
| | 6.4.1 <i>Calculations for Butterworth Prototype Elements</i> | 395 |
| | 6.4.2 <i>Calculations for Chebyshev Prototype Elements</i> | 400 |
| | 6.4.3 <i>Calculations for Bessel Prototype Elements</i> | 404 |
| | 6.4.4 <i>Calculations for Elliptic Prototype Elements</i> | 405 |
| 6.5 | Filter Impedance and Frequency Scaling | 405 |
| | 6.5.1 <i>Impedance Scaling</i> | 405 |
| | 6.5.2 <i>Frequency Scaling</i> | 410 |
| | 6.5.3 <i>Low Pass to Low Pass Expansion</i> | 410 |
| | 6.5.4 <i>Low Pass to High Pass Transformation</i> | 412 |
| | 6.5.5 <i>Low Pass to Band Pass Transformation</i> | 414 |
| | 6.5.6 <i>Low Pass to Band Stop Transformation</i> | 418 |
| | 6.5.7 <i>Resonant Network Transformations</i> | 421 |
| 6.6 | Elliptic Filter Transformation | 423 |
| | 6.6.1 <i>Low Pass Elliptic Translation</i> | 423 |
| | 6.6.2 <i>High Pass Elliptic Translation</i> | 425 |
| | 6.6.3 <i>Band Pass Elliptic Translation</i> | 426 |
| | 6.6.4 <i>Band Stop Elliptic Translation</i> | 426 |
| 6.7 | Filter Normalisation | 429 |
| | 6.7.1 <i>Low Pass Normalisation</i> | 429 |

| | | |
|----------|---|------------|
| 6.7.2 | <i>High Pass Normalisation</i> | 430 |
| 6.7.3 | <i>Band Pass Normalisation</i> | 431 |
| 6.7.3.1 | Broadband band pass normalisation | 432 |
| 6.7.3.2 | Narrowband band pass normalisation | 433 |
| 6.7.4 | <i>Band Stop Normalisation</i> | 435 |
| 6.7.4.1 | Broadband band stop normalisation | 436 |
| 6.7.7.2 | Narrowband band stop normalisation | 438 |
| 7 | Oscillators, Frequency Synthesisers and PLL Techniques | 461 |
| | <i>E. Artal, J. P. Pascual and J. Portilla</i> | |
| 7.1 | Introduction | 461 |
| 7.2 | Solid State Microwave Oscillators | 461 |
| 7.2.1 | <i>Fundamentals</i> | 461 |
| 7.2.1.1 | An IMPATT oscillator | 463 |
| 7.2.2 | <i>Stability of Oscillations</i> | 466 |
| 7.3 | Negative Resistance Diode Oscillators | 467 |
| 7.3.1 | <i>Design Technique Examples</i> | 469 |
| 7.4 | Transistor Oscillators | 469 |
| 7.4.1 | <i>Design Fundamentals of Transistor Oscillators</i> | 471 |
| 7.4.1.1 | Achievement of the negative resistance | 472 |
| 7.4.1.2 | Resonator circuits for transistor oscillators | 473 |
| 7.4.2 | <i>Common Topologies of Transistor Oscillators</i> | 475 |
| 7.4.2.1 | The Colpitts oscillator | 476 |
| 7.4.2.2 | The Clapp oscillator | 477 |
| 7.4.2.3 | The Hartley oscillator | 477 |
| 7.4.2.4 | Other practical topologies of transistor oscillators | 478 |
| 7.4.2.5 | Microwave oscillators using distributed elements | 478 |
| 7.4.3 | <i>Advanced CAD Techniques of Transistor Oscillators</i> | 479 |
| 7.5 | Voltage-Controlled Oscillators | 481 |
| 7.5.1 | <i>Design Fundamentals of Varactor-Tuned Oscillators</i> | 481 |
| 7.5.2 | <i>Some Topologies of Varactor-Tuned Oscillators</i> | 482 |
| 7.5.2.1 | VCO based on the Colpitts topology | 482 |
| 7.5.2.2 | VCO based on the Clapp topology | 483 |
| 7.5.2.3 | Examples of practical topologies of microwave VCOs | 483 |
| 7.6 | Oscillator Characterisation and Testing | 484 |
| 7.6.1 | <i>Frequency</i> | 485 |
| 7.6.2 | <i>Output Power</i> | 485 |
| 7.6.3 | <i>Stability and Noise</i> | 485 |
| 7.6.3.1 | AM and PM noise | 486 |
| 7.6.4 | <i>Pulling and Pushing</i> | 488 |
| 7.7 | Microwave Phase Locked Oscillators | 489 |
| 7.7.1 | <i>PLL Fundamentals</i> | 489 |
| 7.7.2 | <i>PLL Stability</i> | 493 |
| 7.8 | Subsystems for Microwave Phase Locked Oscillators (PLOs) | 493 |
| 7.8.1 | <i>Phase Detectors</i> | 494 |
| 7.8.1.1 | Exclusive-OR gate | 495 |
| 7.8.1.2 | Phase-frequency detectors | 496 |
| 7.8.2 | <i>Loop Filters</i> | 501 |
| 7.8.3 | <i>Mixers and Harmonic Mixers</i> | 505 |
| 7.8.4 | <i>Frequency Multipliers and Dividers</i> | 506 |

| | | |
|--------------|---|------------|
| 7.8.4.1 | Dual modulus divider | 506 |
| 7.8.4.2 | Multipliers | 508 |
| 7.8.5 | <i>Synthesiser ICs</i> | 508 |
| 7.9 | Phase Noise | 509 |
| 7.9.1 | <i>Free running and PLO Noise</i> | 513 |
| 7.9.1.1 | Effect of multiplication in phase noise | 514 |
| 7.9.2 | <i>Measuring Phase Noise</i> | 514 |
| 7.10 | Examples of PLOs | 514 |
| | References | 518 |
| Index | | 519 |

