

# Index

## *Numerics*

- 1:1 transformer, 108
- 60/40 rosin core, of solder, 196
- 555 timer
  - blinky lights project, 329–330
  - in circuit builder kit, 207
  - integrated circuits, 159–164
  - lighting effects project, 349
  - siren project, 339–340
- 4017 decade counter, 165–166, 207

## • A •

- AC. *See* alternating current (AC)
- acceptor dopants, for semiconductors, 114
- acoustic energy, 183
- Action Electronics (Web site), 372
- active components, 32
- AC-to-DC adapters, 26
- actual resistance, 43
- adhesives, 203
- air, as inductor core, 100
- air dielectric, 78
- air-core transformer, 229
- alarm clocks, 70
- alarms
  - 555 timer for, 160
  - light project, 343–344
  - siren project, 338–340
- alkaline batteries, 175, 375
- All About Circuits (Web site), 369, 371
- All Electronics (Web site), 363
- Allied Electronics (Web site), 364
- alligator clips
  - in capacitor discharging example, 68
  - in circuit builder starter kit, 208
  - for soldering, 248, 250
- Alltronics (Web site), 372
- alternating current (AC)
  - capacitive reactance of, 81–83
  - capacitors to pass, 69–70
  - coupling, 71
  - current direction reversals in, 27
  - defined, 22, 209, 375
  - electromagnetic induction of, 94
  - function generator for, 356
  - in inductor-containing circuits, 97
  - not recommended for circuits, 177–178
  - oscilloscope waveform, 286–287, 289
  - overview, 22, 24–26
  - rectification of, 112, 121–122
  - on schematics, 223, 225
  - speaker resistance to, 187
  - voltage, 25
- aluminum electrolytic dielectric materials, 73–74
- American Science and Surplus (Web site), 373
- ammeter, 235, 261
- ampere (amp), 13, 375
- amp-hour rating for batteries, 34, 176
- amplifiers
  - building, 345–346
  - common-emitter, 137
  - operational, 157–158, 207, 230, 380
  - for radio-receiver system, 36
- amplitude
  - of audio waveform, 296
  - defined, 285, 375
  - of voltage, 285
- analog electrical signals, 36
- analog integrated circuits (ICs), 145
- analog-to-digital (A/D) converter, 166
- AND gate, 148–150, 231
- anode
  - as battery terminal, 23–24
  - defined, 23, 375
  - in pn-junction, 116

antenna, 36, 185, 234  
anti-static wrist strap, 204, 216, 218, 248  
application notes, on datasheets, 157  
approximate value ( $\approx$ ), 57  
approximation of signal frequency, 299  
*The Art of Electronics* (Hayes and Horowitz), 137  
artist brushes, 202  
artwork, 220. *See also* schematics  
astable multivibrator  
  in blinky light project, 329  
  555 timer as, 159–162  
  in siren project, 340  
atoms, electrical charge of, 11–12  
attenuating frequencies, 89–90  
audible frequency range, 187  
automobile audio systems, 70  
auto-ranging feature, in multimeter, 263, 266, 375  
axial leads, in capacitors, 74

## • B •

back voltage, 95  
band-pass and band-reject filters, 90  
bands, on resistors, 45–46  
band-stop filters, 105  
bandwidth  
  defined, 157, 375  
  operational amplifier, 157  
  oscilloscope, 288–289  
base 2 system, 146–147  
base 10 system, 146–147  
base leads, in transistors, 126, 128  
base-collector junction, in NPN transistor, 129  
base-emitter junction, in NPN transistor, 129–131  
bat detector circuit, 356  
batteries  
  amp-hour rating for, 34, 176  
  capacitors compared to, 66–68  
  in circuit builder starter kit, 208  
  for circuit projects, 304  
  current supplied by, 60  
  defined, 375  
  direct current from, 22–24  
  in light bulb circuit example, 28  
  oscilloscope to test, 295–296  
  schematics of, 221–224  
  types of, 173–176  
battery clips and holders, 208  
BG Micro (Web site), 364  
biasing  
  defined, 117, 376  
  diodes, 117–118  
  transistors, 135–136, 182  
  voltage, 117–118  
bimetallic strip temperature sensors, 185  
binary system, 36, 145–147  
bipolar transistor  
  for circuit projects, 321–323  
  in Darlington pair, 137  
  defined, 126–127, 376  
  identifying, 139–140  
  overview, 126–127  
  phototransistor as, 182  
  testing, 275–276  
bistable multivibrator, 163–164  
bits (binary digits), 36, 146–147  
bleeder jumper, to discharge capacitors, 274  
block diagram for radio-receiver system, 37  
bonding, in crystals, 112  
Bowden's Hobby Circuits (Web site), 370–371  
breadboard, 170, 376. *See also* solderless breadboard  
break, in schematics, 221  
breakdown voltage, 115, 122  
bridge, in schematics, 221  
bus (connection point), 254–255, 376  
buzzers, 188

## • C •

- CA (cyanoacrylate) glue, 203
- cable
  - defined, 172, 376
  - ribbon, 172
  - testing, 276–277
- calculators, 19, 304, 370
- calibrating, 184, 268
- cameras, capacitors in, 70
- capacitance, 72, 247, 376
- capacitive coupling, 71
- capacitors
  - batteries compared to, 66
  - capacitive reactance in, 81–83, 88, 103
  - capacity of, 72–73
  - charging and discharging, 67–70, 313–316
  - in circuit builder starter kit, 207
  - in circuits, 90, 304
  - defined, 66, 376
  - dielectric types for, 73–74
  - inductors compared to, 99
  - inductors with, 91
  - multimeter to test, 274–275, 278
  - in parallel, 79–80
  - polarity of, 75–76, 331
  - purpose of, 70–71
  - in RC filters, 87–90
  - resistors with, 83–87
  - on schematics, 229
  - in series, 80–81
  - shapes and sizes of, 74
  - static shocks from, 215
  - to store electrical energy, 32, 66–67
  - values of, 76–78
  - variable, 78–79
  - for voltage swings, 42
  - working voltage for, 73
- cathode
  - as battery terminal, 23–24
  - defined, 23, 376
  - in pn-junction, 116
- cathode-ray tube (CRT), 18, 37
- cell, in battery, 24
- cellphones, 19
- ceramic dielectric materials, 73–74
- ceramic resonators, 106
- changeover switch, 181
- changing readings, detecting, 263
- charge, electric, 11, 13
- charging capacitors
  - experiment, 313–316
  - Ohm’s Law for, 84
  - process, 67–70
- chassis ground, 223, 226
- chemical energy, 30
- chip, 144. *See also* integrated circuits (ICs)
- chip assembly, 153
- chip densities, 144
- chokes, 95. *See also* inductors
- circle containing waveform, on schematics, 225
- circuit board, 47. *See also* printed circuit boards (PCBs)
- circuit breadboard, 240. *See also* solderless breadboard
- circuit builder starter kit, 207–208
- circuit simulator, 359–360
- circuits. *See also* ground; integrated circuits (ICs); multimeter; open circuits
  - AC, 27
  - bat detector, 356
  - batteries connected to, 174–175
  - for blinking light project, 330–333
  - capacitive, 65, 90
  - capacitors in, 71
  - in cellphones, 19
  - closed, 28
  - combination, 34–35
  - defined, 17, 376
  - for electrons, 15–17
  - frequency-sensitive, 357
  - inductors in, 99–102
  - Internet resources for, 370–371
  - live, 213, 215, 379

- circuits (*continued*)
  - loaded by logic probes, 284
  - mixed signal, 359
  - Ohm's Law
    - to analyze, 56–62
    - to design, 62–63
  - oscillator, 106
  - parallel, 33–34
  - power isolated from, 108
  - RC
    - impedance in, 103
    - operation of, 84–85
    - RC time constant for, 86, 90, 315–316, 381
    - timers created with, 86–87
  - resistors in, 64
  - RF (radio-frequency), 355, 357
  - RL
    - impedance in, 103
    - inductors in, 101–102
    - RL time constants for, 102
  - RLC, 104–106
  - semiconductor diodes in, 120–125
  - semiconductors in, 141
  - series, 33
  - short
    - defined, 96, 382
    - inductors as, 96–97
    - ohmmeter to test for, 276–277
  - single point in, 29
  - tuning
    - inductors in, 99–102
    - overview, 71
    - resonance in, 105
- circuits, constructing. *See* solderless
  - breadboard
  - permanent, 252–257
  - soldering for, 247–252
- circuits, projects on
  - capacitor charging and discharging, 313–316
  - logic gates, 323–326
  - Ohm's Law in
    - parallel parking resistors, 311–313
    - in series circuit, 306–309
    - voltage division, 309–311
  - overview, 303–305
  - transistors, 321–323
  - voltage drop across diodes, 317–320
- Circuits Specialists (Web site), 372
- cladding, of printed circuit boards, 257, 376
- clock signals, 152
- clocking logic chips, 159
- clocking notch, on integrated
  - circuits, 154–155, 332
- closed circuit, 28, 376
- closed position, of switches, 179, 376
- cloths and cleansers in workshop, 200–202
- CMOS (complementary metal-oxide semiconductor), 164, 246, 253
- coils, 95, 107–108. *See also* inductors
- cold solder joint, 250, 376
- collector leads, in transistors, 126, 129
- color coding, 45–46, 171
- combination circuit, 34–35
- combination plate integrated
  - circuits (ICs), 145
- common ground, 30, 223, 226
- common-emitter amplifier, 137
- commutator, in DC motors, 189, 376
- compass, electronic, 340–343
- complementary metal-oxide
  - semiconductor (CMOS), 164, 246, 253
- components. *See* electronic components
- compressed air, 200
- computers, electronic components in, 19
- condenser microphone, 79, 183
- conductors
  - defined, 12, 377
  - overview, 12–13
  - resistance of, 40
  - semiconductors as, 112–116
  - wire form of, 15

connection. *See also* parallel connection;  
series connection  
bus, 254–255  
on schematics, 219–220, 235  
on solderless breadboard, 245  
connectors, 172–173  
constant resistance, 59  
contact cleaner, 202  
contact holes, on solderless  
breadboard, 205, 240  
continuity tests, 262, 377  
conventional current, 26–27, 222, 377  
copper, as conductor, 15  
cord of wire, 172  
cotton swabs, 202  
coulomb (charge measurement), 13  
counter-surveillance, infrared detector  
for, 337–338  
coupling capacitor, 71  
covalent bond, in crystals, 112  
CPR (cardio-pulmonary resuscitation), 214  
cross-reference book of diode data, 119  
CRT (cathode-ray tube), 18, 37  
crystal microphone, 183  
crystals, 106, 112, 230. *See also*  
semiconductors  
current. *See also* alternating current  
(AC); capacitors; direct current (DC);  
inductors; resistance  
ampere (amp) measurement of, 13  
amplifying, 321–322  
controlling, 31–32  
conventional, 26–27, 222, 377  
defined, 11, 12, 377  
diodes for, 118–119, 125  
electron movement as, 12  
forward, 117, 124  
leakage, 70  
in light bulb circuit example, 27–30  
limiting, 330  
magnetism to induce, 94  
maximum collector, 139  
multimeter to measure, 270–272

overview, 11  
in power calculation, 16  
for radio-receiver system, 35–37  
real electron flow compared to, 26–27  
reverse, 118  
rheostat handling of, 47  
series and parallel connections, 33–35  
sink, 156  
source, 156  
supply, 312  
for television, 37–38  
current gain ( $h_{FE}$ ), 132, 139  
current rating of diodes, 119  
cuticle sticks, 202  
cut-off frequency, 89–90, 102  
cycle, in alternating current, 25, 377

## • D •

Darlington pair of transistors, 137  
datasheets, integrated circuit  
(ICs), 149, 154, 156–157  
DC. *See* direct current (DC)  
DC motors, 189–190  
decibel level, 188  
decimal system, 146, 147  
decision making. *See* integrated  
circuits (ICs)  
degreaser, 202  
DeGunther, Rik (*Solar Power Your Home  
For Dummies*), 26  
delayed sweep, in oscilloscopes, 289  
desoldering iron, 251  
desoldering pump, 251, 377  
detector, for radio-receiver system, 36  
dial pots, 47  
diaphragm, 183, 188  
dielectrics  
air, 78  
in capacitor testing, 274  
as insulators, 66  
types of, 73–74  
differential amplifier, 157

- Digi-Key (Web site), 364
  - digital circuits, 145
  - digital electrical signals, 36
  - digital format, 36
  - digital integrated circuits (ICs), 145
  - digital logic, 147
  - digital storage, in oscilloscopes, 289
  - digital waveform, 286
  - digital-to-analog (D/A) converter, 166
  - dimers, 10, 43
  - “dinsmore compass,” 342
  - diodes. *See also* LEDs (light-emitting diodes); semiconductors; Zener diode
    - in circuit builder starter kit, 207
    - for circuit projects, 304
    - conducting current through, 118–119
    - current restricted by, 32
    - defined, 116, 377
    - junction, 116–120
    - multimeter to test, 275, 278
    - rectifier, 121
    - reverse-biasing, 117, 120–121, 131
    - on schematics, 230
    - semiconductor, 120–125
    - signal, 121
    - unbiased, 118
    - as variable capacitors, 78
    - voltage drop across, 317–320
  - DIPs (dual in-line packages), for integrated circuits, 153
  - direct current (DC)
    - to capacitor, 81
    - capacitors to stop, 71
    - defined, 22, 209, 377
    - motors, 189–190
    - oscilloscope waveform, 285–286, 288–289
    - overview, 22–24
    - rectification of, 112
    - on schematics, 223
    - solderless breadboard used with, 240
    - “split,” 224
  - direction of current, 27
  - disable pin, in integrated circuits, 165
  - discharging capacitors
    - experiment, 313–316
    - Ohm’s Law for, 85
    - process, 67–70
  - Discover Circuits (Web site), 371
  - discrete components, in solderless breadboard, 205
  - discussion forums, Internet, 371–372
  - D&L Products (Web site), 372
  - donor dopants, for semiconductors, 114
  - dopants, for semiconductors, 113–114
  - double-pole double-throw (DPDT) switch, 181, 233, 277, 377
  - double-pole single-throw (DPST) switch, 181, 233, 277, 377
  - double-pole switch, 180, 377
  - double-sided foam tape, 203
  - double-throw switch, 180
  - drain, in field-effect transistors, 127
  - drum line, 336
  - dual in-line packages (DIPs), for integrated circuits (ICs), 153
  - dual-gate MOSFETs (metal-oxide-semiconductor FETs), 127, 140
  - dual-trace oscilloscope, 290, 294
  - Dummer, Geoffrey (integrated circuit concept), 144
  - dynamic microphone, 183
- E ●**
- earth ground, 30, 223, 226, 377
  - eBay (Web site), 361
  - EDAboard International Electronics Forum Center (Web site), 371
  - Edison, Thomas (inventor), 14
  - electric charge, 11, 13
  - electric current. *See* current
  - electrical circuit, 10. *See also* circuits
  - electrical energy. *See also* current
    - dangers of, 210–214
    - overview, 11

- source of, 16
  - transformation of, 14
  - electrical signals, 36
  - electrically neutral atoms, 12
  - electricity, 10–11, 378. *See also* current
  - electrochemical reaction, 22
  - electrocution, 3, 214
  - electromagnet, 93
  - electromagnetic induction, 24, 94, 183
  - electromagnetism, 92–93, 378. *See also* inductors
  - electromotive force, 378
  - electronic compass, 340–343
  - electronic components
    - current controlled by, 31–32
    - defined, 17, 377
    - in devices, 17–19
    - discrete, 205
    - Joule’s Law for, 63
    - logical, 151–152
    - on schematics, 228–230
    - solderless breadboard connections for, 245
    - transistors in, 141
    - values of, 228
  - Electronic Goldmine (Web site), 364–365
  - electronic systems
    - conductors, 12–13
    - description, 10–11
    - devices using, 17–19
    - electrons in atoms, 11–12
    - voltage, 13–14
    - work done by, 14–17. *See also* power
  - Electronics Calculator Web site, The, 370
  - electronics cleanser, 202
  - Electronics Converters and Calculators (Web site), 370
  - Electronics Hobbyist (Web site), 369
  - electronics kits, ready-made, 354
  - Electronics Lab (Web site), 371
  - Electronics Zone Discussion (Web site), 371
  - electrons
    - charge of, 11–12
    - conductive circuits for, 15–17
    - defined, 11, 378
    - electrical energy of, 15
    - movement of, 12–13
    - recombining, 131
    - in transistor emitter to collector, 131
    - valence, 112–113
  - electrostatic discharge (ESD), 127, 215, 378. *See also* static electricity
  - emitter leads, in transistors, 126, 129
  - en masse* movement of electrons, 12
  - epoxy cement, 203
  - equivalent capacitance, 79–80
  - equivalent resistance
    - of complex circuits, 60
    - formula for, 312
    - overview, 49
    - of parallel resistors, 51–52
    - of series resistors, 50–51
  - Europe, schematic symbols in, 238
  - European Union Restriction on Hazardous Substances (RoHS) regulations, 367
  - expanded notation for numbers, 146
  - experimenter’s PC board, 253–254
- **F** ●
- Fair Radio Sales (Web site), 373
  - Fairchild Semiconductor, 144
  - Faraday, Michael (scientist), 14, 92
  - farads, capacitance measured in, 72–73
  - Farnell (Web site, U.K.), 366
  - $F_c$  symbol (cut-off frequency), 89
  - ferrite, as inductor core, 100
  - FET. *See* field-effect transistors (FET)
  - fiber-optic microphone, 183
  - field-effect transistors (FET)
    - CMOS technology for, 164
    - dual-gate, 140
    - electrostatic discharge (ESD) sensitivity of, 216

- field-effect transistors (FET) (*continued*)
  - in integrated circuits, 127
  - on schematics, 230
- fillet of solder, 250, 378
- filters
  - band-pass, 90
  - band-reject, 90
  - band-stop, 105
  - capacitors as, 71, 87–90, 104
  - frequency-sensitive circuits as, 357
  - inductors as, 101–102, 104
- first value band on resistors, 45
- first-aid charts, 214
- first-aid kit, 204
- 555 timer
  - blinking lights project, 329–330
  - circuit builder starter kit, 207
  - integrated circuits, 159–164
  - lighting effects project, 349
  - siren project, 339–340
- fixed inductors, 100
- fixed resistors, 43–47, 207
- fixed resistors (zigzag line as symbol), 43
- flashing lights, 555 timer for, 159, 329–330
- flat-head screwdrivers, 200, 378
- flip-flop circuit, 163
- floating ground, 30, 378
- flow of electrons. *See* current
- flux, for soldering, 197
- flux lines, from magnetism, 92–93, 378
- foam tape, 203
- force, 16, 92–93, 378
- forward current, 117, 124
- forward voltage, 117, 124
- forward-bias a diode
  - light energy release in, 123–125
  - by multimeter, 120
  - process, 117
  - in rectifying AC, 121
  - in transistors, 131
- fossil fuels, 24
- 4017 decade counter, 165–166, 207

- Franklin, Benjamin (electricity experiments), 14, 30, 209
- “free” electrons, 12
- frequency
  - alternating current (Hertz), 25
  - of buzzer, 188
  - capacitive reactance vary
    - with, 81–83, 88–90
  - capacitors to tune, 71
  - cut-off, 89–90, 102
  - defined, 25, 378
  - inductors vary with, 99
  - operational amplifiers for, 157
  - oscilloscope approximation of, 299
  - of quartz crystals, 106
  - in RC filter design, 87–90
  - resonance, 104
  - speaker range of, 187
- frequency counter, 299, 355–356
- frequency-sensitive circuit, 357
- full-wave rectification, 122
- fully charged capacitor, 68, 85
- function generator, 297, 356
- fuse
  - in AC-powered circuits, 213
  - correct input for, 272
  - ohmmeter to check, 262
  - resistance measuring of, 278

## ● G ●

- gain
  - current ( $h_{FE}$ ), 132, 139
  - defined, 29, 378
  - voltage, 136–137
- gates (logic gates)
  - circuit project on, 323–326
  - data processing with, 148–150
  - defined, 148, 379
  - diodes for, 125
  - in field-effect transistors, 127–128
  - in integrated circuits (ICs), 148–150

- on schematics, 231
- truth tables for, 150–152
- Gateway Electronics (Web site), 373
- gauge, of wire, 171, 378
- gear head, in DC motors, 190
- glue, 203
- glue gun, 203
- gold third value band on resistors, 45
- Graham Knott's Web site, 369
- grid boards, 254
- ground
  - common, 223
  - defined, 29, 378
  - multimeter receptacle for, 265
  - overview, 30
  - reference, 29
  - on schematics, 224, 226–227
  - on solderless breadboard rail, 245
  - for tools, 217–218
- “gull wing” leads, 153

## • H •

- half-wave rectification, 121
- halving resistance value, 51
- hand tools, 199–200
- Hayes, Thomas C. (*The Art of Electronics*), 137
- heat dissipation, 97
- heat energy, 15
- heat sensors, 183–184
- heat sink, 49, 378
- helping hands clamp, 200, 249, 378
- Henry, Joseph (scientist), 95
- henrys, as inductance measure, 95
- Hertz (Hz) frequency measure, 25, 378
- $h_{FE}$  symbol (current gain), 132, 139
- high voltage warnings, 211, 379
- high-load applications, 49
- high-pass filter
  - capacitor as, 104
  - design of, 88–89
  - RL circuit as, 101–102

- high-precision capacitor, 72
- high-precision resistor, 43, 46
- Horowitz, Paul (*The Art of Electronics*), 137
- hot-melt glue gun, 203
- household electronics, 48
- hydroelectric power plant, 24

## • I •

- $I_C$  max symbol (maximum collector current), 139, 379
- ICs. *See* integrated circuits (ICs)
- impedance
  - defined, 59, 379
  - formulas for, 103–104
  - in RLC circuits, 104–105
  - of speakers, 187
- incandescent lamp, 234
- induced current, 24, 94
- inductance
  - henrys, as measure for, 95
  - L symbol for, 95
  - mutual, 107
  - self-, 95, 107
- inductors (induction coil)
  - in circuits, 99–102
  - defined, 91, 379
  - inductive reactance of, 98–99, 103
  - overview, 91, 95–97
  - on schematics, 229
  - to store electrical energy, 32
  - in tuning circuits, 104–106
  - unshielded, 91, 107–109
- infrared light
  - detector project, 336–338
  - light-emitting diodes (IR LEDs), 123
  - presence or absence of, 184
- infrared temperature sensors, 185, 379
- input transducers, 181, 186
- instantaneous current, 25
- insulators
  - defined, 66, 379
  - dielectrics as, 66

insulators (*continued*)  
 electrons of, 12  
 inductors as, 100  
 semiconductors as, 112–116

integrated circuits (ICs)  
 for circuit projects, 304  
 datasheets on, 156–157  
 defined, 141, 379  
 electrostatic discharge (ESD) sensitivity  
 of, 216  
 555 timer as, 159–164  
 4017 decade counter as, 165–166  
 linear, digital, and combination plate, 145  
 logic for decision making with  
 binary system for, 145–147  
 gates in, 148–150  
 logical components for, 151–152  
 truth tables in, 150–151  
 microcontrollers as, 166  
 miniaturized circuits on, 2  
 operational amplifiers as, 157–158  
 packaging, 153–154  
 part numbers to identify, 152–153  
 pinouts of, 154–156  
 plug-and-play, 253  
 purpose of, 144  
 resistors to limit current to, 41  
 on schematics, 231–232  
 on solderless breadboard, 205  
 transistors in, 141  
 unloaded pulse sensitivity of, 358  
 wire wrapped sockets for, 255  
 working with, 166–167

Internet. *See* Web resources

inverse proportionality, of resistors in  
 parallel, 52

inverter, as NOT gate  
 defined, 379  
 description of, 148  
 on schematics, 231  
 truth table for, 150

inverting amplifier, 157–158, 379  
 isolation transformers, 108

## • J •

jacks, 172, 234–235, 379  
 Jameco Electronics (Web site), 365  
 JFETs (junction FETs), 127  
 Job, Steve (Apple, Inc., chairman), 126  
 joint, solder, 247, 250, 262  
 Joule, James Prescott (Joule's Law), 63  
 Joule's Law, 63–64, 379  
 joystick controls, 43  
 jumper wires, 208, 243  
 junction diode, 116–120  
 junction FETs, 127

## • K •

k symbol (kilohms), 238  
 Kelsey Park School Electronics Club (Web  
 site), 370–371  
 Kilby, Jack (integrated circuits), 144  
 Kirchoff's Voltage Law, 29, 305  
 Knott, Graham (electronics teacher), 369

## • L •

L symbol (inductance), 95  
 lamp, incandescent, 234  
 lantern battery, 174  
 layout diagrams, 220. *See also* schematics  
 LCD (liquid-crystal display), for  
 television, 37  
 LDRs (light-dependent resistors), 182  
 leads  
 axial, 74  
 base, 126, 128  
 collector, 126, 129  
 correct connections for, 237  
 emitter, 126, 129  
 "gull wing," 153  
 radial, 74  
 for switches, 28  
 leaf switch, 179

- leakage current, 70
  - LEDs (light-emitting diodes)
    - blinky light project, 328–333
    - in circuit builder starter kit, 207
    - circuit diagram for, 41–42
    - for circuit projects, 304, 317–319
    - forward-biased, 123–125
    - lighting effects project, 349–350
    - Ohm's Law for, 62
    - on schematics, 230, 234
  - light, from electrical energy, 15
  - light bulb circuit example, 27–30
  - light machine oil, 203
  - light-dependent resistors (LDRs), 182
  - light-emitting diodes. *See* LEDs (light-emitting diodes)
  - light-sensitive devices, as sensors, 182, 184
  - lighting-effects generator project, 165, 348–350
  - lightning, 14, 215
  - linear integrated circuits, 145
  - linear power supply, 122
  - linear resistance tracks, 47
  - liquid-crystal display (LCD), for television, 37
  - lithium batteries, 175, 379
  - live circuit, 213, 215, 379
  - load
    - for electrical energy, 16
    - high-wattage resistors for, 49
    - of logic probes, 284
    - voltmeter to measure, 260
    - Zener diode for, 123
  - logic, integrated circuits for
    - binary system for, 145–147
    - logical components for, 151–152
    - on schematics, 231–232
    - truth tables in, 150–151
    - types of, 164
  - logic analyzer, 359
  - logic chips, clocking, 159
  - logic gates
    - circuit project on, 323–326
    - data processing with, 148–150
    - defined, 148, 379
    - diodes for, 125
    - in field-effect transistors, 127–128
    - in integrated circuits (ICs), 148–150
    - on schematics, 231
    - truth tables for, 150–152
  - logic probe. *See also* oscilloscope
    - defined, 281–282
    - digital circuits tested with, 281–283
    - fast changing signals tested with, 269
    - operation of, 283–285
  - logic pulser, 357–358
  - loop, in schematics, 221
  - low-pass filter
    - defined, 88, 380
    - description of, 88
    - inductors as, 104
    - resistor and inductor roles in, 102
  - Low-Power Schottky series of TTL, 164
  - low-static clothing, 216
  - lubricants, 202–203
- M •
- magnet, electromagnetic induction in, 24
  - magnetic field
    - electricity to produce, 92–94
    - inductor coils for
      - in circuits, 99–102
      - inductive reactance of, 98–99
      - overview, 95–97
      - unshielded, 107–109
    - in inductors and transformers, 32
  - magnetic tape head, 185
  - magnifying glass, 200
  - manufacturer's warranty, 363
  - Maplin (Web site), 366
  - Marlin P Jones & Associates (Web site), 373
  - matrix mathematics, 53
  - mats, anti-static, 216
  - maximum collector current, 139, 379
  - maximum collector-to-emitter voltage, 139

- maximum power dissipation, 139
  - maximum range, of multimeter, 266
  - mechanical energy, 15
  - memory effect, in batteries, 176
  - metal-oxide-semiconductor field effect transistor. *See* MOSFET
  - metals, 12, 74
  - metronome, 158–159
  - mica dielectric materials, 73–74
  - microcontrollers, 166, 253, 380
  - microphones
    - condenser, 79, 183
    - crystal, 183
    - dynamic, 183
    - fiber-optic, 183
    - on schematics, 233
  - microprocessors, 147
  - milliamperes, 13, 27, 49
  - millihenrys, 95
  - miniaturized circuits, 2. *See also* integrated circuits (ICs)
  - minus sign, for cathode, 24
  - Minute Man Electronics (Web site), 372
  - mixed signal integrated circuits (ICs), 145, 359
  - monostable multivibrator, 162
  - Morse code, 36
  - MOSFET (metal-oxide-semiconductor field-effect transistors)
    - CMOS technology for, 164
    - dual-gate, 140
    - electrostatic discharge (ESD) sensitivity of, 216
    - in integrated circuits, 127
    - on schematics, 230
  - motion detectors, 184
  - motors, speed control for, 18
  - Mouser Electronics (Web site), 365
  - multimeter
    - analog, 263–264
    - circuit checking, 279
    - for circuit projects, 304
    - current measurement, 270–272
    - defined, 198, 380
    - digital, 263–266
    - overview, 198–199, 260–262
    - range of, 266–267
    - resistance measurement, 272–278
    - on schematics, 235
    - setting up, 267–268
    - voltage measurement, 268–270
  - multiple ground symbols, 227
  - Multisym simulator (National Instruments), 360
  - multivibrator
    - astable, 159–162, 329, 340
    - bistable, 163–164
    - monostable, 162
  - mutual inductance, 107
  - Mylar dielectric materials, 73–74
- *N* ●
- nail files, 202
  - NAND gate
    - description of, 148
    - in integrated circuit building, 167
    - Low-Power Schottky version of, 164
    - in projects, 324–326
    - on schematics, 231
    - universal gate name for, 149–150
  - National Electrical Code, 171
  - National Instruments, 360
  - NC (normally closed) switch, 179
  - needlenose pliers, 200, 247
  - negative current, waveform of, 25
  - negative temperature coefficient (NTC) thermistor, 183, 380
  - neon light project, 334–336
  - neutral, electrically, 12
  - new surplus merchandise, 363
  - nickel-cadmium (NiCd) batteries, 176, 380
  - nickel-metal hydride (NiMH) batteries, 176, 380
  - nippy cutters, 199
  - no ground symbol, 226

- Nobel Prize in Physics, 144  
 nominal value of resistors, 44–46, 380  
 non-inverting input, 157  
 non-rechargeable batteries, 175  
 NOR gate, 148–150, 231  
 normally closed (NC) switch, 179  
 normally open (NO) switch, 179  
 North Carolina State University Electronics  
 Tutorial (Web site), 370  
 NOT gate (inverter), 148, 150, 231  
 notation for numbers, expanded, 146  
 Noyce, Richard (integrated circuits), 144  
 NPN transistor  
 base-collector and base-emitter junctions  
 of, 129  
 for circuit projects, 321, 323  
 description of, 127  
 model of, 133–135  
 on schematics, 230  
 testing, 276  
 NTC (negative temperature coefficient)  
 thermistor, 183, 380  
 N-type semiconductors, 114–116, 380  
 numbers, notation for, 146
- 0 •
- Ocean State Electronics (Web site), 372  
*ohm* ( $\Omega$ )  
 as capacitive reactance measure, 81  
 defined, 41, 380  
 as inductive reactance measure, 98  
 as resistance measure, 41, 46  
 Ohm, Georg (Ohm's Law), 54–55  
 ohmmeter, 235, 262  
 Ohm's Law  
 to analyze circuits, 35  
 for bipolar transistor base current, 322  
 for capacitive circuits, 65  
 for capacitive reactance, 81–83  
 circuit analysis by, 39, 56–62  
 circuit design and alteration by, 62–63  
 defined, 35, 380  
 electricity dangers, 211  
 impedance in, 103  
 for inductive reactance, 98–99  
 for inductors, 91  
 Joule's Law with, 64  
 in LED (light-emitting diode)  
 example, 124–125  
 overview, 54–56  
 parallel parking resistors project, 311–313  
 series circuit project, 306–309  
 voltage division project, 309–311  
 1:1 transformer, 108  
 Online Guide to Beginners in Electronics  
 (Web site), 370  
 op-amp. *See* operational amplifier  
 (op-amp)  
 open circuits  
 battery switch as, 28  
 capacitive reactance as, 82  
 defined, 16, 380  
 inductor as, 97  
 transistor as, 137  
 open position, of switches, 179, 380  
 operational amplifier (op-amp)  
 in circuit building starter kit, 207  
 defined, 157, 380  
 as linear integrated circuit, 157–158, 224  
 on schematics, 230  
 OR gate  
 description of, 148  
 NAND gates converted to, 325–326  
 on schematics, 231  
 truth tables for, 150  
 Ørsted, Hans Christian (inventor), 92–93  
 oscillators  
 astable multivibrator as, 159–162  
 crystals in, 106  
 defined, 106, 380  
 oscilloscope. *See also* logic probe  
 bandwidth and resolution, 288–289  
 benefits of, 289–290  
 defined, 269, 381  
 fast-changing signals tested with, 269

oscilloscope (*continued*)

setup of, 290–293

signal display on, 293–295

testing with, 295–299

voltage changes in, 285–288

output transducer, 186

over range indicator, in multimeter, 266

overvoltage protection, diodes for, 125

## • p •

packaging, for integrated circuits

(ICs), 153–154

pads, on printed circuit boards, 257, 380

paper capacitor, 74

parallel connection

capacitors in, 79–80

for multimeter, 269

overview, 33–35

resistors in, 51–53, 61–62

parallel parking resistors, 311–313

parallel resistors, 60

part numbers, on schematics, 228

Parts Express (Web site), 365

parts list

batteries, 173–176

buzzers, 188

connectors, 172–173

DC motors, 189–190

sensors, 181–185

solar cells, 177

speakers, 186–187

switches, 179–181

wall power, 177–178

wire, 170–172

passive components, 32

passive infrared (PIR) motion detector, 184

path, energy, 16

peak current, 25, 124

peak inverse voltage (PIV), 118

peak reverse voltage (PRV), 118–120

peak-to-peak voltage, 25

pencil eraser, 202

perf board, 247, 254–255

permanent circuits, 252–257

Phillips head screwdriver, 200, 380

Philmore-DataK (Web site), 372

phosphors, in television, 18, 38

photodiodes, 138, 177, 182, 230, 234

photographic bulb brush, 202

photoresistor, 182, 229, 233

phototransistor, 230, 234, 297–298

phototranslator, 182

photovoltaic cell. *See* solar cell

piezoelectric effect

buzzer project, 188

in crystal microphone, 183

crystals for, 106

defined, 106, 381

neon light project, 334–336

on schematics, 234

pin headers, 172

pinouts, integrated circuit

correct connections for, 237

disable, 165

explanation of, 154–156

leads in, 148, 153

PIR (passive infrared) motion detector, 184

PIV (peak inverse voltage), 118

pixels (picture elements), 37, 147

plasma screen, for television, 37

plates, capacitor, 68

plugs, cable, 172, 234–235

plus sign, for anode, 24

pn-junction, of semiconductors,

115–116, 381

PNP transistors, 127, 230, 276

polarity

of capacitors, 75–76, 229, 231, 274

on schematics, 43, 224–225

of speakers, 187

polyester dielectric material, 73–74

polypropylene dielectric material, 73–74

polystyrene dielectric material, 73–74

position sensors, 185

positive current, waveform of, 25

- positive temperature coefficient (PTC)  
 thermistor, 183, 381
- potential difference, 13, 29
- potential drop, 13, 29
- potentiometer (pot)  
 for blinky light project, 331  
 in circuit builder starter kit, 207  
 for circuit projects, 304  
 defined, 32, 381  
 encasing, 204  
 multimeter to test, 273–274  
 operation of, 46–47  
 on schematics, 229  
 for timers, 87
- power  
 battery size for, 23  
 calculation of, 16  
 defined, 16, 381  
 isolating circuits from, 108  
 Joule's Law of, 63  
 maximum dissipation of, 139  
 on schematics, 220, 223–227
- power converters, 26
- power plant, 24, 94
- power rating  
 of components, 31  
 of resistors, 48–49  
 of speakers, 187  
 of Zener diode, 122
- power supply, 213, 354–355
- power transistor, 140
- power transmission network, 91
- precision resistors, 43, 46, 381
- precision screwdrivers, 200
- preset pots, 47
- Press-n-Peel (Web site), 372
- pressure sensors, 185
- primary coil, 107–108
- printed circuit boards (PCBs)  
 capacitors on, 74  
 custom, 257  
 Internet resources for, 372  
 resistors on, 48  
 solderless breadboard compared to, 206  
 through-hole mounted DIPs for, 153
- protons in atoms, 11, 381
- prototyping, 254–255
- prototyping board, 240, 381. *See also*  
 solderless breadboard
- PRV (peak reverse voltage), 118–120
- PRV rating of diodes, 119
- PTC (positive temperature coefficient)  
 thermistor, 183, 381
- $P_{\text{total}}$  symbol (maximum power  
 dissipation), 139
- P-type semiconductors, 114–116, 381
- Pulsar Professional fx (Web site), 372
- pulse current, 124
- pulse-width modulation, 190
- pulsing  
 defined, 282, 381  
 digital circuits tested by, 357–358  
 logic probe to detect, 282–283  
 oscilloscope to detect, 286, 290, 293, 298  
 timing of, 330
- pushbutton switch, 179
- push-to-break switch, 179
- **Q** •
- quad 2-input AND gate, 149
- quad 2-input NAND gate, 164, 167
- quarks, in atoms, 11
- quartz crystals, 106
- **R** •
- R symbol (resistance), 40, 381. *See also*  
 resistance
- radial leads, in capacitors, 74
- radio-frequency (RF) circuits, 355, 357
- radio-receiver systems  
 capacitors in tuning circuits of, 71  
 electronics in, 35–37  
 inductors for, 104–106

- radio-receiver systems (*continued*)
  - oscilloscope to test, 296–297
  - RF (radio-frequency) circuits, 355, 357
- RadioShack (Web site), 366
- rail, 220, 245
- RC circuits
  - impedance in, 103
  - operation of, 84–85
  - RC time constant for, 86, 90, 315–316, 381
  - timers created with, 86–87
- RC filters, capacitors in, 87–90
- ready-made electronics kits, 354
- real current, 26–27, 381
- rechargeable batteries, 176
- recombining electrons, 131
- rectification (AC to DC conversion), 112, 121–122
- rectifier diodes, 121
- reference direction of current, 27
- reference ground, 29
- reference ID, on schematics, 228–229
- register circuits, 152
- regulated power supplies, 26
- relay, 180, 233, 382
- remote-control devices, 18, 337
- resist pattern, on printed circuit boards, 257
- resistance
  - capacitive reactance compared to, 81
  - in combination circuits, 34–35
  - current flow restricted by, 31–32
  - defined, 39, 382
  - factors in, 40–41
  - fixed resistors for, 43–46
  - in impedance, 103
  - infinite, 82
  - Joule’s Law in, 63–64
  - multimeter to measure, 272–278
  - Ohm’s Law of
    - circuit analysis by, 56–62
    - circuit design and alteration by, 62–63
    - overview, 54–56
    - purposes of, 41–43
  - R symbol for, 40, 381
  - resistor circuits for, 64
  - resistor combinations for, 49–53
  - resistor power ratings for, 48–49
  - of speakers, 187
  - testing unpowered circuits for, 262
  - in thermistors, 183
  - variable resistors for, 43, 46–48. *See also* potentiometer (pot)
- resistivity of conductors, 40
- resistor tolerance, 43
- resistors
  - capacitors with, 83–87
  - for circuit projects, 304
  - circuits for, 64
  - combinations of, 49–53
  - defined, 39, 382
  - fixed, 207
  - human body as, 210
  - inductors compared to, 101
  - inductors with, 91
  - to limit current through LED, 330
  - multimeter to test, 272–273
  - parallel parking, 311–313
  - power ratings for, 48–49
  - in transistors, 133
- resolution of oscilloscope, 288–289
- resonance, 104–106, 357
- reverse current, 118
- reverse voltage, 117
- reverse-bias diodes, 117, 120–121, 131
- reverse-bias voltage, 319
- reversing switch, 181
- RF (radio-frequency) circuits, 355, 357
- rheostat, 43, 47. *See also* potentiometer (pot)
- ribbon cable, 172
- RL circuits
  - impedance in, 103
  - inductors in, 101–102
  - RL time constants for, 102
- RLC circuits, 104–106

rms (root-mean-square) voltage, 25  
 Robsonco Co. (Web site), 342  
 rocker switch, 179  
 RoHS (European Union Restriction on Hazardous Substances) regulations, 367  
 root-mean-square (rms) voltage, 25  
 rosin core of solder, 60/40, 196, 382  
 rosin flux remover, 197, 382  
 rotary resistance tracks, 47  
 Ryerson wire wrapping (Web site), 256

## ● S ●

### safety

of adhesives, 203  
 checklist for, 218  
 of circuit builder starter kit, 207–208  
 of cloths and cleansers, 200–202  
 electricity dangers, 210–214  
 of hand tools, 199–200  
 of household electronics, 48  
 importance of, 3–4  
 of lubricants, 202–203  
 of multimeter, 198–199  
 of soldering equipment, 196–198  
 soldering process, 214–215, 252  
 of solderless breadboard, 205–206  
 static electricity, 215–217  
 of supplies, 204  
 in workshop placement, 194–195  
 safety glasses, 204, 218, 248  
 saturating transistors, 132–133, 136  
 schematics  
 alternative drawing styles for, 238  
 analog electronic components on, 228–230  
 connections on, 235  
 defined, 219, 382  
 digital logic components on, 231–232  
 example of, 236–237  
 fixed resistors on, 43  
 integrated circuits on, 155, 231–232

for light bulb circuit, 27–29  
 overview, 219–222  
 power sources on, 223–227  
 resistor tolerance on, 46  
 switches and relays on, 233  
 transducers on, 233–234  
 screwdrivers, 200  
 second value band on resistors, 45  
 secondary coil, 107–108  
 secondary energy sources, 24  
 self-contained power supply, 213  
 self-inductance, 95, 107  
 semiconductor temperature sensors, 185, 382  
 semiconductors  
 as active components, 32  
 circuits with, 141  
 combining N- and P-types, 114–116  
 as conductors and insulators, 112–116  
 defined, 26, 382  
 as diodes in circuits, 120–125  
 doping, 113–114  
 for integrated circuits (ICs), 144  
 junction diode with, 116–120  
 rheostats replaced by, 47  
 for solar cells, 26  
 in transistors  
 amplifying signals with, 135–137  
 bipolar junction, 126–127  
 field-effect, 127  
 identifying, 139–141  
 model of, 133–135  
 operations of, 128–133  
 ratings for, 138–139  
 switching signals with, 137–138  
 sensors  
 defined, 18, 382  
 description, 18  
 traffic-light, 99  
 types of, 181–185  
 series connection  
 capacitors in, 71, 80–81  
 circuit project on, 306–309

- series connection (*continued*)
  - defined, 33, 382
  - for multimeter, 269–271
  - overview, 33–35
  - resistors in, 50–51, 53
- shielded inductor, 100–101
- shielded jack, 235
- shielded wire, 172
- shock, electrical, 210
- short circuits
  - defined, 96, 382
  - inductors in, 96–97
  - ohmmeter to test for, 276–277
- signal
  - amplified by transistors, 135–137
  - clock, 152
  - function generator for, 356
  - oscilloscope display of, 293–295
  - switched by transistors, 137–138
- signal diode, 121
- signal ground, 223, 226
- signal transistors, 140
- silver solder, 215
- silver third value band on resistors, 45
- Simpson Model 260 multimeter, 199
- sine wave, 25, 286, 382
- single ground symbol, 226
- single point in circuit, 29
- single-pole double-throw (SPDT) switch,
  - 181, 233, 277, 382
- single-pole single-throw (SPST) switch, 181,
  - 233, 277, 336, 382
- single-pole switch, 180, 382
- single-throw switch, 180
- sink current, 156
- siren project, 338–340
- 60/40 rosin core, of solder, 196, 382
- Skycraft Parts & Surplus (Web site), 373
- slide pots, 47
- slide switch, 179, 382
- small-outline integrated circuit (SOIC), 153
- smoothing capacitors, 71
- SMT (surface-mount technology), 48, 153
- SMT resistors, 48
- sockets, 153, 172, 255
- SOIC (small-outline integrated circuit), 153
- solar cell
  - defined, 26, 383
  - overview, 26
  - in parts list, 177
  - on schematics, 223–224
- solar panels, 177
- Solar Power Your Home For Dummies* (DeGunther), 26
- solder, 196–197, 383
- solder breadboard, 247, 253–254, 383
- solder sucker, 197, 251
- solder wick or braid, 197, 251, 383
- soldering
  - defined, 196, 383
  - process, 247–252
  - safety in, 214–215
  - solder for, 383
  - solder removal tools for, 197
- soldering iron, 196
- soldering irons, 3, 196, 383
- soldering joint, 196
- soldering pencil, 196
- soldering stand, 196
- soldering station, 196
- soldering tips, 197
- solderless breadboard
  - for circuit projects, 304–305
  - damage avoiding, 246–247
  - defined, 153, 383
  - jumper wires for, 208
  - laying out circuits on, 244–246
  - overview, 205–206
  - parts and tools for, 243
  - pre-stripped wire for, 243–244
  - project ideas for, 328
  - using, 240–243
- solenoids, 95. *See also* inductors
- solid wire, 170, 243, 383
- solid-core transformer, 230
- solid-state electronics, 116

- source, in field-effect transistors, 127
- source current, 156
- source of electrical energy, 16, 22, 24. *See also* batteries; current; solar cell
- SPDT (single-pole double-throw) switch, 181, 233, 277, 382
- speakers
- in circuit builder starter kit, 208
  - in parts list, 186–187
  - for radio-receiver system, 36
  - on schematics, 234
- specifications, for integrated circuits (ICs), 152
- speed, of DC motors, 190
- SPICE (Simulation Program with Integrated Circuit Emphasis) algorithm, 359
- spike, voltage, 289, 385
- “split” DC power, 224
- sponge, wet, to remove solder, 197
- SPST (single-pole single-throw) switch, 181, 233, 277, 382
- square wave, 293, 297, 383
- standard-precision resistors, 43, 45
- static electricity
- avoiding, 215–217
  - CMOS chip sensitivity to, 164
  - defined, 14, 383
  - description, 14
  - dissipation of, 154
  - soldering generating, 253
- stepped up/stepped down power, 25, 225
- step-up/step-down transformers, 32, 109
- stocking distributors, 364
- straight-head screwdriver, 200
- strain relief, 213, 383
- stranded wire, 170, 243–244, 384
- stray capacitance, 247, 384
- strength of current, from solar cells, 26
- super glue, 203
- superconductors, 40
- supply current, 312
- surface-mount technology (SMT), 48, 153
- surplus merchandise, 363, 367, 372
- surveillance, infrared detector for, 337–338
- sweep generator, 357, 384
- switches
- to amplify current, 322–323
  - in circuit builder starter kit, 208
  - infrared detector, 336
  - leads for, 28
  - multimeter to test, 277–278
  - on schematics, 233
  - testing resistance of, 262
  - types of, 179–181
- synthetic grease, 203

## ● T ●

- T symbol (time period), 159
- tantalum capacitor, 331
- tantalum electrolytic dielectric material, 73–74
- television, 18, 37–38
- temperature, resistance strength by, 40
- temperature sensors, 183–185
- terminal, 22, 47, 172, 384
- terminal block, 172
- Texas Instruments, Inc., 144
- thermistor
- defined, 40, 384
  - purpose of, 183–184
  - resistance behavior in, 40
  - on schematics, 233
- thermocouple, 185, 384
- third hand clamp, 200, 249, 384
- third value band on resistors, 45
- through-hole mounted DIPs, 153
- tie post, 255
- time period (T), 159
- time slice, on oscilloscopes, 293
- timer
- for blinking light project, 328
  - capacitors for, 71
  - 555, 159–164
  - for light bulb circuits, 10
  - RC circuits for, 86–87

- tinning solder tips, 248, 384
  - tip cleaner paste, to remove solder, 197
  - toggle switch, 179
  - tolerance
    - of capacitors, 77–78
    - defined, 44, 384
    - of resistors, 44–45
  - tone generator, 340
  - total capacitance, 80
  - trace
    - defined, 257, 384
    - oscilloscope, 285
    - in printed circuit boards, 257, 262
  - transducer, 181, 186, 233–234
  - transformer
    - air-core, 229
    - solid-core, 230
    - to store electrical energy, 32
    - unshielded inductors for, 91, 107–109
    - wall, 178, 213
  - transformer action, 107
  - transistor action, 133
  - transistor battery, 174
  - transistors
    - amplifying signals with, 135–137
    - bipolar junction, 126–127, 182
    - in circuit builder starter kit, 207
    - for circuit projects, 304, 321–323
    - defined, 32, 384
    - electrostatic discharge (ESD) sensitivity
      - of, 216
    - field-effect
      - CMOS technology for, 164
      - dual-gate, 140
      - electrostatic discharge (ESD) sensitivity
        - of, 216
      - in integrated circuits, 127
      - on schematics, 230
    - identifying, 139–141
    - model of, 133–135
    - multimeter to test, 275–276, 278
    - operations of, 128–133
    - overview, 32
    - ratings for, 138–139
    - resistors to limit current to, 41
    - switching signals with, 137–138
  - transistor-transistor logic (TTL), 164
  - trim pots, 47
  - troubleshooting
    - live circuits, 213
    - logic analyzer for, 359
    - logic pulser for, 357
    - oscilloscopes for, 288–289
  - truth tables, 150–151
  - TTL (transistor-transistor logic), 164
  - tuner, for radio-receiver system, 36
  - tuning circuits
    - inductors in, 99–102
    - overview, 71
    - resonance in, 105
  - turbines, in power plant, 24
  - two-state representation, in binary
    - system, 147
- 
- U •
  - unbiased diodes, 118
  - uninterruptible power supplies
    - (UPSs), 70, 125
  - United Kingdom, schematic
    - symbols in, 238
  - universal gates, 149
  - universal solder board, 253–254
  - University of Cambridge, 369
  - unloaded pulses, 358
  - unpolarized capacitors, 331
  - unpowered circuits, for testing, 262
  - UPSs (uninterruptible power
    - supplies), 70, 125
- 
- V •
  - V symbol (volts), 13
  - valence electrons, 112–113
  - varactors, 78
  - variable capacitor, 229

- variable capacitors, 78–79, 384
  - variable coil, 100, 384. *See also* inductors
  - variable inductors, 100
  - variable power supply, 354–355
  - variable resistors. *See also* potentiometer (pot)
    - defined, 43, 384
    - description of, 43
    - operation of, 46–48
    - on schematics, 229
  - varicaps, 78
  - $V_{CE}$  symbol (maximum collector-to-emitter voltage), 139, 384
  - visible light-emitting diodes (visible LEDs), 123
  - voltage
    - AC source symbol for, 25
    - across quartz crystals, 106
    - back, 95
    - base-emitter junction control of, 131
    - batteries for, 28–29
    - battery terminals for, 22
    - bias, 117–118
    - breakdown, 115
    - of buzzer, 188
    - calculating, 62
    - capacitor, 68–69, 71
    - clipping, 319–320
    - of DC motors, 190
    - defined, 13, 384
    - fluctuating, 25
    - as force, 13–14, 16
    - forward, 117, 124
    - frequency of, 81, 99
    - magnetism to induce, 94
    - maximum collector-to-emitter, 139
    - multimeter to measure, 269–270
    - Ohm's Law for, 54–56, 58–61
    - oscilloscope to test, 285–288, 290
    - overvoltage protection, diodes for, 125
    - in parallel circuits, 34
    - peak reverse, 118–120
    - resistors to control, 42–43
    - reverse, 117
    - rheostat handling of, 47
    - as safety concern, 3
    - on schematics, 224
    - spike in, 289, 385
    - warnings of, 211
    - working, 68, 73
    - Zener diode to regulate, 122–123
  - voltage across the bulb, 30
  - voltage divider
    - circuit as, 58
    - defined, 42, 385
    - project on, 309–311
    - resistance as, 42
  - voltage drop
    - as alternative term, 13
    - calculating, 62
    - circuit project on, 317–320
    - defined, 13, 385
    - explanation of, 29
  - voltage gain, 136–137
  - voltage potential, 13
  - voltage rise, 29
  - voltmeter, 30, 235, 260–261
  - volts (V), 13
  - volume control, potentiometer for, 43
- *W* ●
- wall power (use not recommended), 177–178
  - wall transformer, 213
  - “wall warts,” 178
  - warranty, manufacturer's, 363
  - water tester project, 346–347
  - water-based household cleaner, 202
  - watt hour, as power measure, 31, 48, 385
  - waveform
    - of alternating current, 25
    - audio, 296
    - defined, 25, 385
    - on oscilloscope, 285–287, 289
    - on schematics, 225

Web resources. *See also various distributors' Web sites*

for calculators, 370

for circuits, 370–371

discussion forums, 371–372

for printed circuit boards, 372

for surplus merchandise, 372

tutorials, 369–370

wetted sponge, to remove solder, 197

white household glue, 203

Williamson Labs Electronics Tutorial

(Web site), 370

windmills, 24

wiper, on multimeter, 273

wire

in circuit builder starter kit, 208

for circuits, 15

defined, 385

gauge of, 171, 378, 385

jumper, 243

multimeter to test, 276–277

pre-stripped, 243–244

securing, 213

strain relief, 213, 383

types of, 170–172

wrapping of, 171, 255–256, 385

wire cutter, 199

wire stripper, 200, 244

work, electrical energy for, 14–17

working voltage, 68, 73

workshop, placement of, 194–195

wrapping, wire, 171, 255–256, 385



$X_c$  symbol (capacitive reactance), 82

$X_L$  symbol (inductive reactance), 98

XNOR gate, 148, 150, 231

XOR gate, 148, 150, 231



Z symbol (impedance), 103

Zener diode

breakdown voltage for, 115

reverse biasing, 118

reverse-bias voltage applied to, 319–320

on schematics, 230

in semiconductor circuits, 141

voltage regulated with, 122–123

zinc-carbon batteries, 175, 385