

Contents

Preface	xi
1 Introduction	1
1.1 The Conventional Power Grid	1
1.1.1 Power Transfer Mechanism	1
1.2 Towards a More Flexible Power Grid	5
1.2.1 Power Electronics Control	5
1.3 HVDC Transmission	8
1.3.1 Thyristor-Based CSC Transmission	10
1.3.2 VSC Transmission Based on the Integrated Gate Bipolar Transistor (IGBT)	11
1.3.3 Multi-terminal HVDC	12
1.3.4 The Flexibility Concept Applied to HVDC	13
1.4 Relative Power Carrying Capability of AC and DC Transmission Lines	13
1.5 The Impact of Distributed Generation	16
1.6 The Effect of Electricity Deregulation	16
1.7 Discussion	18
References	19
2 Semiconductor Power Devices	21
2.1 Introduction	21
2.2 Semiconductor Principles	21
2.3 Power Semiconductor Elements	22
2.3.1 The pn Rectifier	22
2.3.2 The Transistor	25
2.3.3 Metal-Oxide-Semiconductor Field-Effect Transistor	25
2.4 Dynamic Stresses on Power Switches	27
2.4.1 Rate of Change of Voltage (dv/dt)	27
2.4.2 Rate of Change of Current (di/dt)	28
2.4.3 Balancing Problems in Series Chains	28

2.5	Other Switching Issues	29
2.5.1	Switching Frequency	29
2.5.2	Switching Losses	29
2.5.3	Soft Switching	29
2.5.4	Use of Snubbers	30
2.6	Thyristor-Type Power Switches	31
2.6.1	The Thyristor	31
2.6.2	Gate Turn-Off Thyristor	36
2.6.3	Insulated Gate-Commutated Thyristor	41
2.6.4	MOS Turn-Off Thyristor	42
2.6.5	MOS Controlled Thyristor	44
2.6.6	Emitter Turn-Off Thyristor	45
2.7	Insulated Gate Bipolar Transistor	47
2.7.1	IGBT (Series) Chains	49
2.8	Diodes	51
2.9	Prognostic Assessment	53
2.9.1	Ratings and Applicability	53
2.9.2	Relative Losses	55
	References	56
3	Line-Commutated HVDC Conversion	57
3.1	Introduction	57
3.2	Three-Phase AC–DC Conversion	57
3.2.1	Basic CSC Operating Principles	58
3.2.2	Effect of Delaying the Firing Instant	58
3.3	The Commutation Process	62
3.3.1	Analysis of the Commutation Circuit	62
3.4	Rectifier Operation	64
3.5	Inverter Operation	67
3.6	Power Factor and Reactive Power	69
3.7	Characteristic Harmonics	71
3.7.1	DC Side Harmonics	72
3.7.2	AC Side Harmonics	73
3.8	Multi-Pulse Conversion	74
3.8.1	Transformer Phase Shifting	74
3.8.2	DC Ripple Reinjection	77
3.9	Uncharacteristic Harmonics and Interharmonics	81
3.9.1	Imperfect AC Source	83
3.9.2	DC Modulation	87
3.9.3	Control System Imperfections	88
3.9.4	Firing Asymmetry	88
3.9.5	Magnification of Low-Order Harmonics	89
3.10	Harmonic Reduction by Filters	90
3.10.1	AC Side Filters	90
3.10.2	DC Side Filters	92

3.11	Frequency Cross-Modulation Across the LCC	93
3.12	Summary	94
	References	94
4	Self-Commutating Conversion	97
4.1	Introduction	97
4.2	Voltage Source Conversion	97
4.2.1	VSC Operating Principles	97
4.2.2	Converter Components	102
4.2.3	The Three-Phase VSC	105
4.3	Comparison of LCC and VSC	114
4.4	Current Source Conversion	114
4.4.1	Analysis of the CSC Waveforms	116
4.5	The Reinjection Concept with Self-Commutation	116
4.5.1	Application to VSC	116
4.5.2	Application to CSC	121
4.6	Discussion	124
	References	125
5	Pulse Width Modulation	127
5.1	Introduction	127
5.2	PWM Operating Principles	127
5.3	Selective Harmonic Cancellation	128
5.4	Sinusoidal (Carrier-Based) PWM	131
5.5	PWM Carrier-Based Implementation	133
5.5.1	Naturally Sampled PWM	134
5.5.2	Uniformly Sampled	136
5.6	Modulation in Multi-Bridge Converters	137
5.7	Summary	138
	References	140
6	Multi-Level Conversion	141
6.1	Introduction	141
6.2	Diode Clamping	142
6.2.1	Three-Level Neutral Point Clamped VSC	142
6.2.2	Five-Level Diode-Clamped VSC	145
6.2.3	Diode Clamping Generalisation	149
6.3	Flying Capacitor Configuration	154
6.3.1	Three-Level Flying Capacitor	154
6.3.2	Multi-Level Flying Capacitor	155
6.4	Cascaded H-Bridge Configuration	158
6.5	Combined PWM/Multi-Level Conversion	161
6.6	Relative Merits of the Multi-Level Alternatives	164
6.6.1	A Cost Comparison of Alternative Configurations for Use in HVDC	165
	References	167

7	Multi-Level DC Reinjection	169
7.1	Introduction	169
7.2	Soft Switching in Multi-Level Reinjection Converters	170
7.3	Clamp-Controlled MLVR	170
7.3.1	Firing Coordination	174
7.3.2	Analysis of the Voltage Waveforms	174
7.3.3	Analysis of the Output Current	178
7.3.4	Capacitor Voltage Balancing	179
7.3.5	Dynamic Performance	185
7.4	Transformer-Coupled MLVR	187
7.5	Cascaded H-Bridge MLVR	193
7.5.1	Basic Structure and Waveforms	193
7.5.2	Switching Pattern of the Reinjection Bridges	196
7.5.3	Design of the Cascaded H-Bridge Chain	197
7.5.4	Capacitors' Balancing	199
7.5.5	STATCOM Application	204
7.6	Summary of Main Characteristics of MLVR Alternatives	209
7.7	Multi-Level Current Reinjection (MLCR)	210
7.7.1	Structure and Operating Principles	210
7.7.2	Self-Commutating Thyristor Conversion	213
7.7.3	EMTDC Verification	216
7.8	MLCR-CSC Versus MLVR-VSC	221
	References	222
8	Line-Commutated CSC Transmission	225
8.1	Introduction	225
8.2	The Line-Commutated HVDC Converter	226
8.3	HVDC Converter Disturbances	232
8.4	Structure of the HVDC Link	233
8.5	DC System Configurations	239
8.6	DC System Control and Operation	242
8.6.1	General Philosophy	242
8.6.2	Different Control Levels	243
8.6.3	Overall Control Coordination	243
8.6.4	Pole Controls	245
8.6.5	Converter Unit Controls	253
8.7	AC–DC System Interaction	257
8.7.1	Voltage Interaction	257
8.7.2	Dynamic Voltage Regulation	258
8.7.3	Dynamic Stabilisation of AC Systems	259
8.7.4	Controlled Damping of DC-Interconnected Systems	260
8.7.5	Damping of Sub-Synchronous Resonances	260
8.7.6	Active and Reactive Power Coordination	261
8.7.7	Transient Stabilisation of AC Systems	261
8.8	AC–DC–AC Frequency Interactions	262
8.8.1	Harmonic Cross-Modulation Across the DC Link	262
8.8.2	Complementary and Composite Resonances	265

8.9	DC Link Response to External Disturbances	266
8.9.1	Response to AC System Faults	266
8.9.2	Response to DC Line Faults	267
8.10	Reliability of LCC Transmission	267
8.11	Concluding Statements	273
	References	273
9	Developments in Line-Commutated HVDC Schemes	275
9.1	Introduction	275
9.2	Capacitor Commutated Conversion	276
9.2.1	Basic CCC Operation	277
9.2.2	Simulated Performance	277
9.3	Continuously Tuned AC Filters	280
9.4	Active DC Side Filters	281
9.5	STATCOM-Aided DC Transmission	282
9.6	AC Transmission Lines Converted for Use with HVDC	286
9.6.1	Modulated (Tripole) DC Transmission	287
9.7	HVDC Transmission at Voltages above 600 kV	288
9.8	Concluding Statements	289
	References	289
10	VSC Transmission	291
10.1	Introduction	291
10.2	Power Transfer Characteristics	292
10.2.1	Current Relationships	294
10.3	Structure of the VSC Link	296
10.3.1	VSC-HVDC Cable Technology	297
10.4	VSC DC System Control	299
10.4.1	General Philosophy	299
10.4.2	Different Control Levels	302
10.4.3	DC Link Control Coordination	303
10.4.4	Control Capability of VSC Transmission	304
10.4.5	Assistance During Grid Restoration	305
10.5	HVDC Light Technology	306
10.5.1	Two-Level PWM Schemes	308
10.5.2	Three-Level PWM Schemes	312
10.5.3	HVDC Light Performance	314
10.6	Other VSC Projects	321
10.7	Potential for Multi-Terminal Sub-Transmission Systems	323
10.8	Discussion	324
	References	326
11	Multi-Level VSC and CSC Transmission	327
11.1	Introduction	327
11.2	Multi-Level VSC Transmission	328
11.2.1	Power Flow Considerations	328
11.2.2	DC Link Control Characteristics	331

11.2.3	Test System and Simulation Results	332
11.2.4	Provision of Independent Reactive Power Control	337
11.3	Multi-Level CSC Transmission	341
11.3.1	Dynamic Model	343
11.3.2	Control Structure	344
11.3.3	Simulated Performance under Normal Operating Conditions	345
11.3.4	Simulated Performance Following Disturbances	348
11.3.5	Reactive Power Control in Multi-Level CSC Transmission	352
11.4	Summary	356
	References	357
	Index	359