

# CONTENTS

<b>Foreword</b>	<b>xiii</b>
<b>Preface</b>	<b>xv</b>
<b>PART I MICROWAVE FILTER FUNDAMENTALS</b>	<b>1</b>
<b>1 Scattering Parameters and <i>ABCD</i> Matrices</b>	<b>3</b>
1.1 Introduction, 3	
1.2 Scattering Matrix of a Two-Port System, 4	
1.2.1 Definitions, 4	
1.2.2 Computing the <i>S</i> Parameters, 6	
1.2.3 <i>S</i> -Parameter Properties, 10	
1.3 <i>ABCD</i> Matrix of a Two-Port System, 10	
1.3.1 <i>ABCD</i> Matrix of Basic Elements, 11	
1.3.2 Cascade and Multiplication Property, 12	
1.3.3 Input Impedance of a Loaded Two-Port, 14	
1.3.4 Impedance and Admittance Inverters, 14	
1.3.5 <i>ABCD</i> -Parameter Properties, 17	
1.4 Conversion from Formulation <i>S</i> to <i>ABCD</i> and <i>ABCD</i> to <i>S</i> , 18	
1.5 Bisection Theorem for Symmetrical Networks, 18	
1.6 Conclusions, 21	
References, 21	
<b>2 Approximations and Synthesis</b>	<b>23</b>
2.1 Introduction, 23	
2.2 Ideal Low-Pass Filtering Characteristics, 24	

2.3	Functions Approximating the Ideal Low-Pass Magnitude Response, 25	
2.3.1	Butterworth Function, 25	
2.3.2	Chebyshev Function, 26	
2.3.3	Elliptic Function, 27	
2.3.4	Generalized Chebyshev (Pseudoelliptic) Function, 29	
2.4	Functions Approximating the Ideal Low-Pass Phase Response, 30	
2.4.1	Bessel Function, 30	
2.4.2	Rhodes Equidistant Linear-Phase Function, 31	
2.5	Low-Pass Lumped Ladder Prototypes, 32	
2.5.1	General Synthesis Technique, 32	
2.5.2	Normalized Low-Pass Ladders, 36	
2.6	Impedance and Frequency Scaling, 39	
2.6.1	Impedance Scaling, 39	
2.6.2	Frequency Scaling, 40	
2.7	<i>LC</i> Filter Example, 41	
2.8	Impedance and Admittance Inverter Ladders, 41	
2.8.1	Low-Pass Prototypes, 41	
2.8.2	Scaling Flexibility, 42	
2.8.3	Bandpass Ladders, 44	
2.8.4	Filter Examples, 45	
2.9	Conclusions, 46	
	References, 46	
<b>3</b>	<b>Waveguides and Transmission Lines</b>	<b>49</b>
3.1	Introduction, 49	
3.2	Rectangular Waveguides and Cavities, 49	
3.2.1	Rectangular Waveguides, 49	
3.2.2	Rectangular Cavities, 52	
3.3	Circular Waveguides and Cavities, 53	
3.3.1	Circular Waveguides, 53	
3.3.2	Cylindrical Cavities, 55	
3.4	Evanescence Modes, 56	
3.5	Planar Transmission Lines, 57	
3.6	Distributed Circuits, 60	
3.7	Conclusions, 63	
	References, 64	
<b>4</b>	<b>Categorization of Microwave Filters</b>	<b>67</b>
4.1	Introduction, 67	
4.2	Minimum-Phase Microwave Filters, 68	
4.2.1	General Design Steps, 68	

4.2.2	Minimum-Phase Filter Examples, 70	
4.3	Non-Minimum-Phase Symmetrical Response Microwave Filters, 70	
4.3.1	General Design Steps, 71	
4.3.2	Non-Minimum-Phase Symmetrical Response Filter Examples, 73	
4.3.3	Microwave Linear-Phase Filters, 73	
4.4	Non-Minimum-Phase Asymmetrical Response Microwave Filters, 74	
4.4.1	General Design Steps, 74	
4.4.2	Non-Minimum-Phase Asymmetrical Response Filter Examples, 77	
4.4.3	Multimode Microwave Filters by Optimization, 79	
4.5	Conclusions, 79	
	References, 80	
 <b>PART II MINIMUM-PHASE FILTERS</b>		<b>83</b>
<b>5</b>	<b>Capacitive-Gap Filters for Millimeter Waves</b>	<b>85</b>
5.1	Introduction, 85	
5.2	Capacitive-Gap Filters, 86	
5.2.1	Capacitive-Gap Filter Structure, 86	
5.2.2	Design Procedures, 87	
5.2.3	Step-by-Step Design Example, 91	
5.2.4	Filter Realizations, 93	
5.3	Extension to Millimeter Waves, 95	
5.3.1	Millimeter-Wave Technology, 95	
5.3.2	Fifth-Order Chebyshev Capacitive-Gap Filter at 35 GHz, 96	
5.4	Electromagnetic Characterization of SSS, 99	
5.5	Conclusions, 102	
	References, 102	
<b>6</b>	<b>Evanescent-Mode Waveguide Filters with Dielectric Inserts</b>	<b>105</b>
6.1	Introduction, 105	
6.2	Evanescent-Mode Waveguide Filters, 106	
6.2.1	Scattering and <i>ABCD</i> Descriptions of the Structure, 108	
6.2.2	Equivalent Circuit of the Structure, 110	
6.2.3	Filter Design Procedure, 115	
6.2.4	Design Examples and Realizations, 117	
6.3	Folded Evanescent-Mode Waveguide Filters, 121	
6.3.1	Scattering and <i>ABCD</i> Descriptions of the Additional Elements, 123	

6.3.2	Filter Design Procedure, 125	
6.3.3	Design Examples and Realizations, 125	
6.4	Conclusions, 127	
	References, 128	
<b>7</b>	<b>Interdigital Filters</b>	<b>131</b>
7.1	Introduction, 131	
7.2	Interdigital Filters, 131	
7.3	Design Method, 135	
7.3.1	Prototype Circuit, 135	
7.3.2	Equivalent Circuit, 137	
7.3.3	Input and Output, 140	
7.3.4	Case of Narrowband Filters, 141	
7.3.5	Frequency Transformation, 141	
7.3.6	Physical Parameters of the Interdigital Filter, 142	
7.4	Design Examples, 145	
7.4.1	Wideband Example, 145	
7.4.2	Narrowband Example, 147	
7.5	Realizations and Measured Performance, 148	
7.6	Conclusions, 150	
	References, 151	
<b>8</b>	<b>Comblin Filters Implemented in SSS</b>	<b>153</b>
8.1	Introduction, 153	
8.2	Comblin Filters, 153	
8.3	Design Method, 156	
8.3.1	Prototype Circuit, 156	
8.3.2	Equivalent Circuit, 157	
8.3.3	Input and Output, 159	
8.3.4	Feasibility, 162	
8.3.5	Physical Parameters of the Comblin Structure, 162	
8.4	Design Example, 165	
8.5	Realizations and Measured Performance, 168	
8.6	Conclusions, 169	
	References, 170	
<b>PART III</b>	<b>NON-MINIMUM-PHASE SYMMETRICAL RESPONSE FILTERS</b>	<b>171</b>
<b>9</b>	<b>Generalized Interdigital Filters with Conditions on Amplitude and Phase</b>	<b>173</b>
9.1	Introduction, 173	
9.2	Generalized Interdigital Filter, 174	
9.3	Simultaneous Amplitude and Phase Functions, 175	

9.3.1	Minimum-Phase Functions with Linear Phase, 175	
9.3.2	Non-Minimum-Phase Functions with Simultaneous Conditions on the Amplitude and Phase, 177	
9.3.3	Synthesis of Non-Minimum-Phase Functions with Simultaneous Conditions on the Amplitude and Phase, 180	
9.4	Design Method, 182	
9.4.1	Even-Mode Equivalent Circuit, 182	
9.4.2	Frequency Transformation, 186	
9.4.3	Physical Parameters of the Interdigital Structure, 187	
9.5	Design Example, 191	
9.6	Realizations and Measured Performance, 194	
9.7	Conclusions, 195	
	References, 197	
<b>10</b>	<b>Temperature-Stable Narrowband Monomode TE<sub>011</sub> Linear-Phase Filters</b>	<b>199</b>
10.1	Introduction, 199	
10.2	TE <sub>011</sub> Filters, 200	
10.3	Low-Pass Prototype, 200	
10.3.1	Amplitude, 200	
10.3.2	Delay, 201	
10.3.3	Synthesis of the Low-Pass Prototype, 202	
10.4	Design Method, 204	
10.4.1	Matching the Coupling, 204	
10.4.2	Selecting the Cavities, 207	
10.4.3	Defining the Coupling, 208	
10.5	Design Example, 210	
10.6	Realizations and Measured Performance, 213	
10.6.1	Amplitude and Phase Performance, 213	
10.6.2	Temperature Performance, 214	
10.7	Conclusions, 215	
	References, 217	
<b>PART IV</b>	<b>NON-MINIMUM-PHASE ASYMMETRICAL RESPONSE FILTERS</b>	<b>219</b>
<b>11</b>	<b>Asymmetrical Capacitive-Gap Coupled Line Filters</b>	<b>221</b>
11.1	Introduction, 221	
11.2	Capacitive-Gap Coupled Line Filters, 222	
11.3	Synthesis of Low-Pass Asymmetrical Generalized Chebyshev Filters, 222	
11.3.1	In-Line Network, 225	
11.3.2	Analysis of the In-Line Network, 226	

11.3.3	Synthesis of the In-Line Network,	229
11.3.4	Frequency Transformation,	232
11.4	Design Method,	233
11.5	Design Example,	238
11.6	Realization of the CGCL Filter,	243
11.7	Conclusions,	244
	References,	245
<b>12</b>	<b>Asymmetrical Dual-Mode TE<sub>102</sub>/TE<sub>301</sub> Thick Iris Rectangular In-Line Waveguide Filters with Transmission Zeros</b>	<b>247</b>
12.1	Introduction,	247
12.2	TE <sub>102</sub> /TE <sub>301</sub> Filters,	248
12.3	Synthesis of Low-Pass Asymmetrical Generalized Chebyshev Filters,	248
12.3.1	Fundamental Element,	249
12.3.2	Analysis of the In-Line Network,	250
12.3.3	Synthesis by Simple Extraction Techniques,	252
12.3.4	Frequency Transformation,	254
12.4	Design Method,	256
12.4.1	Equivalent Circuit of Monomode and Bimode Cavities,	256
12.4.2	Optimization Approach,	256
12.5	Design Example,	262
12.6	Realizations and Measured Performance,	266
12.6.1	Third-Order Filter with One Transmission Zero,	266
12.6.2	Fourth-Order Filter with Two Transmission Zeros,	268
12.7	Conclusions,	269
	References,	270
<b>13</b>	<b>Asymmetrical Cylindrical Dual-Mode Waveguide Filters with Transmission Zeros</b>	<b>273</b>
13.1	Introduction,	273
13.2	Dual-Mode Cylindrical Waveguide Filters,	274
13.3	Synthesis of Low-Pass Asymmetrical Generalized Chebyshev Filters,	275
13.3.1	Synthesis From a Cross-Coupled Prototype,	275
13.3.2	Extracting the Elements from the Chain Matrix,	277
13.3.3	Coupling Graph and Frequency Transformation,	281
13.4	Design Method,	284
13.4.1	Rotation Matrix,	284
13.4.2	Cruciform Iris,	286
13.4.3	Physical Parameters of the Irises,	290
13.5	Realizations and Measured Performance,	292

13.5.1	Fourth-Order Filter with One Transmission Zero on the Left, 292	
13.5.2	Fourth-Order Filter with Two Transmission Zeros on the Right, 293	
13.5.3	Sixth-Order Filter with One Transmission Zero on the Right, 295	
13.6	Conclusions, 296	
	References, 296	
<b>14</b>	<b>Asymmetrical Multimode Rectangular Building Block Filters Using Genetic Optimization</b>	<b>299</b>
14.1	Introduction, 299	
14.2	Multimode Rectangular Waveguide Filters, 300	
14.3	Optimization-Based Design, 302	
	14.3.1 Genetic Algorithm, 302	
	14.3.2 Example, 308	
14.4	Realizations, 313	
	14.4.1 Fourth-Order Filter with Two Transmission Zeros, 313	
	14.4.2 Seventh-Order Filter with Four Transmission Zeros, 314	
	14.4.3 Extension to a Tenth-Order Filter with Six Transmission Zeros, 318	
14.5	Conclusions, 320	
	References, 320	
	<b>Appendix 1: Lossless Systems</b>	<b>323</b>
	<b>Appendix 2: Redundant Elements</b>	<b>325</b>
	<b>Appendix 3: Modal Analysis of Waveguide Step Discontinuities</b>	<b>328</b>
	<b>Appendix 4: Trisections with Unity Inverters on the Inside or on the Outside</b>	<b>338</b>
	<b>Appendix 5: Reference Fields and Scattering Matrices for Multimodal Rectangular Waveguide Filters</b>	<b>340</b>
	<b>Index</b>	<b>353</b>

