
CONTENTS

| | |
|---|-----------|
| Preface | xv |
| 1 Introduction | 1 |
| 1.1 Microwave Frequencies | 1 |
| 1.2 Microwave Applications | 3 |
| 1.3 Microwave Circuit Elements and Analysis | 6 |
| References | 16 |
| 2 Electromagnetic Theory | 17 |
| 2.1 Maxwell's Equations | 17 |
| 2.2 Constitutive Relations | 23 |
| 2.3 Static Fields | 28 |
| 2.4 Wave Equation | 31 |
| 2.5 Energy and Power | 33 |
| 2.6 Boundary Conditions | 39 |
| 2.7 Plane Waves | 44 |
| Plane Waves in Free Space | 44 |
| 2.8 Reflection from a Dielectric Interface | 49 |
| 1. Parallel Polarization | 49 |
| 2. Perpendicular Polarization | 52 |
| 2.9 Reflection from a Conducting Plane | 53 |
| 2.10 Potential Theory | 56 |
| ★2.11 Derivation of Solution for Vector Potential | 59 |
| 2.12 Lorentz Reciprocity Theorem | 62 |
| Problems | 65 |
| References | 70 |
| 3 Transmission Lines and Waveguides | 71 |
| Part 1 Waves on Transmission Lines | 72 |
| 3.1 Waves on An Ideal Transmission Line | 72 |
| 3.2 Terminated Transmission Line: Resistive Load | 78 |

| | | |
|------|---|-----|
| 3.3 | Capacitive Termination | 82 |
| 3.4 | Steady-State Sinusoidal Waves | 85 |
| 3.5 | Waves on a Lossy Transmission Line | 86 |
| | Loss-Free Transmission Line | 88 |
| | Low-Loss Transmission Line | 89 |
| 3.6 | Terminated Transmission Line: Sinusoidal Waves | 89 |
| | Terminated Lossy Line | 94 |
| | Part 2 Field Analysis of Transmission Lines | 96 |
| 3.7 | Classification of Wave Solutions | 96 |
| | TEM Waves | 99 |
| | TE Waves | 100 |
| | TM Waves | 102 |
| 3.8 | Transmission Lines (Field Analysis) | 104 |
| | Lossless Transmission Line | 104 |
| | Transmission Line with Small Losses | 108 |
| 3.9 | Transmission-Line Parameters | 112 |
| 3.10 | Inhomogeneously Filled Parallel-Plate Transmission Line | 117 |
| | Low-Frequency Solution | 121 |
| | High-Frequency Solution | 123 |
| 3.11 | Planar Transmission Lines | 125 |
| 3.12 | Microstrip Transmission Line | 130 |
| | Low-Frequency Solutions | 136 |
| | Microstrip Attenuation | 153 |
| | High-Frequency Properties of Microstrip Lines | 158 |
| | Attenuation | 163 |
| 3.13 | Coupled Microstrip Lines | 164 |
| 3.14 | Strip Transmission Lines | 170 |
| | Attenuation | 171 |
| 3.15 | Coupled Strip Lines | 173 |
| 3.16 | Coplanar Transmission Lines | 175 |
| | Attenuation | 178 |
| | High-Frequency Dispersion | 180 |
| | Part 3 Rectangular and Circular Waveguides | 180 |
| 3.17 | Rectangular Waveguide | 181 |
| | TE Waves | 182 |
| | Power | 186 |
| | Attenuation | 187 |
| | Dominant TE_{10} Mode | 190 |
| | TM Modes | 193 |
| 3.18 | Circular Waveguides | 194 |
| | TM Modes | 194 |
| | TE Modes | 196 |
| 3.19 | Wave Velocities | 198 |
| | Phase Velocity | 199 |
| | Group Velocity | 200 |
| | Energy-Flow Velocity | 204 |
| 3.20 | Ridge Waveguide | 205 |
| 3.21 | Fin Line | 208 |
| | Problems | 210 |
| | References | 219 |

| | | |
|----------|--|------------|
| 4 | Circuit Theory for Waveguiding Systems | 220 |
| 4.1 | Equivalent Voltages and Currents | 221 |
| 4.2 | Impedance Description of Waveguide Elements and Circuits | 224 |
| | One-Port Circuits | 224 |
| | Lossless One-Port Termination | 228 |
| *4.3 | Foster's Reactance Theorem | 230 |
| *4.4 | Even and Odd Properties of Z_{in} | 232 |
| 4.5 | N -Port Circuits | 233 |
| | Proof of Symmetry for the Impedance Matrix | 235 |
| | Proof of Imaginary Nature of $[Z]$ for a Lossless Junction | 236 |
| | Normalized Impedance and Admittance Matrices | 237 |
| 4.6 | Two-Port Junctions | 238 |
| | Some Equivalent Two-Port Circuits | 245 |
| 4.7 | Scattering-Matrix Formulation | 248 |
| | Symmetry of Scattering Matrix | 250 |
| | Scattering Matrix for a Lossless Junction | 251 |
| 4.8 | Scattering Matrix for a Two-Port Junction | 254 |
| 4.9 | Transmission-Matrix Representation | 257 |
| | Voltage-Current Transmission Matrix | 257 |
| | Wave-Amplitude Transmission Matrix | 259 |
| *4.10 | Signal Flow Graphs | 260 |
| *4.11 | Generalized Scattering Matrix for Power Waves | 268 |
| *4.12 | Excitation of Waveguides | 276 |
| | Probe Coupling in a Rectangular Waveguide | 276 |
| | Radiation from Linear Current Elements | 281 |
| | Radiation from Current Loops | 283 |
| *4.13 | Waveguide Coupling by Apertures | 284 |
| | Aperture in a Transverse Wall | 286 |
| | Aperture in Broad Wall of a Waveguide | 290 |
| | Problems | 294 |
| | References | 302 |
| 5 | Impedance Transformation and Matching | 303 |
| 5.1 | Smith Chart | 304 |
| 5.2 | Impedance Matching with Reactive Elements | 308 |
| | Single-Stub Matching | 309 |
| 5.3 | Double-Stub Matching Network | 312 |
| 5.4 | Triple-Stub Tuner | 317 |
| 5.5 | Impedance Matching with Lumped Elements | 319 |
| | Circuit Q and Bandwidth | 325 |
| 5.6 | Design of Complex Impedance Terminations | 330 |
| 5.7 | Invariant Property of Impedance Mismatch Factor | 334 |
| 5.8 | Waveguide Reactive Elements | 339 |
| | Shunt Inductive Elements | 340 |
| | Shunt Capacitive Elements | 341 |
| | Waveguide Stub Tuners | 342 |

| | | |
|----------|---|------------|
| 5.9 | Quarter-Wave Transformers | 343 |
| 5.10 | Theory of Small Reflections | 347 |
| 5.11 | Approximate Theory for Multisection Quarter-Wave Transformers | 348 |
| 5.12 | Binomial Transformer | 350 |
| 5.13 | Chebyshev Transformer | 352 |
| *5.14 | Chebyshev Transformer (Exact Results) | 356 |
| 5.15 | Filter Design Based on Quarter-Wave-Transformer Prototype Circuit | 360 |
| | Junction Capacitance and Length Compensation | 365 |
| 5.16 | Tapered Transmission Lines | 370 |
| | Exponential Taper | 372 |
| | Taper with Triangular Distribution | 372 |
| *5.17 | Synthesis of Transmission-Line Tapers | 373 |
| *5.18 | Chebyshev Taper | 380 |
| *5.19 | Exact Equation for the Reflection Coefficient | 383 |
| | Problems | 387 |
| | References | 393 |
| 6 | Passive Microwave Devices | 394 |
| 6.1 | Terminations | 394 |
| | Variable Short Circuit | 395 |
| 6.2 | Attenuators | 397 |
| | Electronically Controlled Attenuators | 400 |
| 6.3 | Phase Shifters | 404 |
| | Rotary Phase Shifter | 404 |
| | Electronically Controlled Phase Shifters | 409 |
| 6.4 | Directional Couplers | 413 |
| | Directional-Coupler Designs | 416 |
| | Coupled-Line Directional Couplers | 427 |
| | Branch-Line Directional Coupler | 432 |
| | Lange Directional Coupler | 434 |
| 6.5 | Hybrid Junctions | 435 |
| | Magic T | 435 |
| | Hybrid Ring | 437 |
| 6.6 | Power Dividers | 442 |
| 6.7 | Microwave Propagation in Ferrites | 450 |
| 6.8 | Faraday Rotation | 460 |
| 6.9 | Microwave Devices Employing Faraday Rotation | 464 |
| | Gyator | 464 |
| | Isolator | 466 |
| | Resonance Isolator | 467 |
| 6.10 | Circulators | 468 |
| | Three-Port Circulator | 471 |
| | Field Analysis of Three-Port Circulator | 473 |
| 6.11 | Other Ferrite Devices | 476 |
| | Problems | 476 |
| | References | 479 |

| | | |
|----------|---|------------|
| 7 | Electromagnetic Resonators | 481 |
| 7.1 | Resonant Circuits | 481 |
| 7.2 | Transmission-Line Resonant Circuits | 485 |
| | Series Resonance; Short-Circuited Line | 485 |
| | Open-Circuited Line | 487 |
| | Antiresonance | 488 |
| 7.3 | Microstrip Resonators | 490 |
| | Circular Disk Resonator | 496 |
| 7.4 | Microwave Cavities | 500 |
| | Rectangular Cavity | 500 |
| | Cylindrical Cavity | 504 |
| 7.5 | Dielectric Resonators | 508 |
| 7.6 | Equivalent Circuits for Cavities | 517 |
| | Aperture-Coupled Cavity | 517 |
| | Loop-Coupled Cavity | 523 |
| ★7.7 | Field Expansion in a General Cavity | 525 |
| | Cavity Field Expansions in Terms of Short-Circuit Modes | 527 |
| | Electric Field Expansion | 528 |
| | Orthogonality Properties | 529 |
| | Magnetic Field Expansion | 531 |
| | Orthogonality Properties | 531 |
| | Relationship between \mathbf{E}_n and \mathbf{H}_n Modes | 532 |
| ★7.8 | Oscillations in a Source-Free Cavity | 533 |
| | Cavity with Lossy Walls | 534 |
| | Degenerate Modes | 536 |
| ★7.9 | Excitation of Cavities | 538 |
| ★7.10 | Cavity Perturbation Theory | 541 |
| | Problems | 545 |
| | References | 548 |
| | | |
| 8 | Periodic Structures and Filters | 550 |
| 8.1 | Capacitively Loaded Transmission-Line–Circuit Analysis | 551 |
| 8.2 | Wave Analysis of Periodic Structures | 557 |
| 8.3 | Periodic Structures Composed of Unsymmetrical Two-Port Networks | 559 |
| 8.4 | Terminated Periodic Structures | 560 |
| 8.5 | Matching of Periodic Structures | 563 |
| 8.6 | k_0 - β Diagram | 564 |
| ★8.7 | Group Velocity and Energy Flow | 566 |
| 8.8 | Floquet's Theorem and Spatial Harmonics | 569 |
| 8.9 | Periodic Structures for Traveling-Wave Tubes | 571 |
| | Periodic Structures for Millimeter-Wave Traveling-Wave Tubes | 577 |
| 8.10 | Sheath Helix | 580 |
| ★8.11 | Some General Properties of a Helix | 583 |
| 8.12 | Introduction to Microwave Filters | 585 |
| 8.13 | Image-Parameter Method of Filter Design | 587 |

| | | |
|-----------|--|------------|
| 8.14 | Filter Design by Insertion-Loss Method | 591 |
| 8.15 | Specification of Power Loss Ratio | 592 |
| | Maximally Flat Filter Characteristic | 593 |
| | Chebyshev Filter | 593 |
| 8.16 | Some Low-Pass-Filter Designs | 595 |
| 8.17 | Frequency Transformations | 598 |
| | Frequency Expansion | 599 |
| | Low-Pass to High-Pass Transformation | 599 |
| | Low-Pass to Bandpass Transformation | 600 |
| | Period Bandpass Mapping | 602 |
| 8.18 | Impedance and Admittance Inverters | 603 |
| 8.19 | A Microstrip Half-Wave Filter | 617 |
| 8.20 | Microstrip Parallel Coupled Filter | 626 |
| 8.21 | Quarter-Wave-Coupled Cavity Filters | 635 |
| 8.22 | Direct-Coupled Cavity Filters | 639 |
| 8.23 | Other Types of Filters | 642 |
| | Problems | 642 |
| | References | 647 |
| 9 | Microwave Tubes | 648 |
| 9.1 | Introduction | 648 |
| 9.2 | Electron Beams with dc Conditions | 650 |
| | Ion-Neutralized Beam | 650 |
| | Beam with Axially Confined Flow | 651 |
| | Brillouin Flow | 652 |
| 9.3 | Space-Charge Waves on Beams with Confined Flow | 654 |
| 9.4 | Space-Charge Waves on Unfocused Beams | 661 |
| 9.5 | Ac Power Relations | 667 |
| 9.6 | Velocity Modulation | 670 |
| 9.7 | Two-Cavity Klystron | 678 |
| | Excitation of a Cylindrical Cavity | 679 |
| | Cavity Excitation by a Velocity-Modulated Beam | 683 |
| 9.8 | Reflex Klystron | 686 |
| 9.9 | Magnetron | 690 |
| 9.10 | <i>O</i> -Type Traveling-Wave Tube | 692 |
| 9.11 | <i>M</i> -Type Traveling-Wave Tube | 699 |
| 9.12 | Gyrotrons | 701 |
| | Field-Particle Interaction in a Gyrotron | 703 |
| 9.13 | Other Types of Microwave Tubes | 708 |
| | Problems | 709 |
| | References | 712 |
| 10 | Solid-State Amplifiers | 713 |
| 10.1 | Bipolar Transistors | 716 |
| | Transistor Biasing | 720 |
| 10.2 | Field-Effect Transistors | 721 |
| | FET Biasing | 724 |

| | | |
|-----------|---|------------|
| 10.3 | Circle-Mapping Properties of Bilinear Transformations | 725 |
| 10.4 | Microwave Amplifier Design Using S_{ij} Parameters | 726 |
| 10.5 | Amplifier Power Gain | 728 |
| | Derivation of Expressions for Gain | 730 |
| 10.6 | Amplifier Stability Criteria | 735 |
| | Conditionally Stable Devices | 740 |
| 10.7 | Constant Power-Gain Circles | 744 |
| | Properties of the Constant Gain Circles | 746 |
| | Stable Devices | 746 |
| | Unstable Devices | 750 |
| 10.8 | Basic Noise Theory | 760 |
| | Filtered Noise | 762 |
| | Noise in Active Devices | 765 |
| | Noisy Two-Port Networks | 766 |
| 10.9 | Low-Noise Amplifier Design | 767 |
| | Noise Figure | 768 |
| | Noise Figure for Cascaded Stages | 770 |
| | Constant Noise-Figure Circles | 772 |
| 10.10 | Constant Mismatch Circles | 776 |
| | Constant Input Mismatch Circle | 778 |
| | Output Impedance-Mismatch Circle | 780 |
| 10.11 | Microwave Amplifier Design | 780 |
| | Single-Stage Amplifier Design | 781 |
| | Design of Second Stage for a Two-Stage Amplifier | 788 |
| 10.12 | Other Aspects of Microwave Amplifier Design | 793 |
| | Problems | 795 |
| | References | 798 |
| 11 | Parametric Amplifiers | 799 |
| 11.1 | <i>p-n</i> Junction Diodes | 800 |
| 11.2 | Manley-Rowe Relations | 804 |
| 11.3 | Linearized Equations for Parametric Amplifiers | 807 |
| 11.4 | Parametric Up-Converter | 809 |
| 11.5 | Negative-Resistance Parametric Amplifier | 814 |
| 11.6 | Noise Properties of Parametric Amplifiers | 821 |
| | Problems | 829 |
| | References | 830 |
| 12 | Oscillators and Mixers | 831 |
| 12.1 | Gunn Oscillators | 832 |
| | Gunn Oscillator Circuits | 835 |
| 12.2 | IMPATT Diodes | 837 |
| 12.3 | Transistor Oscillators | 840 |
| 12.4 | Three-Port Description of a Transistor | 843 |
| 12.5 | Oscillator Circuits | 849 |
| 12.6 | Oscillator Design | 851 |

| | | |
|-------|---|-----|
| 12.7 | Mixers | 856 |
| | Linear Mixer Operation | 861 |
| | Nonlinear Mixer Operation | 862 |
| 12.8 | Mixer Noise Figure | 864 |
| 12.9 | Balanced Mixers | 865 |
| 12.10 | Other Types of Mixers | 868 |
| 12.11 | Mixer Analysis Using Harmonic Balancing | 869 |
| | Problems | 873 |
| | References | 875 |

Appendixes

| | | |
|------------|---|-----|
| I | Useful Relations from Vector Analysis | 876 |
| I.1 | Vector Algebra | 876 |
| I.2 | Vector Operations in Common Coordinate Systems | 877 |
| | Rectangular Coordinates | 877 |
| | Cylindrical Coordinates | 877 |
| | Spherical Coordinates | 878 |
| I.3 | Vector Identities | 879 |
| I.4 | Green's Identities | 880 |
| II | Bessel Functions | 881 |
| II.1 | Ordinary Bessel Functions | 881 |
| II.2 | Modified Bessel Functions | 883 |
| | References | 885 |
| III | Conformal Mapping Techniques | 886 |
| III.1 | Conformal Mapping | 886 |
| III.2 | Elliptic Sine Function | 889 |
| III.3 | Capacitance between Two Parallel Strips | 892 |
| III.4 | Strip Transmission Line | 896 |
| III.5 | Conductor Loss | 898 |
| III.6 | Conductor Losses for a Microstrip Transmission Line | 903 |
| III.7 | Attenuation for a Coplanar Line | 905 |
| IV | Physical Constants and Other Data | 911 |
| IV.1 | Physical Constants | 911 |
| IV.2 | Conductivities of Materials | 912 |
| IV.3 | Dielectric Constants of Materials | 912 |
| IV.4 | Skin Depth in Copper | 912 |
| | Index | 913 |