

Index

• Symbols & Numbers •

~ (tilde), 236
1N4733A Zener diode, 309
2-conductor wire, 187
2N3904 transistor, 111, 271
2N3906 transistor, 272
2N7000 transistor, 273
2-wire power cord, 187, 189, 197
3-wire power cord, repairing, 201–204
3-wire RS-232 configuration, 141
3-wire-to-2-wire ground adapter, 187
5-wire RS-232 configuration, 141
555 timer, 106
9V battery, 259, 319, 320

• A •

A (ampere), 234
A jack, 236
AA and AAA batteries, 319, 320
Abbatron-HH Smitch Web site, 368
AC (alternating current), 357
AC fuseholder, wiring, 192–195
AC in-line switch, adding, 188–191
AC plug, installing, 196–200
AC power, troubleshooting flow chart for, 298
AC socket tester, 294
AC voltage, symbol for, 236
AC wiring, 185
Ace Hardware Web site, 8, 11, 12
acid flux, 29
adapter
 3-wire-to-2-wire ground, 187
 coaxial, 161–162, 164
adapter cable, 206
Adel Nibbler Web site, 13
adjustable capacitor, BC10
adjustable resistor, BC3
Ah (ampere-hours), 319
air circuit style, 97
air variable, BC10
alarm, audible, building, 75–76, 90–94
algorithm, 357

alkaline battery, 321, 322
Allen wrenches, set of, 11, 12
all-in-one tool, 7
alternating current (AC), 357
aluminum foil, 54, 63
Alvin ML100 swing-arm magnifier, 8
American Radio Relay League Web site, 21, 339, 370
American Wire Gauge (AWG) standard, 187
ammeter, 357
ampacity, 357
ampere (A), 234
ampere-hours (Ah), 319
amplification, 357
amplifier. *See also* audio amplifier
 buzz or hum in output from, 207, 300, 301
 inverting, 45
 linear, 361
 vertical, 248
amplitude, 357
analog circuit, troubleshooting, 304–305
analog computing, 241
analog multimeter, 235, 251
analog oscilloscope, 248–249
analog signal, 357
analog switch, 357
anode, identifying, 56
antenna analyzer, 246
antenna, repairing broken, 354
anti-oxidation compound, 179
anti-theft security, 334
arcing, 300
astable, 76
attenuate, 357
audible alarm, building, 75–76, 90–94
audio amplifier
 breadboarding, 44
 constructing, 49–51
 explanation of, 45–46
 schematic for, 44–45
 testing circuit, 52–53
audio cable, 220
audio level controller, building, 73–75, 77–82

- audio problem, diagnosing
 - distortion, 301
 - hum and ripple, 301
 - noise, white and crackling, 302–304
 - overview of, 300
- audio taper pot, 74, BC3
- auto manufacturer service bulletin, 329
- autorange, 357
- auto-ranging meter, 237
- AWG (American Wire Gauge) standard, 187

• B •

- backshell, 220
- balanced wiring, 206
- band-pass filter, 339
- bare feet, working in, 186
- barrier strip, 130
- base, 357
- battery
 - alkaline, 321, 322
 - basics of, 317–318
 - charging and discharging, 326, 355
 - checking voltage of, 258–260
 - description of, 317
 - disposable, 320–322
 - disposing of, 322, 327
 - getting most out of, 325
 - handling, 327
 - lithium-ion (Li-Ion), 324
 - nickel-cadmium (Ni-Cad), 323, 326
 - nickel-metal (NiMH), 321, 323–324, 326
 - 9V, 259, 319, 320
 - operation of, 318
 - power, troubleshooting, 295–296
 - ratings of, 319
 - rechargeable, 320–325, 355
 - replacing, 315
 - safety and, 325–327
 - storing, 327
 - types of, 319, 320
 - vehicle, 888, 331, 333–334
 - working around, 252
- battery charger kit, 60
- battery pack, 319, 324–325
- battery tester, 296
- Battery University Web site, 370
- bayonet-style locking connector, 163
- bead, ferrite, 338, 340–341
- Belkin toolkits, 13
- bent-nose pliers, 8
- beta, 357
- bias voltage, 46
- bipolar voltage, 239, 241
- bistable, 357
- bleeder resistor, BC8
- blind panel, 334
- block diagram, 357
- blow, 357
- blow time, 357
- blunt-nose cutters, 9–10
- blunt-nose tweezers, 9
- BNC connector, 162–163, 179
- body diode, 273
- Bolt Depot Web site, 638
- book
 - recommended, 369
 - Web site of, 1–4
- braid, desoldering, 33
- breadboard, solderless
 - audio amplifier and, 44–46, 49–53
 - components inserted into, 18
 - digital timer and, 46–48, 54–57
 - limitations of, 19
 - materials for, 18–19
 - organization of connections, 17
 - using, 15–18
- breadboarding, 18
- breaker, troubleshooting, 295
- bridge rectifier, 358
- brushing off printed circuit board, 66
- buddy, working with, 186, 253, 350
- buffer, definition of, 111
- bug, 358. *See also* debugging
- building. *See* constructing
- burn, treating, 30
- bus, 34, 39
- butt contact, 109
- butt-splice terminal, 131
- buying
 - batteries, 325
 - cables, 158
 - components, 91, 367
 - function generators, 242
 - tools, 7, 28, 349
- buzz in amplifier output, 207, 300

• C •

- C battery, 319, 320
- cable
 - adapter, 206
 - audio, 220
 - buying, 158
 - choosing correct, 129
 - coaxial, 159–160, 165
 - computer network, 138–139, 152–154
 - crossover, 138, 139, 141, 154
 - maintaining, 311
 - microphone, 205
 - null modem, 141
 - patch, for audio and video, 208
 - RS-232 data, making, 155–158
 - stereo patch, creating, 220–223
 - telephone, 135–137
- cable checker, 152, 246
- CAD (Computer-Aided Drafting), 21
- CadSted software, 21
- CAL signal, 274
- calculator, electronic, 22
- calibration to test equipment, checking, 308
- calibrator, building, 309
- calipers, 15
- capacitance, 358, BC7
- capacitor
 - adjustable or variable, BC10
 - ceramic, BC9
 - construction of, BC8
 - definition of, BC7
 - electrolytic, 51, BC8
 - film, BC9
 - mica and glass, BC9
 - tantalum, BC9
- capacitor tester, 245
- capacity, 358
- car battery
 - connecting regulator to, 88
 - setting up and maintaining connection to, 333–334
 - tapping into power from, 331
- car manufacturer service bulletin, 329
- carbon-composition resistor, BC1–BC2
- caring for tools and equipment, 307, 309–310
- Carson MV-23 dual-power magnifier, 8
- CAT5 UTP (Unshielded Twisted Pair), 138
- cathode, identifying, 56
- Cathode Ray Tube (CRT), 313
- CB-style connector, installing, 168–172
- center, marking before drilling, 13
- center set punch, 13
- centi, 358
- ceramic and metal oxide (cermet) resistor, BC2
- ceramic capacitor, BC9
- certification, 314
- Chaney Electronics C6880 learn-to-solder kit, 32
- channel, 248
- characteristic impedance, 160
- characteristic voltage, 318, 319
- charging algorithm, 326
- charging battery, 326, 355
- chassis of power supply, 240
- chip, definition of, 44
- choke
 - RF, 337, 338, 339, 341
 - split-core ferrite, installing, 345–346
- cigarette lighter socket, 333
- circuit. *See also* integrated circuit (IC)
 - analog, troubleshooting, 304–305
 - closed, 358
 - DC-to-DC converter, constructing, 117–125
 - digital, 46, 305–306
 - linear, 304
 - open, 361
 - precision, BC4
 - repairing, 353–354
 - series, 362
 - shorting out, 236
 - shortwave buffer, constructing, 111–116
 - timer, constructing, 106–110
- circuit breaker, troubleshooting, 295
- cladding, 85
- classes, 314
- cleaning. *See also* maintaining
 - electronic equipment, 311, 314
 - workspace, 60, 310
- clip lead, 353
- clipping, definition of, 53
- closed circuit, 358
- clothespin, 354
- clubs, 314
- CMOS (Complementary Metal-Oxide Semiconductor), 358
- coax stripping tool, 164
- coaxial cable, 159–160, 165
- coaxial connector, 161–164

- coaxial connector crimping tool, 160–161, 171–172, 175, 177
- coincells, 319, 320
- collector, 358
- color
 - for AC wiring, 186
 - modular cable codes, 137
 - network cable codes, 139
 - resistor code for, BC4
 - using consistently, 43–44, 81, 123, 331
- COMMON jack, 236, 262
- comparator, 305
- Complementary Metal-Oxide Semiconductor (CMOS), 358
- component lead
 - soldering to circuit board, 30–32
 - tinning, 109
- component tester, 245
- components
 - buying, 91, 367
 - inserted into solderless breadboard, 18
 - leaded, 19
 - line-rated, 185
 - passive, BC1, 365
 - picking out of tape strip, 68
 - resources for, 365–367
 - semiconductor, 366
 - storing, 366–367
 - tacking in place, 108
- compound ratchet, 160
- compression connector, 167
- compression trimmer, BC10
- computer network cable
 - description of, 138–139
 - making, 152–154
- Computer-Aided Drafting (CAD), 21
- configuration input, 306
- connect, definition of, 51
- connections
 - bad PC-board, 304
 - close terminals and, 79
 - ground, 51
 - heat, and electrical, 196
 - insulation displacement, 139
 - keeping short, 43
 - marking off when building, 107
 - mobile installation and, 331
 - organization of, on solderless breadboard, 17
 - overlapped end-to-end, 109
 - standard conventions for, 206
 - to vehicle battery, setting up and maintaining, 333–334
 - weatherproofing exterior, 179–183
- connector
 - bayonet-style locking, 163
 - BNC, 162, 163, 179
 - CB-style, installing, 168–172
 - cleaning, 314
 - coaxial, 161–164
 - compression, 167
 - DB-style, 139–140
 - direct crimp style, 165–167
 - microphone, installing, 211–215
 - molded, 354
 - PL-249, installing, 168–172
 - RCA, 207–208
 - repairing loose, 354
 - resources for, 365
 - RJ-11, 135, 137
 - RJ-45, 153
 - RS-232, making, 139–141
 - scanner-style, installing, 173–178
 - TV-style, installing, 165–167
 - Type F, 162–163, 165–167, 179
 - twist-on, 167
 - UHF, 162–163, 170
 - XLR, 205–206, 211–215
- constructing
 - audible alarm, 75–76
 - audio amplifier, 49–51
 - audio level controller, 73–75, 77–82
 - calibrator, 309
 - DC-to-DC converter circuit, 117–125
 - dead-bug style, using, 97–99
 - digital timer, 54–57
 - from published schematics, 95–96
 - regulator, 12V-to-5V, 75, 83–89
 - shortwave buffer circuit, 111–116
 - surface-mount printed circuit board, 68–71
 - through-hole printed circuit board, 62–67
 - timer circuit, 106–110
 - voltage calibrator, 309
- contact cleaner spray, 303
- contact, intermittent, 304
- contact wear-out and breadboards, 19
- control input, 306
- Convert software, 22
- convex fillet, 32

- core, 358. *See also* ferrite core
 - corner frequency, 283
 - countersink, 12
 - CPR training, 186, 253
 - crackling noise, 303–304
 - craft show, 314
 - Crescent® wrench, 11, 12
 - crimp splice, 354
 - crimp terminal
 - description of, 130–131
 - installing, 142–143
 - crimping, description of, 129
 - crimping ring, 174
 - crimping tools
 - coaxial connector, 160–161, 171–172, 175, 177
 - hand, 131–135
 - modular-plug, 135–137, 146–148
 - RJ-45, 138–139, 154
 - crossover cable, 138, 139, 141, 154
 - Crowbar Electrical Parts, 332
 - CRT (Cathode Ray Tube), 313
 - current
 - of batteries, 327
 - breadboards and, 19
 - definition of, 233
 - measuring, 249, 251–253, 262–264
 - units of, 234
 - wire and, 187
 - current gain, 255
 - current probe, 249
 - cutoff frequency, 283
 - cutoff state, 305
 - cycle, 358
- D •**
- D battery, 319–320
 - dashboard, installing device inside or under, 334
 - data sheet
 - creating folder for, 269
 - downloading, 54, 104
 - finding, 366
 - DB-9P RS-232 cable, making, 155–158
 - DB-style connector, 139–141
 - DC (direct current), 359
 - DC power fuse, adding, 144–145
 - DC power, troubleshooting flow chart for, 299
 - DC voltage, symbol for, 236
 - DC-blocking capacitor, 76
 - DC-to-DC converter circuit, constructing, 117–125
 - dead-bug technique
 - building circuit using, 97–99
 - constructing timer circuit using, 106–110
 - drawbacks of, 99
 - overview of, 95
 - debugging
 - bug, definition of, 358
 - definition of, 289
 - troubleshooting log and, 293
 - deburring hole, 26
 - decade of frequency difference, 284
 - decibels, measuring in, 256–257, 278–279
 - decoupling resistor, 210
 - deep-cycling lead-acid battery, 326
 - defects in solder, 32
 - delay time, 358
 - Designworks Lite software, 20
 - desoldering, 33
 - detent, 163
 - diac, 359
 - diagonal cutters, 9–10
 - Dial and Panel software, 22
 - dielectric, 359
 - digital circuit, 46, 305–306
 - digital oscilloscope, 248–249
 - digital signal, 359
 - digital timer
 - breadboarding, 46
 - constructing, 54–57
 - explanation of, 47–48
 - schematic for, 46–47
 - digital voltmeter or multimeter, 235, 237, 251
 - diode junction test, 270
 - diode-checking function, 255
 - DIP (Dual In-line Package), 44
 - Dip Trace software, 20
 - direct crimp style connector, 165–167
 - direct current (DC), 359
 - direct detection of interference, 339
 - directions, following, 62
 - disabling input, 306
 - discharge curve, 321
 - discharging battery, 326
 - Discover Circuits Web site, 370
 - discrete component, 359
 - disposable battery, 320–322
 - disposing of battery, 322, 327
 - dissipating static, 15, 54

- distortion of audio, troubleshooting, 301
- double-pole, double-throw (DPDT) switch, 359
- double-pole, single-throw (DPST) switch, 359
- downloading data sheets for IC, 54, 104
- drain, 359
- drawing schematic diagram, 39
- drill press, 11
- drills and drill bits, 11–13, 78
- drip loop, 180
- drive shaft hump, installing device on or to side of, 334
- driving safely, 331
- dry-cell battery, 318
- Dual In-line Package (DIP), 44
- dual power supply, 240
- dummy load, 246
- dust, removing, 313
- duty cycle, 359

● **E** ●

- Eagle software, 20
- ears, as test equipment, 243, 294
- Easy PC software, 20
- Electrical Static Discharge (ESD) protection, 15, BC4
- electrical tape
 - splicing and, 204
 - uses for, 354
 - wrapping around exterior connection, 181–183
- electrolyte, 318
- electrolytic capacitor, 51, BC8
- electromagnetic-frequency interference (EMI), 339
- electromotive force (EMF), 233
- electron, 359
- electronic calculator, 22
- electronic equipment, maintaining, 311–314
- Electronic Kits FG-500 kit, 241
- electronic simulator, 21
- electronics with moving parts, maintaining, 314
- electropotential, 318
- element, 74, BC3
- Elenco
 - AK100 learn-to-solder kit, 32
 - SM-200K SMT Training Course kit, 61
- EMF (electromotive force), 233
- EMI (electromagnetic-frequency interference), 339
- emitter, 359
- enabling input, 306
- energy capacity, 319
- energy density, 322
- equivalent series resistance (ESR), BC7
- errata sheet in instruction manual, 63
- ESD (Electrical Static Discharge) protection, 15, BC4
- expected performance, 290
- Express PCB software, 21
- extension cord, 187
- exterior connection, weatherproofing, 179–183
- eyes
 - protecting, 8, 30
 - as test equipment, 243, 293

● **F** ●

- failure, definition of, 290
- family, 161
- Farad, 359
- fast-blow fuse, 145
- FCC Part 15 rules, 340
- feedback from senses, 243, 293–294
- ferrite bead, 338, 340–341
- ferrite core
 - description of, 337–339
 - installing, 345–346
- ferrite material, 340
- ferrule, 174
- Field-Effect Transistor (FET), 359
- film capacitor, BC9
- film resistor, BC2
- filter
 - high-pass, 284–285, 337–338, 342–344
 - interference-reducing, 338–339
 - low-pass, 281, 285, 339
 - MFJ Enterprises MFJ-711B, 342
 - RC, 281, 285, 341
 - telephone, 337–338
- filtering techniques, 339–341
- fine-point tweezers, 9
- firewall, 333
- first aid
 - burn, treating, 30
 - friend and, 253
 - Web site resources for, 186
- 555 timer, 106
- 5-wire RS-232 configuration, 141
- flagging, 204
- flattopping, definition of, 53

flip-flop, 46
float charge, 326
floating power supply, 240
floor, finding part on, 61
flow charts for troubleshooting
 audio problems, 302
 power problems, 297–299
flux, 28–29
fork terminal, 130–131
forward center console, installing device in, 334
frequency
 definition of, 160
 measurement of, 234, 249
 measuring, 274–277
frequency limit and breadboards, 19
frequency response, measuring, 280–285
friend, working with, 186, 253, 350
front-end overload, 359
full-scale value, 236
full-wave rectifier, 359
function generator, 241–242
fuse
 choosing, 145
 DC power, adding, 144–145
 resources for, 365
 troubleshooting, 295, 300
fuse holder
 AC in-line, wiring, 192–295
 installing fuse in, 144–145
fuse tap, 332–333

• G •

gain, 45
galloping effect, 210
gate punchthrough, 273
gauge, 187
gel-cell battery, 318
GFCI (Ground-Fault Circuit Interrupter) breaker,
 252, 295
giga, 360
glass-cartridge fuse, 145
gluing pads to PC board, 113–114
goggles, 8, 30
Gpaper software, 22
graticle, 246–247
grommet, 333
ground, 360
ground connection, 51

ground loop, 207, 301
ground plane, 97
ground potential, 233
ground rod, 360
Ground-Fault Circuit Interrupter (GFCI) breaker,
 252, 295
grounding clip, personal, 15

• H •

Hakko 936ESD soldering station, 27
half-wave rectifier, 360
Hamcalc software, 22
hand crimper, 131–135
hand drill, 11, 78
hand reamer, 13, 26, 79
handheld device, using in car, 335
handling battery, 327
hazards of AC voltage, 186
heat
 from battery, 327
 electrical connection and, 196
 maintaining equipment and, 312
heat sink, 65
Henry, 360
Hertz (Hz), 234
high-pass filter
 description of, 284–285, 337–338
 installing, 342–344
hiss, 302–303
hot wire, 186, 188
hum in amplifier output, 207, 300–301
hypothesis and troubleshooting, 290, 292
Hz (Hertz), 234

• I •

IC adapter, 366
IC (integrated circuit)
 attaching, 63, 107
 common replacement, 353
 definition of, 44
 555 timer, 106
 ICL7662, 104–105
 keeping in shipping bags, 69
 regulator, 65
 soldering, 71
 voltage regulator, 75

- IC pin, soldering to PC board, 107
- ICL7662 IC, 104–105
- impedance, characteristic, 160
- in parallel, definition of, 266
- in series, definition of, 265
- inductance, 360
- inductor, 365
- inductor tester, 245
- in-line fuse, 332
- in-line fuse holder, wiring, 192–195
- in-line fuse kit, 144–145
- in-line switch, adding, 188–191
- input-signal connection, 51
- installing. *See also* mobile installation
 - AC plug, 196–200
 - CB-style connector, 168–172
 - crimp terminal, 142–143
 - high-pass filter, 342–344
 - marine electronics, 330
 - microphone connector, 211–215
 - phono plug, 216–219
 - PL-249 connector, 168–172
 - scanner-style connector, 173–178
 - split-core ferrite choke, 345–346
 - telephone plug, 146–148
 - transistor, 66
 - TV-style connector, 165–167
- instantaneous voltage, 238
- instructions, following, 62
- insulation displacement connection, 139
- insulator, 360
- integrated circuit (IC)
 - attaching, 63, 107
 - common replacement, 353
 - definition of, 44
 - 555 timer, 106
 - ICL7662, 104–105
 - keeping in shipping bags, 69
 - regulator, 65
 - soldering, 71
 - voltage regulator, 75
- interference
 - avoiding causing, 339–341
 - definition of, 337
 - devices to fight, 337–338
 - direct detection of, 339
 - received, 338–339
- interlock, 252

- Intusoft ICAP software, 21
- inverting amplifier, 45
- isolation transformer, 252

• J •

- J battery, 319
- jack
 - A, 236
 - COMMON, 236, 262
 - phono, 207
 - telephone, replacing, 149–151
- Jameco
 - IC Adapter, 366
 - solderless breadboard, 17
 - Web site, 370
- jeweler screwdrivers, 11
- JFET (Junction Field-Effect Transistor), 360
- Joule, 360
- jumper wires
 - bare, 19
 - insulated, 18
 - single-sided PC board kits and, 64
 - stripping insulation off, 43
- junction between wires, 109
- Junction Field-Effect Transistor (JFET), 360
- junk box, keeping, 350, 367

• K •

- Keystone Electronics Company Web site, 368
- kilo, 360
- kit
 - battery charger, 60
 - Elenco SM-200K SMT Training Course, 61
 - function generator, 241
 - in-line fuse, 144–145
 - learn-to-solder, 32
 - sockets and, 90
 - for surface-mount printed circuit board, 61, 68–71
 - for through-hole printed circuit board, 60, 62–67
 - UT-5 Universal Timer, 76
- Klein Company, 8
- knife, utility, 10, 84
- Kronus
 - toolkits, 13
 - wire stripper, 14
- Kynar® insulation, 102

• L •

lab standards, setting, 310
ladder diagram, 34
layout, starting with, 24
lead, working with, 28
lead-acid battery, 318, 324, 326
leaded components, 19
leads
 clip, 353
 component, 30–32
 identifying negative and positive, 51
 tinning, 114–115
leakage resistance, BC4, BC7
LED, color of, 67
legal issues with mobile installation, 331
Lexic Web site, 12
licensing, 314
lighter fluid, 311
lighting workspace, 8, 59, 349
limitations of breadboard, 19
line voltage, 361
linear amplifier, 361
linear circuit, 304
linear power supply, 297
linear regulator, 83
linear tapered pot, 74
Linear Technology, LTSPICE, 21
line-rated component, 185
lithium-ion (Li-Ion) battery, 324
LM34 sensor, 209–210, 224–229
load, 361
loading circuit being tested, 248
lock washers, 92
locking pliers, 8
lockout, 252
log, 256
log book, keeping, 291–292
logarithmic ratio versus numeric ratio, 256–257
logarithmic taper pot, 74, BC3
logic analyzer, 250
logic probe, 245
long-nose pliers, 8–9
low-pass filter, 281, 285, 339
LTSPICE (Linear Technology), 21

• M •

machinist's vise, 12, 60
magazines
 building circuits from schematics in, 95–96
 recommended, 369
Magic Smoke, 289
magnification, 8, 19, 61
maintaining
 electronic equipment, 311–314
 skills, 314
 tools and equipment, 307, 309–310
 workspace, 310–311
maintenance schedule, 315
Manhattan style
 building circuit using, 99–100
 constructing shortwave buffer circuit using,
 111–116
 drawbacks of, 101
 overview of, 95
marine electronics, installing, 330
marking
 center of hole before drilling, 13
 connections when building, 107
Maryland Metrics Web site, 15
mat, static-dissipation, 15, 54
maximum applied voltage, BC4
MC14536B IC, 54
measurement
 of current, 262–264
 in decibels, 256–257, 278–279
 equipment for, 234–242
 of frequency response, 280–285
 of period and frequency, 274–277
 recording in log, 292
 of resistance, 253–254, 265–268
 safety issues and, 251–253
 sight, sound, smell, touch, and, 243, 293–294
 types of, 233–234
 of voltage, 233, 249, 251–253, 258–261
measuring stick, 14–15
mechanical assembly, tightening up, 65
mechanical drawing software, 21–22
mechanical hardware, 367–368
mechanic's rule, 14
Mega, 361
memory effect, 323

- Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET), 269, 305
- metalworking, 23–26
- MFJ Enterprises MFJ-711B filter, 342
- mica and glass capacitor, BC9
- micro, 361
- Micro Cap software, 21
- microphone cable, 205
- microphone connector, installing, 211–215
- milli, 361
- mobile installation
 - finding room for gadget, 334–335
 - overview of, 329–330
 - power supply for, 331–334
 - safety issues with, 330–331
- modular-plug crimping tool
 - description of, 135–137
 - using, 146–148
- molded connector, 354
- monostable configuration, 106
- MOSFET (Metal-Oxide Semiconductor Field-Effect Transistor), 269, 305
- mounting equipment
 - mobile electronics, 334–335
 - safety issues and, 330
- multi-conductor cable, 159
- multimeter
 - description of, 234–237
 - using to test audio amplifier circuit, 52–53
- multimeter resistance scale, 80
- Murphy's Law, 361

• *N* •

- nano, 361
- National Electrical Code, 361
- National Electrical Manufacturers Association (NEMA) rating number, 196
- N-channel, 273
- needle files, 13
- needle-nose pliers, 8, 19, 106
- negative lead, identifying, 51
- network cable, 138–139
- neutral wire, 186
- nibbling tool, 13
- nickel-cadmium (Ni-Cad) battery, 323, 326
- nickel-metal (NiMH) battery, 321, 323–324, 326
- 9V battery, 259, 319, 320
- noise, white and crackling, 302–304

- nominal value, BC5, BC7
- non-inductive resistor, BC1–BC2
- non-linear taper, BC3
- notch filter, 339
- notebook
 - keeping, 20, 350–351
 - loaned tools and, 307
 - parts supply and, 311
 - troubleshooting and, 291–292
- NPN device, 271
- NPN transistor, 305
- null modem cable, 141
- numeric ratio versus logarithmic ratio, 256–257
- nutdrivers, 11–12

• *O* •

- observed performance, 290
- octave of frequency difference, 284
- offset, 361
- Ohm's Law, 234, 253–254, 265–268, 305
- “one hand in pocket” rule, 186
- 1N4733A Zener diode, 309
- online tutorial, 314
- op-amp, 44, 305
- open circuit, 361
- open-terminal voltage, 259, 295
- organization and troubleshooting, 291–294
- oscillator, 46
- oscilloscope
 - analog and digital, 248–249
 - function of, 246–248
 - logic and spectrum analyzers, 250
 - measuring with, 249
- output-signal connection, 51
- overload, 338, 342

• *P* •

- packaging styles, 366
- pad-based technique (Manhattan style)
 - building circuit using, 99–100
 - constructing shortwave buffer circuit using, 111–116
 - drawbacks of, 101
 - overview of, 95
- Panavise 301 vise, 14, 60
- panel, making, 23–26
- parallel, 361

- parasitic inductance or capacitance, BC1, BC7
Part 15 device, 340
- parts
- checking against list of, 68
 - finding on floor, 61
 - obsolete, finding, 96
 - sorting, 63
 - storing, 69
- pass transistor, 83
- passive component, 365, BC1
- patch cable
- for audio and video, 208
 - stereo, creating, 220–223
- patch cord, 137
- PC board. *See* printed circuit (PC) board
- PC board vise head, 14
- PCB. *See* printed circuit (PC) board
- PCB layout, 20
- peak hold, 237
- peak voltage, 238
- pegging needle, 237
- perfboard, 102–103, 117
- performance, difference between expected and observed, 290
- period
- definition of, 234
 - measuring, 274–277
- phone plug, 137, 208–209
- phono plug
- installing, 216–219
 - types of, 207–208
- photovoltaic effect, 362
- Pi filter, 341
- pico, 362
- pin label, 102
- pink noise, 302
- PL-249 connector, installing, 168–172
- pliers, 8–9, 131
- plug
- AC, installing, 196–200
 - phone, 208–209
 - phono, 207–208, 216–219
 - polarized, 187
- plugboard, 15–19
- PNP device, 272
- PNP transistor, 305
- pointed-nose cutters, 9–10
- polarized plug, 187
- Pomona Electronics 1508 test lead holder, 310
- positive lead, identifying, 51
- potential, 233
- potentiometer (pot), 74, BC3
- power cord, splicing, 201–204
- power dissipation, 83, BC3–BC4
- power problems
- batteries, 295–296
 - common, 300
 - flow chart for troubleshooting, 297–299
 - fuses and breakers, 295
 - overview of, 294
- power supply
- for building and testing circuits, 239–240
 - for mobile installation, 331–334
- practicing repairs, 293
- precision circuit, BC4
- premises wiring, 150
- preventing shock, 186, 195, 251–253
- pride, taking in craft, 351
- primary battery, 320
- printed circuit (PC) board. *See also* surface-mount printed circuit board; through-hole printed circuit board
- bad connections on, 304
 - definition of, 49
 - gluing pads to, 113–114
 - single-sided, 64
 - soldering IC pins to, 107
 - types of, 49
- prototype, definition of, 73
- prototyping, 73
- prototyping board, 15–19
- pull-out strength, 132
- punch-down block, 150
- *Q* •
- quiescent value, 46
- *R* •
- radiator, unintentional, 340
- radio-frequency interference (RFI), 339
- radio-frequency (RF) signal
- coaxial cable and, 159–160
 - exposure to, 252
 - ferrite material and, 340
 - resistor for, BC4
- radio-frequency test equipment, 245–246

- rail, 17–18, 34
 - Ramsey Electronics
 - LABC1C Lead-Acid Battery Charger kit, 60
 - UT-5 Universal Timer kit, 76
 - Web site, 371
 - range switch, 236, 237
 - ratcheting action, 160–161
 - RC filter, 281, 285, 341
 - RCA connector, 207–208
 - reading schematic diagram, 35–38
 - reamer, 13, 26, 79
 - received interference, 338–339
 - rechargeable battery
 - disposable compared to, 320–321
 - grouping and conditioning, 325
 - quick-charging dead, 355
 - types of, 322–324
 - rechargeable battery voltage, 258
 - rectifier, 362
 - recycling battery, 322, 327
 - refrigerating battery, 325
 - refrigerator storage container lid, 69
 - regulation, 75
 - regulator
 - troubleshooting, 300
 - 12V-to-5V, building, 75, 83–89
 - regulator IC, 65
 - regulator transistor, 300
 - remote control panel, 335
 - removing
 - dust, 313
 - wrapped wire, 121
 - repairing
 - broken antenna, 355
 - circuit, 353–354
 - loose connection, 354
 - 3-wire power cord, 201–204
 - resistance, measurement of, 234, 236, 253–254, 265–268
 - resistor
 - adjustable, BC3
 - bleeder, BC8
 - carbon-composition, BC1–BC2
 - ceramic and metal oxide (cermet), BC2
 - choosing, BC4
 - decoupling, 210
 - description of, BC1
 - film, BC2
 - reading, BC4
 - tolerance and temperature coefficient of, BC5
 - variable, 363
 - wirewound, BC2
 - resistor network, BC3
 - resources. *See also* Web sites
 - assembling, 350
 - audio installation, 334
 - books, 369
 - CB radios, 168
 - electronic components, 365–367
 - interference, 339
 - magazines, 369
 - marine electronics, 330
 - measuring with oscilloscope, 249
 - mechanical hardware, 367–368
 - resistors, BC5
 - schematic diagrams, 38
 - tutorials, 370
 - RF choke, 337–339, 341
 - RF (radio-frequency) signal
 - coaxial cable and, 159–160
 - exposure to, 252
 - ferrite material and, 340
 - resistor for, BC4
 - RFI (radio-frequency interference), 339
 - rheostat, BC3
 - ribbon-cable crimp, 139
 - right-angle adapter, 164
 - ring, 137
 - ring terminal, 130
 - ripple, 300–301
 - RJ-11 connector, 135, 137
 - RJ-45 connector, 153
 - RJ-45 crimping tool, 138–139, 154
 - RMS (root-mean-square) voltage, 238–239
 - robot, working around, 252–253
 - Rochester Electronics Web site, 96
 - roll capacitor, BC8
 - rolloff, 284
 - root-mean-square (RMS) voltage, 238–239
 - RS-232 connector, making, 139–141
 - RS-232 data cable, making, 155–158
 - rubberband, 354
- S ●
- safety equipment, 8, 30
 - safety ground wire, 186

- safety issues
 - with batteries, 325–327
 - buddy, working with, and, 186, 253, 350
 - installing filters to input cable on TV receiving equipment, 342
 - with measuring, 251–253
 - mobile installation and, 330–331
 - working when tired and, 70
- saturated state, 305
- scale, 362
- Scale software, 21
- scanner-style connector, installing, 173–178
- scheduling maintenance, 315
- schematic capture, 20
- schematic diagram. *See also* schematic diagram, published
 - for audio amplifier, 44–45
 - audio level controller, 74
 - for digital timer, 46–47
 - drawing, 39
 - history of, 34
 - purposes of, 34
 - reading, 35–38
 - tracking progress on, 44
- schematic diagram, published
 - being wary of, 96
 - building from, 95
 - preparing to build from, 96–97
- scissors, 10
- scope (oscilloscope)
 - analog and digital, 248–249
 - function of, 246–248
 - logic and spectrum analyzers, 250
 - measuring with, 249
- Scotch electrical tape, 204
- SCR (Silicon-Controlled Rectifier), 362
- scratch awl, 13, 78
- screwdrivers, 11, 12
- scrubbing pad, synthetic, 85
- seat, mounting equipment under, 335
- secondary battery, 320
- semiconductor components, 366
- senses, feedback from, 243, 293–294
- sensor. *See also* temperature sensor
 - cleaning, 314
 - definition of, 209
- serial, 362
- series circuit, 362
- service bulletins of car manufacturer, 329
- sharing information with others, 351
- shell, 163, 220
- shielded twisted-pair cable, 220
- shock, preventing, 186, 195, 251–253
- shorting out circuit, 236
- shortwave buffer circuit, constructing, 111–116
- side mount, 334
- signal generator, 245
- Silicon-Controlled Rectifier (SCR), 362
- sine wave, 362
- single-pole, double-throw (SPDT) switch, 362
- single-pole, single-throw (SPST) switch, 362
- skills, maintaining, 314
- sleeve, 137
- slip-joint pliers, 8–9
- slow-blow fuse, 145
- Small Parts Company Web site, 368
- smell, as test equipment, 243, 293
- SMT (surface-mount technology), 59
- socket header, 102–103
- sockets
 - cigarette lighter, 333
 - kit and, 90
 - placing on perfboard, 118
 - wall, 294
- software tools
 - electronic simulators, 21
 - mechanical drawing, 21–22
 - schematic and PC board layout, 20–21
 - utilities and calculators, 22
- solder bridge, 363
- solder cup, 139–140
- solder mask, 363
- solder sucker, 33
- soldering
 - desoldering, 33
 - IC pins to PC board, 107
 - ICs, 71
 - introduction to, 30–32
 - with kit, 32
 - as skill, 223
 - SMT parts, 69–70
 - tools for, 27–29
- soldering gun, 28
- soldering iron, 27, 354
- soldering iron tips, 28
- soldering pencil, 27
- soldering station, 27

- solderless breadboard
 - audio amplifier and, 44–46, 49–53
 - components inserted into, 18
 - digital timer and, 46–48, 54–57
 - limitations of, 19
 - materials for, 18–19
 - organization of connections, 17
 - using, 15–18
- solid wire, 131
- sorting parts, 63
- spade terminal, 130–131
- SPDT (single-pole, double-throw) switch, 362
- spectrum analyzer, 250
- splicing power cord, 201–204
- split-core, 340
- split-core ferrite choke, installing, 345–346
- splitter, description of, 75
- sponge, using, 30
- SPST (single-pole, single-throw) switch, 362
- square wave, 363
- stack capacitor, BC8
- standard connection conventions, 206
- Standing Wave Ratio meter, 245
- static, dissipating, 15, 54
- station cable, 137
- steel wool, 85
- stereo patch cable, creating, 220–223
- storing
 - battery, 327
 - components, 366–367
 - parts, 69
 - tools and equipment, 308
- straight-through cable, 138–139, 154
- stripping
 - coax cable, 164
 - wire, 134
- stud size, 130
- surface-mount printed circuit board
 - building, 61
 - constructing, 68–71
 - description of, 59
- surface-mount technology (SMT), 59
- sweep speed, 246
- swing-arm magnifier, 8
- switch
 - AC in-line, adding, 188–191
 - analog, 357
 - double-pole, double-throw, 359
 - double-pole, single-throw, 359

- range, 236–237
- resources for, 365
- single-pole, double-throw, 362
- single-pole, single-throw, 362
- transistor operated as, 305
- trigger, 248
- symbols for schematic diagram, 35

● T ●

- tacking component in place, 108
- tackle box, 308
- tack-solder technique, 70–71
- tantalum capacitor, BC9
- tape, electrical
 - splicing and, 204
 - uses for, 354
 - wrapping around exterior connection, 181–183
- tape strip, picking components out of, 68
- tapered pot, 74
- Technology Systems Web site, 20
- telephone filter, 337–338
- telephone jack, replacing, 149–151
- telephone modular cable, crimping, 135–137
- telephone plug, installing, 146–148
- temperature coefficient, 363, BC5
- temperature sensor
 - creating, 224–229
 - overview of, 209
 - wiring diagram, 210
- terminal, crimp
 - description of, 130–131
 - installing, 142–143
- terminal crimping tool, 131–135
- terminal strip, 98, 130
- test equipment
 - checking calibration of, 308
 - component tester, 245
 - counter, 243–244
 - function generator, 241–242
 - logic probe, 245
 - oscilloscope, 246–250
 - power supply, 239–240
 - radio-frequency, 245–246
 - taking care of, 307, 309–310
 - voltmeter, 234–237
- test lead holder, 310
- test point, making, 44
- test probe, 236, 247

- testing. *See also* test equipment
AC socket, 294
audio amplifier circuit, 52–53
DC-to-DC converter circuit, 125
scanner-style connector, 178
shortwave buffer circuit, 116
in steps, 350
temperature sensor, 227
timer circuit, 110
transistor, 255, 269–273
THD, 363
thermal shutdown, 83
thermistor, 363
3-wire power cord, repairing, 201–204
3-wire RS-232 configuration, 141
3-wire-to-2-wire ground adapter, 187
through-hole printed circuit board
battery charger kit and, 60
constructing, 62–67
description of, 59
thyristor, 363
tie point, 98
tilde (~), 236
time
measurement of, 234, 249
taking when working, 349
timer circuit, constructing, 106–110
timer
breadboarding, 46
constructing, 54–57
explanation of, 47–48
schematic for, 46–47
tinning
definition of, 30
pads and leads of transistor, 114–115
tip, 137
Tip contact, 80
tired, working when, 70
TO-92 package, 209–210
tolerance, BC5
tools. *See also* crimping tools; test equipment
buying, 7, 349
coax stripping tool, 164
cutters and knives, 9–10, 84
drills and drill bits, 11–13, 78
Klein Company and, 8
measuring stick, 14–15
notebook, 20
overview of, 7–8
pliers and tweezers, 8–9, 131
safety equipment, 8
screwdrivers and wrenches, 11–12
SMT assemblies, 61
software, 20–22
solderless breadboard, 15–19
specialized electronic, 14
taking care of, 307, 309–310
unwrapping tool, 121
wire-wrap method and, 102–103
toroid, 340
touch, as test equipment, 243, 294
traces, 274
tracking progress on schematic diagram, 44
trade show, 314
transformer, isolation, 252
transient, 363
transient protection, BC4
transistor
analog circuit and, 304–305
common replacement, 353
installing, 66
MOSFET, 269, 305
NPN, 305
pass, 83
PNP, 305
regulator, 300
testing, 255, 269–273
tinning leads of, 114–115
2N3904, 111, 271
2N3096, 272
2N7000, 373
transistor tester, 245
transition, 276
trap filter, 339
triac, 363
trickle charge, 326
trigger switch, 248
trimmer, BC3
trimming, BC2
trip, 363
troubleshooting
analog circuits, 304–305
audio level control, 82
audio problems, 300–304
cable, 152
crimping, 143
DC power fuse, 145
DC-to-DC converter circuit, 125

troubleshooting (*continued*)

- dead-bug technique and, 110
- definition of, 289
- digital circuits, 305–306
- failure and, 290
- microphone connector, 215
- organizing thoughts and, 291–294
- output voltage, 89
- phono plug, 219
- power problems, 294–300
- process of, 290–291
- scanner-style connector, 178
- sharing stories of, 293
- shortwave buffer circuit, 116
- stereo patch cable, 223
- telephone jack, 151
- telephone plug, 148
- TV-style connector, 166
- wiring error, checking for, 57
- true-RMS measurement capability, 237, 239
- TV-style connector, installing, 165–167
- tweezers, 8–9
- twisting pairs of wires, 110
- twist-on connector, 167
- 2-conductor wire, 187
- 2N3904 transistor, 111, 271
- 2N3906 transistor, 272
- 2N7000 transistor, 273
- 2-wire power cord, 187, 189, 197
- Type F connector, 162–163, 165–167, 179

• U •

- UHF connector, 162–163, 179
- unbalanced wiring, 206
- Underwriters Laboratories, 185
- unintentional radiator, 340
- University of Nebraska Electrical Engineering Shop
 - page, 20
- University of Washington Electrical Engineering
 - Store Web site, 370
- Unshielded Twisted Pair (UTP), 137
- unwrapping tool, 121
- utility knife, 10, 84
- utility software packages, 22
- UTP (Unshielded Twisted Pair), 137

• V •

- vacuuming workspace, 310
- vacuum-tube equipment, 313
- varactor, 363
- variable capacitor, 363, BC10
- variable resistor, 363
- varistor, 363
- Vector Engineer software, 21
- Vectronics VEC-4001K kit, 241
- vehicle battery
 - connecting regulator to, 88
 - setting up and maintaining connection to, 333–334
 - tapping into power from, 331
- vehicle manufacturer service bulletin, 329
- ventilation for workspace, 8
- vertical amplifier, 248
- video problems, diagnosing, 304
- vise
 - clothespin or rubberband as, 354
 - holding PC board with, 60
 - Panavise, 14
 - using, 12
- Vise-Grips™, 8
- volt, 363
- voltage
 - AD and DC components of, 260
 - of battery, checking, 258–260
 - bias, 46
 - bipolar, 239, 241
 - breadboards and, 19
 - characteristic, 318–319
 - hazards of AC, 186
 - instantaneous, 238
 - line, 361
 - maximum applied, BC4
 - measuring, 233, 249, 251–253, 258–261
 - open-terminal, 259, 295
 - peak, 238
 - of rechargeable battery, 258
 - RMS (root-mean-square), 238–239
 - symbols for, 236
 - troubleshooting output, 89
 - voltage calibrator, building, 309
 - voltage divider, 45, 74
 - voltage ratings, BC4

voltmeter
description of, 234–237
using to test audio amplifier circuit, 52–53

• W •

wall socket, 294
water, dealing with equipment that fell in, 312
watt, 363
watt-hour, 319
waveform, 241
weatherproofing exterior connection, 179–183
Web sites
Abbatron-HH Smitch, 368
Ace Hardware, 8, 11–12
Adel Nibbler, 13
Alvin Company, 8
American Radio Relay League, 21, 339, 370
audio installation, 330
battery operation, 318
battery recycling, 327
Battery Tender company, 326
Battery University, 370
Bolt Depot, 368
for book, 1–4
building circuits from schematics on, 95–96
car manufacturer service bulletins, 329
Carson Optical, 8
CPR training, 186
Crowbar Electrical Parts, 332
for desoldering tools, 33
Discover Circuits, 370
electrical safety, 186
Electrical Static Discharge (ESD), 15
electronic calculators, 22
electronic components, 365–366
electronic simulators, 21
Elenco Electronics, 61
exposure to RF, 252
film capacitors, BC9
first aid, 186
free electronic design software, 20
function generator kits, 241
fuseology, 145
ground loops, 301
home phone wiring, 149
Jameco, 17
Keystone Electronics Company, 368

Klein Company, 8
learn-to-solder kits, 32
Lexic, 12
Linear Technology, 21
logic probe, 245
magazines, 369
Maryland Metrics, 15
measuring with oscilloscope, 249
mechanical drawing software, 21–22
MFJ Enterprises, 342
network connector wiring, 138
PC board fabricator, 21
Pomona Electronics 1508 test lead holder, 310
power-supply circuit description, 297
for radio installation, 330
Ramsey Electronics, 60
resistor color code, BC4
resistors, BC5
Rochester Electronics, 96
schematic and PC board layout software, 20
schematic diagram symbols, 35
schematic diagrams, 38
Small Parts Company, 368
Standing Wave Ratio meter, 245
telephone system, 137
transistor functions and basic amplifiers, 111
tutorials, 370
University of Washington Electrical Engineering Store, 370
vendors, 370–371
Wikipedia, 370
Webtronics LP-1 logic probe, 245
Weller soldering station, 27
Western Union knot, 87, 197
wet-cell battery, 318
white noise, 302–303
wick, desoldering, 33
Wikipedia Web site, 370
wiper
adjustable resistor and, BC3
tapered pot and, 74
wire
bare, keeping, 108
choosing correct, 129
color of, 81, 123
crimp terminal and, 131
current-capacity of, 187
insulated, 18, 185

wire (*continued*)

junction between, 109

making contacts with, 109

for solderless breadboard, 17

stripping, 134

twisting pairs of, 110

wire cutters, 9–10, 19

wire nut, miniature, 354

wire stripper, 14

wirewound resistor, BC2

wire-wrap method

building circuit using, 101–105

constructing DC-to-DC converter circuit using,
117–125

cutting wire for, 122

direction for, 120

drawbacks of, 104

making changes or correcting errors, 121

overview of, 95

wiring

AC, 185–186

AC fuseholder, 192–195

balanced and unbalanced, 206

error, checking for, 57

premises, 150

working when tired, 70

workspace

lighting, 8, 59, 349

maintaining, 310–311

preparing, 59–60

ventilation of, 8

wrapping electrical tape around exterior connec-
tion, 181–183

wrapping tool, motorized, 103

wrenches, 11

• X •

XLR connector

description of, 205–206

installing, 211–215

• Y •

yardstick, 15

• Z •

Zener diode, 309

zero-crossing, 238

zinc-carbon battery, 321–322

zip cord, 187, 197