
INDEX

- acid rain, 5, 14
- ACSR, 163–164, 170
- actuators, 616, 625, 627–628, 639
- admittance, 53–54, 292
- Alnico, 632
- alternating waveform, 51
- alternator, 359
- Ampere’s law, 172, 253, 265, 268, 272, 376, 381, 625
- arcing, 34–36, 406, 413, 484
- armature reaction, 489
- ash, 14
- audio transformer, 638

- baseline power, 6, 8, 21
- B-H curve, 631–634
- boiling water reactor, 26
- bundled conductors, 164, 193, 218
 - equivalent radius, 193, 218
- bushings, 249–251

- capacitance-to-neutral, 217
- capacity factor, 7–8
- capital cost, 8

- egs units, 670, 672
- circuit breaker, 3, 20, 34–35, 38, 42, 84, 234, 405–406, 409, 413
 - assembly, 34, 38
 - dead-tank, 36–37
 - failure analysis, 38–42
 - live-tank, 36
- cogeneration, 361
- coherent unit systems, 670
- coil energy, 254, 260–261
- coil inductance, 254, 259–260, 283
- combined cycle, 20–21
- commutation, 567, 601
- compensation capacitor, 81, 90, 134–135, 138–139
- complex conjugate, 61
- complex spatial vectors, 177–178
- condenser, 11, 25
- conductance, 292
- conductor table, 170
- conductors, *see* transmission lines
 - ACSR, 163–164, 170
 - bundled, 164, 201

- insulated, 162, 168–169
- magnetic field, 171
- stranded, 163, 169, 188
- consumer service drops, 43–44
 - main breaker 45–46
- converter, 590–591, 596–598, 603, *also see* inverters and rectifiers
- cooling ponds, 11
- cooling towers, 9, 11–12
- corona, 157–158, 164, 198–201
- creosote, 158
- cross-field theory, 467–469
- current, 51
 - definition of, 50
 - ground, 106
 - line, 120
 - load, 81
- current chopping, 410, 413
- current division, 70–71

- dc machines, 483
 - armature, 489
 - commutator, 484–485, 487
 - compound connection, 494
 - efficiency, 500, 506, 514
 - equivalent circuit, 491–493
 - excitation methods, 493–494
 - flux, 491
 - generator, 489–491, 508–509
 - induced voltage, 493
 - inter-poles, 486
 - mechanical output power, 495, 499, 505, 512–513
 - motor, 487–488, 495, 501, 510, 516
 - motor control, 538–542, 603–606
 - operating point, 499, 506, 519
 - operating principle, 487–491
 - rotor, 484–488
 - separately excited, 492, 493, 495–501, 516, 539
 - series connection, 493–494, 510–516
 - shunt connection, 493–494, 501–509, 516
 - speed, 491, 493, 506
 - starting current, 498, 504
 - stator, 483–484, 486
 - supply power, 498, 504, 512
 - terminal voltage, 492
 - torque, 493, 495, 500, 507, 514, 524
 - windings, 483–485
- dead-end towers, 161, 165
- delta connection, 98–99, 113–114
 - generators, 113–114
 - loads, 115–116, 118, 120
- delta–wye transformation
 - generators, 114
 - impedances, 60–61, 99
- diode, 549–552, 560
- disconnect switch, 19–20, 36–38, 158
- distribution
 - overhead line, 42–43
 - pole, 42–44
 - substations, 33–34
 - system, 4–5, 33–45
 - radial, 41
- double revolving field theory, 466–467
- downcomers, 10

- economics, 6–7, 27
- economizer, 10
- eddy current, 247, 252, 283
- electric field
 - charged particle generated, 193
 - definition of, 194
 - force on charge, 616–617
 - intensity, 194–195
 - lines, 193–195
 - transmission line generated, 194
- electric flux density, 193–194
- electric shock, 198, 201
- electrical motor, 619–621, *also see* dc motors and induction motors
- electrostatic force, 617
- electrostatic precipitators, 13, 617
- English units, 670, 672
- EPDM, 167
- even function, 562

- Faraday's equation, 253, 258, 379, 426–427, 490, 619
- Ferranti effect, 83, 225
- ferrite, 261, 632
- firing circuits, 584–585, 599–600
- flashover, 165, 234, 413, 484
- flyash, 13
- Fourier series, 561–562
 - base component, 377

- four-wire system, 106–108
- Francis turbine, 31
- freewheeling diodes, 590, 592–593
- fuel injection, 9–10
- fundamental frequency, 562, 573
- fuse cutout, 44, 157, 159

- gauss (unit), 173, 672–673
- Gauss' Law, 193–194
- generator load, 359
- generator parameters, 374
- geometric mean distance, 192, 217
- geometric mean radius, 169–170, 188, 193, 218
- greenhouse effect, 21
- ground current, 106
- ground fault, 405–406
- grounding, 245
- ground rod, 158, 163
- GTO, 549, 556–557, 560, 590

- harmonic frequencies, 562, 574
- health concerns, 158, 171, 182
- high voltage dc, 155–156, 596–597
- horsepower, 433
- hot stick, 44
- hydroelectric, 5, 27–30
 - low-head, 29
 - high-head, 30, 32
- hysteresis loss, 251, 283

- IEEE, 50
- IGBT, 549, 558–560, 566, 590
- image conductors, 201
- impedance, 51–53, 92
 - parallel connection, 54
 - series connection, 53
 - triangle, 52
- induction motors, 418
 - blocked rotor test, 443, 445–447, 449
 - control, 418, 543–549, 607–611
 - developed power, 433, 437, 467
 - efficiency, 433, 438, 473
 - electrical power, 432, 467
 - energy balance, 433
 - equivalent circuit, 429–432, 448, 468
 - force generation, 426, 428–429
 - induced voltage, 426, 430
 - leakage reactance, 431–432
 - mechanical power, 432–433, 437, 472
 - no-load test, 443–445, 449
 - operating point, 438, 441–443, 472, 475
 - operating principle, 424–425, 429, 466–469
 - parameter measurement, 443
 - rotor, 418, 420, 422–423, 430
 - single-phase, 418–419, 465, 468
 - slip, 427, 430, 437–438, 466–467
 - speed, 427–428, 431, 439
 - squirrel cage rotor, 422–424
 - starting current, 436
 - stator, 418, 420–422, 430
 - supply voltage, 432
 - three-phase, 418–419, 424–425
 - windings, 420–421
 - wound rotor, 423
- insulator string, 165
- insulators, 157–161
 - ball and socket, 164–166
 - cap and pin, 164–166
 - composite, 165–167
 - flashover, 234
 - porcelain post, 165
- interconnection, 4, 155
- inverters, 548, 587–590, 593, 596, 607, *also see* rectifiers
- line-commutated thyristor-controlled, 593
- iron core, 246, 247, 251, 283, 299, 346
 - B-H (magnetization) curve, 251–252, 256, 261–262, 264–267, 271
 - neglecting, 265
 - saturation, 261–262, 265, 267, 269, 382, 626
- iron damage, 101

- Kaplan turbine, 29
- Kirchhoff's current law, 70, 72
- Kirchhoff's voltage law, 76

- lamination, 247–248
- lightning, 20, 38, 157–158, 163, 234, 405
- line current, 120
- line faults, 38, 405
- line losses, 279, 373

- line transposition, 191–192, 217
- line voltage, 2, 102–104, 120, 194
- loads, 80–81, 92
 - current, 81
 - voltage, 107, 120
- loop analysis, 77
- Lorentz force, 426–427, 488, 617–618
- loudspeaker, 635, 640

- machine constant, 491, 495
- magnetic circuit
 - air gap, 262–263, 267–269, 272, 340
 - toroidal, 253, 339
- magnetic field
 - conductor moving in, 426, 618–619
 - current-carrying conductor generated, 171, 174
 - Earth's, 171
 - energy content, 173–174, 186–187, 260, 622–623
 - force generation, 427, 429
 - force on charge, 616–617
 - transformer, 246
- magnetic field intensity, 172, 253
- magnetic flux, 173, 253, 257, 352
 - generation, 622
 - inside conductor, 185–186
 - linkage, 189–191, 353
 - outside conductor, 184–185
 - total conductor generated, 187–188
 - transformer, 245–246
- magnetic flux density, 173, 253
- magnetic path length, 253, 255
- magnetic switch, 623, 627–628
- magnetization curve, *also see*
 - B-H curve
- magnetizing current, 273, 283
- magnetizing inductance, 283, 291–292, 321, 323, *also see* coil inductance
 - rating, 299
- Mathcad, 642
 - arg(), 75
 - complex conjugate, 83
 - cspline, 266
 - editing keystrokes, 645
 - equation solvers, 653
 - Find(), 75, 654–655
 - function definition, 650
 - functions, 647–649
 - imaginary number representation, 73, 646
 - magnitude operator 75
 - matrices, 655–656
 - Maximize(), 226, 652–653
 - Minimize(), 652–653
 - modulus, 575
 - or, 575
 - plot units, 86
 - plotting, 650–652
 - range, 649
 - root(), 87, 653–654
 - toolbars, 642–643
 - units, 643
 - vectors, 655–656
- MATLAB, 659
 - abs(), 52
 - angle(), 53, 662
 - atan2(), 662
 - colon operator, 664
 - constants, 661
 - element-by-element operations, 69, 663
 - matrices, 662–663
 - max(), 457
 - operators, 661
 - plotting, 665–667
 - programming, 668–669
 - vector operations 522
 - vectors, 662
- Maxwell's equations, 172, 619
- microphone, 635–636
- MKS units, 670
- modulation index, 592
- MOSFET, 549, 558, 560, 566, 590

- natural gas, 5
- neodymium-iron-boron, 631–634
- nodal analysis, 71–72
- north pole, 622

- odd function, 562
- oersted (unit), 256
- Ohm's Law, 51, 65
- one-line diagram, 66–67
- open circuit voltage, 222, 226
- operation security, 370
- overcurrent, 44
- overvoltage, 38, 163, 406, 409–413

- parallel, definition of, 54
- passive sign convention, 50, 83, 92, 230, 275–276, 370–371
- peak power, 6, 8, 27, 31
- per unit system, 128–130
 - base values, 129, 132
- permanent magnets, 622, 630–633, 635–637, 641
- permeability, 253, 261–262, 283, 381, 619, 622
 - of free space, 173, 256, 674
 - relative, 256
- permittivity
 - of free space, 194, 674
- PEX, 168
- phase sequence, 98, 353, 425
- phase shift, 51, 62–65, 80
- phasor
 - conjugate, 61
 - definition of, 50–51
 - diagram, 105–106, 117
- pi (Π) circuit, 87, 218–219, 237, 409
- positive phase sequence, *see* phase sequence
- positive sequence capacitance, 215
- positive sequence inductance, 189
- potential coefficients, 203
- power, 50, 61
 - active, 61
 - apparent, 61
 - average, 61
 - complex, 61, 64, 81, 92, 120
 - instantaneous, 61, 63, 98
 - quadrature, 62
 - reactive, 62, 64, 80, 92, 261, 359–360
 - real, 61, 63
- power angle, 95, 230–231, 358–359, 362–363
- power factor, 62–63, 80, 92
 - angle, 62, 92
 - improvement, 90–91
- power plants, 5, 7
 - combined cycle, 20
 - fossil, 8
 - hydroelectric, 27–30
 - nuclear, 21–26
- power system, 2
- power triangle, 62
- pressurized water reactor 23, 25
- PSpice, 675
 - circuit editors, 675
 - examples, 145, 234, 405, 565, 597
 - libraries, 676
 - prefixes, 676
 - pulse source, 238, 410
 - VSIN, 235, 565
- pulse width modulation, 558, 566, 588, 590–592
- pumped storage, 30–32
- radio interference, 157, 198, 201
- reactance, 52–53
- rectifiers, 19, 351, 548, 559, *also see* inverters
 - bridge, 560–561, 567–568, 597–598
 - delay angle, 570, 574, 577–578, 582, 587, 606
 - diode, 542, 560–561
 - full-wave, 560–561
 - half-wave, 560–561, 563–566
 - line commutated, 566, 588
 - three-phase, 585
 - thyristor-controlled, 542, 553, 566–568, 585, 587, 598
- regenerative breaking, 545
- relay, 20, 36, 641
- reserve margin, 232
- residential electrical connection, 45
- reverse current breakdown, 549
- right hand rule, 171, 253, 273–274, 618
- ripple, 561
- root mean square, 2, 63
 - definition of, 51
 - Fourier series, 562
 - sinusoidal waveform, 51
- safety, 107, 160, 245, 300
- samarium cobalt, 631–634
- SCR, 549, 552–556, 560, 599
- scrubbers, 14
- service panel, 45–46
- SF₆, 34–36, 413
- shaded pole motor, 475, 477
- sheet steel, 247, 251–252, 261, 271
- shield conductors, 157–159, 164
- short circuit current, 84, 234
- shunt capacitor, 72

- SI units, 670–672
- smoothing capacitance, 597, 600–601
- smoothing inductance, 597, 600
- snubber circuit, 584–585, 587
- solenoid, 620, 627, 639
- south pole, 622
- space potential, 194
- split-phase motor, 475
- static stability, 360–361, 363–364, 393
- stator, 17–18, 30
- steady-state stability limit, 227
- step motor, 622
- substations, 1, 3, 33–34
- sub-transmission lines, 4, 156, 158, 165
- supply short circuit duty, 242
- supporting towers, 161, 165
- surge arrester, 19–20, 38–39, 44, 160
- susceptance, 292
- switchgear, 3, 161–162
- switching overvoltage, 413
- switching surge, 20, 38
- switchyard, 9, 26
- symbols, 673
- synchronization, 360
- synchronous condenser, 359
- synchronous generators, 17, 19
 - armature, *see stator*
 - armature flux, 355–356
 - armature inductance/reactance, 356
 - armature reaction, 356
 - brushless excitation, 19, 351–352
 - cooling, 18, 345–346
 - equivalent circuit, 357, 361, 374, 389
 - excitation, 19, 346, 351–352
 - hydro, 17, 27
 - induced voltage, 354, 356, 374, 380
 - neutral point, 101, 107, 111
 - operating concept, 352–357
 - rotor, 17–18, 344–348, 350
 - round rotor, 344–345
 - salient pole, 17, 19, 29–30, 344, 346, 349–352
 - short circuit, 405
 - slip rings, 350–351
 - stator, 344–347, 349–350
 - synchronous reactance, 357, 374, 380, 387–388, 406
 - synchronous speed, 353, 355
 - terminal voltage, 354, 356–357, 360
 - transient impedance, 406
 - voltage, 2, 245
- synchronous machines, 344, 359, *also see* synchronous generators
- system efficiency, 66
- system frequency, 1
- television interference, 157, 198, 201
- tension towers, 161, 165
- tesla (unit), 173, 672–673
- thermal efficiency, 5, 21
- thermal pollution, 11, 21
- Thévenin equivalent, 79–80
 - inverter, 595
 - network, 147, 222, 226, 229–230, 574
 - transformer, 276–277
- three-phase circuits
 - advantages, 97
 - balanced systems, 97–98
 - power measurement, 120–123, 320
- three-wire system, 106–107, 111
- thyristor, 549, 552–556, 560, 599
- torque, 433, 440, 473
 - starting, 441–442, 467, 474, 476, 493, 515
- total harmonic distortion, 574, 583
- transducers, 616, 630
- transformers, 4, 245
 - capacitance, 406
 - circuit parameters, 289, 293, 319
 - complex power, 275, 308
 - cooling, 249
 - core resistance, 291, 321, 323
 - core type, 273
 - current, 19–20, 36, 38
 - delta-delta connected, 309–310, 317–319
 - delta-wye connected, 308–310, 315–317, 331
 - distribution, 43
 - dry type, 249
 - equivalent circuit, 293
 - ground level, 44
 - grounding, 300, 566–567
 - ideal, 273–275
 - impedance transfer, 276–277, 284, 289
 - leakage reactance, 283–284, 323
 - oil cooled, 250–251

- transformers (*continued*)
 - open circuit test, 291–293, 319–321, 323, 328
 - parallel connection, 247, 294
 - phase shift, 306–307, 309–310, 315, 317
 - potential, 20, 36
 - power cube, 560
 - power plant, 19
 - rated current, 285, 299
 - rating, 299
 - real, 246, 283–284
 - shell type, 273
 - short circuit test, 289–291, 320, 322–323, 329
 - single-phase, 246, 273
 - single-phase equivalent, 303, 307, 319
 - step-down, 5, 44–45
 - three-phase, 249–251, 298–300
 - turns ratio 300–301, 305, 307, 309–310
 - voltage polarity, 247, 275
 - windings, 245–248, 273, 310
 - wye-delta connected, 305–308, 310, 313–315, 596
 - wye-wye connected, 300–305, 310–313, 325, 596
- transmission line parameters, 218
 - capacitance, 193, 217
 - inductance, 184, 192
 - resistance, 169–170
- transmission lines, 3–4, 155
 - conductors, 163–164
 - conductor arrangements, 179, 211, 220, 241–243
 - high voltage dc, 155–156, 596–597
 - line voltage, 2–4
 - models, 218–219
 - overhead, 4
 - right-of-way, 158
 - sag, 160–161
 - single-phase equivalent, 218, 221
 - siting, 157–158
 - span, 160–161
 - towers, 156–157, 163
- transmission system, 3–4
- transposition, 191–192, 217
- turbine
 - Francis, 31
 - hydraulic, 6, 27, 30
 - Kaplan, 29
 - steam, 15–16
- turbine-generator, 6
- turns ratio, 246, 274–275, 277

- underground cables, 4, 44, 161–163, 168–169
- unit conversions, 672
- unit dimensions, 671

- VAR, 62, 124
- voice coil, 635
- voltage
 - definition of, 49–50
 - extra-high, 2, 4, 156
 - induced, 258–259, 274
 - integrated from electric field, 194–195
 - line-to-ground, 194
 - line-to-line, 102–104, 120, 194
 - line-to-neutral, 102–104, 234
 - open circuit, 222, 226
 - polarity convention, 50, 64, 76
 - sinusoidal, 65
 - standards, 90, 277
 - ultra-high, 2, 4
- voltage division, 76–77
- voltage regulation, 67–68, 86, 278

- wattmeters, 120–121
- weather damage, 160
- weather shed, 165–167
- wye connection, 98–99
 - generators, 101–104
 - loads, 106–107, 109, 120