

Contents

Introduction		xiii
Chapter 1	Magnetism and Electricity	1
	Magnetic Poles	2
	Experiments with Magnets	3
	Formation of Permanent Magnets	7
	Aiding and Opposing Magnetic Fields	9
	Electromagnetism	11
	Volts, Amperes, and Ohms	17
	Electric and Magnetic Circuits	19
	Understanding Electric Circuits	25
	Kirchhoff's Voltage Law	30
	Electrical Power	30
	Quick-Check Instruments for Troubleshooting	32
	Summary	33
	Test Questions	34
Chapter 2	Conductors and Insulators	35
	Classes of Conductors	35
	Conducting Wire	36
	Circular Mil-Foot	37
	American Wire Gauge	39
	Stranded Wires	43
	Aluminum Wire	43
	Line Drop	44
	Temperature Coefficient of Resistance	44
	Earth (Ground) Conduction	45
	Conduction of Electricity by Air	45
	Conduction of Electricity by Liquids	50
	Insulators for Support of Wires	52
	Classes of Insulation	53
	Insulation Resistance	53
	Plastic-Insulated Sheathed Cables	55
	Summary	55
	Test Questions	56

vi Contents

Chapter 3	Electric Circuits	59
	Picture Diagrams and Schematic Diagrams	59
	Voltage Polarities in Series Circuits	60
	Voltage Measurements with Respect to Ground	62
	Resistance of a Battery	63
	Efficiency and Load Power	65
	Circuit Voltages in Opposition	66
	Principles of Parallel Circuits	69
	Shortcuts for Parallel Circuits	72
	Conductance Values	73
	Kirchhoff's Current Law for Parallel Circuits	78
	Practical Problems in Parallel Circuits	80
	Line Drop in Parallel Circuits	81
	Parallel Connection of Cells	84
	Summary	86
	Test Questions	87
Chapter 4	Series-Parallel Circuits	89
	Current Flow in a Series-Parallel Circuit	89
	Kirchhoff's Current Law	90
	Series-Parallel Connection of Cells	92
	Line Drop in Series-Parallel Circuits	93
	Use of a Wattmeter	94
	Circuit Reduction	94
	Power in a Series-Parallel Circuit	98
	Horsepower	99
	Three-Wire Distribution Circuit	100
	Summary	105
	Test Questions	106
Chapter 5	Electromagnetic Induction	107
	Principle of Electromagnetic Induction	107
	Laws of Electromagnetic Induction	109
	Self-Induction of a Coil	110
	Transformers	113

Contents vii

	Advantage of an Iron Core	119
	Choke Coils	119
	Reversal of Induced Secondary Voltage	122
	Switching Surges	122
	The Generator Principle	124
	Summary	126
	Test Questions	126
Chapter 6	Principles of Alternating Currents	129
	Frequency	129
	Instantaneous and Effective Voltages	129
	Ohm's Law in AC Circuits	133
	Power Laws in Resistive AC Circuits	136
	Combining AC Voltages	137
	Transformer Action in AC Circuits	142
	Core Loss and Core Lamination	148
	DC versus AC Resistance	150
	Summary	150
	Test Questions	151
Chapter 7	Inductive and Capacitive AC Circuits	153
	Inductive Circuit Action	153
	Power in an Inductive Circuit	157
	Resistance in an AC Circuit	159
	Impedance in AC Circuits	161
	Power in an Impedance	162
	Capacitive Reactance	163
	Capacitive Reactance and Resistance in Series	166
	Inductance, Capacitance, and Resistance in Series	172
	Inductance and Resistance in Parallel	175
	Capacitance and Resistance in Parallel	177
	Inductance, Capacitance, and Resistance in Parallel	179
	Summary	182
	Test Questions	183

viii Contents

Chapter 8	Electric Lighting	185
	Sources of Light	185
	Measurement of Amount of Illumination	186
	Tungsten Filaments	187
	Starting Surge of Current	188
	Aging Characteristics	190
	Lamp Bases and Bulbs	191
	Vapor-Discharge Lamps	194
	Metal Halide Lamps	201
	High-Pressure Sodium Lamps	202
	Low-Pressure Sodium Lamps	203
	Sun Lamps	204
	Ozone-Producing Lamps	205
	Flash Tubes	205
	Infrared Lamps	208
	Electroluminescent Panels	208
	Summary	209
	Test Questions	210
Chapter 9	Lighting Calculations	213
	Point-by-Point Method	213
	Lumen Method	217
	Lighting Equipment	224
	Level of Illumination	226
	Lamp Wattage	226
	Wire Capacity	227
	Load and Length of Run	229
	Panelboards	229
	Service and Feeders	229
	Watts per Square Foot	231
	Summary	232
	Test Questions	232
Chapter 10	Basic House Wiring	235
	Service Connections	236
	Residential Underground Service	240

Contents ix

Making Connections to the Entrance Panel	241
Circuitry	244
Individual Appliance Circuits	246
Regular Appliance Circuits	246
General-Purpose Circuits	246
New Work in Old Houses	250
Improving Circuits	251
Placing Outlets	251
Placing Switches	254
Roughing-In	254
Mounting Boxes	255
Old Work	256
Special Mounting Devices	258
Running Sheathed Cable	259
Metal Plates	261
Running Boards	261
Connecting Cable to Boxes	262
Fishing Cable in Old Work	263
Two-Person Technique	265
Bypassing One Floor of a Two-Story Home	266
Completing House Wiring: Splicing	268
Solderless Connectors	270
Installing Outlet Receptacles	271
Single-Pole Switches	273
Ceiling Box and Fixture Mounting	274
Summary	274
Test Questions	276
Chapter 11 Wiring with Armored Cable and Conduit	279
Cutting Armored Cable	279
Installing Armored Cable	280
Conduit Fittings	284
Wiring in Flexible Conduit	293

x Contents

	Connectors	296
	Summary	297
	Test Questions	299
Chapter 12	Home Circuiting, Multiple Switching, and Wiring Requirements	301
	Lamp Control from Electroliner Switch	303
	Control of Lamps from More Than One Location with Three-Way and Four-Way Switches	307
	Stairway Lamp Control Lighting	307
	Color-Coding of Switch Wiring	307
	Functional Planning	310
	Planning of Equipment	311
	Lighting the Halls	312
	Lighting the Living Room	314
	Lighting the Dining Room	316
	Lighting the Kitchen	318
	Lighting the Bedroom	320
	Lighting the Bathroom	323
	Lighting the Attic	324
	Lighting the Basement	324
	Lighting the Garage	326
	Fluorescent Lights	327
	Ground Circuit Fault Interrupters	330
	Arc-Fault Circuit Interrupters	331
	Summary	331
	Test Questions	334
Chapter 13	Electric Heating	337
	General Installation Considerations	337
	Circuiting	341
	AC-Operated Relays	344
	Hot-Water Electric Heat	346
	Radiant Heater	346
	Electric Water Heaters	347
	Ground Circuit	352

Contents xi

	Heating Cables	354
	Summary	356
	Test Questions	357
Chapter 14	Alarms and Intercoms	359
	Alarm Devices	359
	Intercoms	365
	System Planning	365
	Planning Details	370
	Wireless Intercom Systems	371
	Music Distribution Systems	374
	Industrial Installations	375
	School Installations	375
	Bells and Chimes	376
	Photoelectric Control of Bell Circuits	378
	Summary	378
	Test Questions	379
Chapter 15	Generating Stations and Substations	381
	Generating Stations	381
	Single-Bus System	385
	Circuit Breakers	385
	Instrument Transformers	386
	Double-Bus System	387
	Paralleling Generators	397
	Distribution	398
	Substations	404
	Automatic Substations	404
	Semiautomatic Substations	408
	Summary	412
	Test Questions	413
	Appendix	415
	Glossary	417
	Index	439

