

Index

- AC–DC system interaction 257
- AC versus DC 18
- Active filters 281
- Active power 2, 251, 301
- Average direct voltage 66, 247

- Back-to-back interconnections 240, 321
- Bipolar link 226, 237
- Break-even distance 14
- Bridge converter 58
- Bypassing of bridges 233

- Cables 236, 297
- Capacitor balancing 153, 159, 179, 199, 202, 299
- Capacitor clamping, *see* Multilevel conversion, flying capacitor
- Cascaded H-bridge 158, 165, 193, 339
- CCC (Capacitor commutated converter) 276, 284
- CEA control, *see* Constant extinction angle
- Clamp control 170
- Commutating voltage 62
- Commutation 62
 - see also* Overlap angle
- Commutation angle 62
- Commutation failure 232, 250
- Commutation reactance 62, 67, 247
- Complementary resonance 265
- Composite resonance 265
- Constant current control 247, 255
- Constant current transmission 242
- Constant extinction angle 245, 255
- Control
 - characteristics 245, 247, 250
 - constant current, *see* Constant current control
 - direct 299
 - equidistant firing 254
 - frequency 252, 300
 - power 251, 301
 - reactive power 301, 337, 352
 - tap changer, *see* On-load tap-changer
 - vector 299
 - voltage 301
 - VSC 299
- Converter
 - back to back 240, 277
 - disturbances 232
 - mercury valve 8
 - multi-pulse 74
 - six-pulse 57
 - twelve-pulse 75
- Cross-modulation 93, 262
- CSC (Current Source Conversion) 6, 12, 58, 97, 106, 114, 121, 124, 141, 221, 225, 327, 341
- Current margin 247
- Current setting 247

- DC capacitor 100, 102
- DC line fault 267
- DC link
 - bipolar 240
 - control 242, 303
 - monopolar, *see* Monopolar link
- DC reactor 231
- DC transmission advantages 9, 14
- Delay angle 58, 246
- Deregulation 16
- DFIG (Doubly fed induction generator) 12, 282

- Diode clamping 145, 149
 - see also* Multilevel conversion
- Diodes 51, 105, 106
- Direct voltage, *see* Average direct voltage
- Displacement factor 69
- Distributed generation (DG) 16
- Dynamic compensation 258

- Earth electrodes 238
- Earth return 239
- Electricity deregulation 16
- Electrode, earth 238
- Electromagnetic interference (EMI) 113
- EMTDC 187, 216, 279, 284, 317, 332, 341, 345
- Environmental influence 5, 306
- Equivalent disturbing current 92
- ETO (Emitter turn-off thyristor) 45, 53
- Extinction angle 67, 245, 249, 277

- FACTS 13, 18, 21
- Fibre optics 245
- Filters
 - AC side 90, 231, 257, 286, 297
 - active 281
 - continuously tuned 280
 - damped 287
 - DC side 92, 231, 297
 - effect of network impedance 91
 - high-pass, *see* Filters, damped
 - quality of 91, 231
 - radio frequency interference (RFI) 2
 - reactive power of 90
 - sharpness of tuning 91
 - tuned 91, 280
- Firethrough 232
- Firing angle, *see* Delay angle
- Firing-shift control 352
- Flexible power 5, 13
- Forced commutation, *see* Self-commutation
- Frequency control 252, 300
- Frequency interactions 262

- Gate turn-off, *see* GTO
- GCT, *see* IGCT
- GTO 36, 53, 210

- H-Bridge, *see* Cascaded H-bridge
- Harmonic cross-modulation 262
- Harmonic distortion 84, 152
- Harmonic filters 90
 - see also* Filters
- Harmonic impedance 91
- Harmonic instability 94, 257

- Harmonic penetration 111
- Harmonics 71, 75, 109, 128, 144, 162
 - AC side 73, 303
 - characteristic 71
 - at no overlap 73, 75
 - at overlap 72, 75
 - DC side 72
 - even 84, 93, 128
 - magnification of 89
 - resonance 265
 - sequence components 84, 94
 - tripen 84, 93
 - uncharacteristic 81, 89
- HVDC Light 304, 306
 - three level 312
 - two level 308

- IEGT (Injection enhanced transistor) 53
- IGBT 11, 47, 49, 53, 98, 103, 121, 306
 - converter 306, 312
 - station layout 296
 - valve 306
- IGCT 41, 53, 98, 121, 210
- Instability, *see* Harmonic instability; Power instability
- Insulated gate bipolar transistor, *see* IGBT
- Interaction, *see* AC–DC system interaction
- Interharmonics 81
- Inversion 67

- LCC (Line Commutated Conversion) 6, 57, 114, 224, 225, 275
- Level number 142
- Light triggered thyristor 32
- Lightning surges 232
- Low voltage current limit (LVCL) 251

- Margin angle, *see* Extinction angle
- MCT (MOS controlled thyristor) 44, 53
- Mercury-arc valve 8
- Misfire 232
- MLCR, *see* Multilevel reinjection
- MLVR, *see* Multilevel reinjection
- Monopolar link 241
- MOSFET 25, 43, 44, 47
- MTO (MOS turn-off thyristor) 42, 53
- Multibrige conversion 74, 111, 137
- Multigroup converters 233
- Multilevel conversion 141, 161
 - cascaded H-bridge 142, 158
 - diode clamping 142, 164, 327
 - flying capacitor 142, 155, 164, 327
 - neutral point clamping 142

- Multilevel CSC 142, 341
- Multilevel reinjection 170
 - MLCR 210, 221, 327
 - MLVR 170, 187, 193, 221, 327
- Multilevel VSC 142, 327
- Multiterminal DC 12, 240
 - series connection 227
 - subtransmission 323

- Off-shore conversion 283
- OLTC, *see* On-load tap-changer
- On-load tap-changer 101, 242, 247, 249, 297, 301
- Overhead lines 235
- Overlap angle, *see* Commutation angle
- Overvoltages 258

- Phase-locked oscillator 253
- PLL (Phase locked loop) 300, 302, 308
- Pn rectifier 22
- Power control 251
- Power diode 24, 51
- Power electronics control 5
- Power factor 2, 69, 334, 337
 - see also* Displacement factor
- Power/frequency control 252
- Power instability 129, 257
- Power losses 112, 125
- Power modulation 249, 252, 261, 305
- Power reversal 249
- Power transfer 1, 3, 292
- PSCAD, *see* EMTDC
- Pulse number 71
- Pulse width modulation 29, 53, 127, 141, 161, 293, 299, 307
- PWM, *see* Pulse width modulation

- Q, *see* Filters, quality of

- Radio interference 226, 236, 297
- Reactive power 2, 69, 301, 337
- Reactive power compensators 259
- Real power, *see* Active power
- Rectifier 64
 - see also* Converter
- Reinjection 77, 116, 121
- Reliability 267
- Resonance
 - complementary 265
 - composite 265
- Reversal of power, *see* Power reversal

- SCR, *see* Silicon Controlled Rectifier; Short circuit ratio
- Sea return, *see* Earth return
- Self-commutating thyristor conversion 213
- Self-commutation 36, 97, 141, 170, 213
- Short circuit ratio 11, 257
- SiC (Silicon carbide) 55
- Silicon controlled rectifier 10, 21, 53
 - see also* Thyristor
- Smoothing reactor, *see* DC reactor
- Snubbers 30, 39, 113, 148
- Soft switching 29, 170
- Stability, of AC transmission 259
- STATCOM 100, 150, 204, 259, 282, 328, 337
- Static power conversion 6
- Sub-synchronous resonance 260
- Surge arrester 235
- Switching losses 29
- Synchronous compensator 257–8

- Tap changer control 248
- Telecommunications 244
- Telephone influence factor 90
- Telephone interference 92
- Thyristor 31
 - electrically triggered 32
 - light triggered 32
 - module (or level) 228
 - station layout 227
 - valve 227
- Transformer 230, 297
 - leakage 231
 - phase-shift 74
 - saturation effects 94, 256
- Transformer connections for increased pulse number 74
- Transient stability 261
- Transistor 25, 47, 53
- Triple harmonics 84, 93
- Tripole DC transmission 287

- Unbalanced AC voltage 84
- Uncharacteristic harmonics 81
- Unit connection 311

- Valve, *see* Thyristor
- Voltage controlled oscillator, *see* Phase-locked oscillator
- Voltage dependent current order limit (VDCOL) 251
- Voltage interaction 257

- Voltage regulation 258
- VSC (Voltage source conversion) 6, 11, 56, 98,
106, 114, 116, 127, 138, 142, 170, 291, 328
- VSC control 304
- Weak AC systems 295, 312
- Wind power 282
farms 310, 322
- ZCS (Zero current switching) 29, 170, 328
- ZVS (Zero voltage switching) 29, 170, 328