

Contents

Foreword	xi
Preface	xiii
Acknowledgements	xv
1 Energy and Electricity	1
1.1 The World Energy Scene	1
1.1.1 History	1
1.1.2 World energy consumption	1
1.1.3 Finite resources	2
1.1.4 Energy security and disparity of use	3
1.2 The Environmental Impact of Energy Use	3
1.2.1 The problem	3
1.2.2 The science	5
1.2.3 The Kyoto protocol	6
1.2.4 The Stern Report	7
1.2.5 Efficient energy use	8
1.2.6 The electricity sector	10
1.2.7 Possible solutions and sustainability	11
1.3 Generating Electricity	11
1.3.1 Conversion from other energy forms – the importance of efficiency	11
1.3.2 The nuclear path	12
1.3.3 Carbon capture and storage	13
1.3.4 Renewables	13
1.4 The Electrical Power System	16
1.4.1 Structure of the electrical power system	16
1.4.2 Integrating renewables into power systems	18
1.4.3 Distributed generation	19
1.4.4 RE penetration	19
References	20
2 Features of Conventional and Renewable Generation	21
2.1 Introduction	21
2.2 Conventional Sources: Coal, Gas and Nuclear	22
2.3 Hydroelectric Power	23
2.3.1 Large hydro	24
2.3.2 Small hydro	25

2.4	Wind Power	27
	2.4.1 <i>The resource</i>	27
	2.4.2 <i>Wind variability</i>	28
	2.4.3 <i>Wind turbines</i>	30
	2.4.4 <i>Power variability</i>	33
2.5	PV and Solar Thermal Electricity	36
	2.5.1 <i>The resource</i>	36
	2.5.2 <i>The technology</i>	37
	2.5.3 <i>Photovoltaic systems</i>	38
	2.5.4 <i>Solar thermal electric systems</i>	40
2.6	Tidal Power	42
	2.6.1 <i>The resource</i>	42
	2.6.2 <i>Tidal enhancement</i>	43
	2.6.3 <i>Tidal barrages</i>	43
	2.6.4 <i>Operational strategies</i>	44
	2.6.5 <i>Tidal current schemes</i>	45
2.7	Wave Power	47
	2.7.1 <i>The resource</i>	47
	2.7.2 <i>The technology</i>	48
	2.7.3 <i>Variability</i>	49
2.8	Biomass	50
	2.8.1 <i>The resource</i>	50
	2.8.2 <i>Resource sustainability</i>	51
2.9	Summary of Power Generation Characteristics	52
2.10	Combining Sources	53
	References	53
3	Power Balance/ Frequency Control	55
3.1	Introduction	55
	3.1.1 <i>The power balance issue</i>	55
3.2	Electricity Demand	56
	3.2.1 <i>Demand curves</i>	56
	3.2.2 <i>Aggregation</i>	57
	3.2.3 <i>Demand-side management – deferrable loads</i>	58
3.3	Power Governing	59
	3.3.1 <i>Power conversion chain</i>	59
	3.3.2 <i>The governor</i>	60
	3.3.3 <i>Parallel operation of two generators</i>	61
	3.3.4 <i>Multigenerator system</i>	62
	3.3.5 <i>The steady state power–frequency relationship</i>	63
3.4	Dynamic Frequency Control of Large Systems	64
	3.4.1 <i>Demand matching</i>	64
	3.4.2 <i>Demand forecasting</i>	65
	3.4.3 <i>Frequency limits</i>	67
	3.4.4 <i>Generation scheduling and reserve</i>	68
	3.4.5 <i>Frequency control at different timescales</i>	68
	3.4.6 <i>Meeting demand and ensuring reliability</i>	70
	3.4.7 <i>Capacity factor and capacity credit</i>	71
3.5	Impact of Renewable Generation on Frequency Control and Reliability	72
	3.5.1 <i>Introduction</i>	72
	3.5.2 <i>Aggregation of sources</i>	73

3.5.3	<i>Value of energy from the wind</i>	76
3.5.4	<i>Impact on balancing</i>	76
3.5.5	<i>Impact on reliability</i>	79
3.5.6	<i>Discarded/curtailed energy</i>	79
3.5.7	<i>Overall penalties due to increasing penetration</i>	80
3.5.8	<i>Combining different renewable sources</i>	81
3.5.9	<i>Differences between electricity systems</i>	81
3.5.10	<i>Limits of penetration from nondispatchable sources</i>	81
3.6	Frequency Response Services from Renewables	84
3.6.1	<i>Wind power</i>	84
3.6.2	<i>Biofuels</i>	85
3.6.3	<i>Water power</i>	86
3.6.4	<i>Photovoltaics</i>	86
3.7	Frequency Control Modelling	86
3.7.1	<i>Background</i>	86
3.7.2	<i>A modelling example</i>	89
3.8	Energy Storage	91
3.8.1	<i>Introduction</i>	91
3.8.2	<i>Storage devices</i>	91
3.8.3	<i>Dynamic demand control</i>	93
	References	94
	Other Useful Reading	95
4	Electrical Power Generation and Conditioning	97
4.1	The Conversion of Renewable Energy into Electrical Form	97
4.2	The Synchronous Generator	98
4.2.1	<i>Construction and mode of operation</i>	98
4.2.2	<i>The rotating magnetic field</i>	101
4.2.3	<i>Synchronous generator operation when grid-connected</i>	103
4.2.4	<i>The synchronous generator equivalent circuit</i>	104
4.2.5	<i>Power transfer equations</i>	105
4.2.6	<i>Three-phase equations</i>	106
4.2.7	<i>Four-quadrant operation</i>	107
4.2.8	<i>Power-load angle characteristic: stability</i>	108
4.3	The Transformer	108
4.3.1	<i>Transformer basics</i>	108
4.3.2	<i>The transformer equivalent circuit</i>	110
4.3.3	<i>Further details on transformers</i>	112
4.4	The Asynchronous Generator	112
4.4.1	<i>Construction and properties</i>	112
4.4.2	<i>The induction machine equivalent circuit</i>	114
4.4.3	<i>The induction machine efficiency</i>	116
4.4.4	<i>The induction machine speed-torque characteristic</i>	117
4.4.5	<i>Induction generator reactive power</i>	120
4.4.6	<i>Comparison between synchronous and asynchronous generators</i>	121
4.5	Power Electronics	121
4.5.1	<i>Introduction</i>	121
4.5.2	<i>Power semiconductor devices</i>	122
4.5.3	<i>Diode bridge rectifier</i>	124
4.5.4	<i>Harmonics</i>	126
4.5.5	<i>The thyristor bridge converter</i>	126

4.5.6	<i>The transistor bridge</i>	128
4.5.7	<i>Converter internal control systems</i>	133
4.5.8	<i>DC–DC converters</i>	133
4.6	Applications to Renewable Energy Generators	134
4.6.1	<i>Applications to PV systems</i>	134
4.6.2	<i>Applications to wind power</i>	137
	References	147
5	Power System Analysis	149
5.1	Introduction	149
5.2	The Transmission System	149
5.2.1	<i>Single-phase representation</i>	151
5.2.2	<i>Transmission and distribution systems</i>	152
5.2.3	<i>Example networks</i>	153
5.3	Voltage Control	153
5.4	Power Flow in an Individual Section of Line	156
5.4.1	<i>Electrical characteristics of lines and cables</i>	156
5.4.2	<i>Single-phase equivalent circuit</i>	156
5.4.3	<i>Voltage drop calculation</i>	157
5.4.4	<i>Simplifications and conclusions</i>	158
5.5	Reactive Power Management	160
5.5.1	<i>Reactive power compensation equipment</i>	160
5.6	Load Flow and Power System Simulation	163
5.6.1	<i>Uses of load flow</i>	163
5.6.2	<i>A particular case</i>	164
5.6.3	<i>Network data</i>	165
5.6.4	<i>Load/generation data</i>	165
5.6.5	<i>The load flow calculations</i>	167
5.6.6	<i>Results</i>	168
5.6.7	<i>Unbalanced load flow</i>	168
5.7	Faults and Protection	169
5.7.1	<i>Short-circuit fault currents</i>	169
5.7.2	<i>Symmetrical three-phase fault current</i>	170
5.7.3	<i>Fault currents in general</i>	170
5.7.4	<i>Fault level (short-circuit level) – weak grids</i>	171
5.7.5	<i>Thévenin equivalent circuit</i>	171
5.8	Time Varying and Dynamic Simulations	172
5.9	Reliability Analysis	173
	References	173
6	Renewable Energy Generation in Power Systems	175
6.1	Distributed Generation	175
6.1.1	<i>Introduction</i>	175
6.1.2	<i>Point of common coupling (PCC)</i>	176
6.1.3	<i>Connection voltage</i>	176
6.2	Voltage Effects	177
6.2.1	<i>Steady state voltage rise</i>	177
6.2.2	<i>Automatic voltage control – tap changers</i>	178
6.2.3	<i>Active and reactive power from renewable energy generators</i>	179
6.2.4	<i>Example load flow</i>	180

6.3	Thermal Limits	183
6.3.1	<i>Overhead lines and cables</i>	183
6.3.2	<i>Transformers</i>	184
6.4	Other Embedded Generation Issues	184
6.4.1	<i>Flicker, voltage steps and dips</i>	184
6.4.2	<i>Harmonics/distortion</i>	185
6.4.3	<i>Phase voltage imbalance</i>	186
6.4.4	<i>Power quality</i>	186
6.4.5	<i>Network reinforcement</i>	187
6.4.6	<i>Network losses</i>	187
6.4.7	<i>Fault level increase</i>	187
6.5	Islanding	188
6.5.1	<i>Introduction</i>	188
6.5.2	<i>Loss-of-mains protection for rotating machines</i>	189
6.5.3	<i>Loss-of-mains protection for inverters</i>	190
6.6	Fault Ride-through	190
6.7	Generator and Converter Characteristics	192
	References	193
7	Power System Economics and the Electricity Market	195
7.1	Introduction	195
7.2	The Costs of Electricity Generation	195
7.2.1	<i>Capital and running costs of renewable and conventional generation plant</i>	195
7.2.2	<i>Total generation costs</i>	197
7.3	Economic Optimization in Power Systems	198
7.3.1	<i>Variety of generators in a power system</i>	198
7.3.2	<i>Optimum economic dispatch</i>	200
7.3.3	<i>Equal incremental cost dispatch</i>	201
7.3.4	<i>OED with several units and generation limits</i>	203
7.3.5	<i>Costs on a level playing field</i>	204
7.4	External Costs	205
7.4.1	<i>Introduction</i>	205
7.4.2	<i>Types of external cost</i>	205
7.4.3	<i>The Kyoto Agreements</i>	206
7.4.4	<i>Costing pollution</i>	207
7.4.5	<i>Pricing pollution</i>	208
7.5	Effects of Embedded Generation	209
7.5.1	<i>Value of energy at various points of the network</i>	209
7.5.2	<i>A cash-flow analysis</i>	210
7.5.3	<i>Value of embedded generation – regional and local issues</i>	212
7.5.4	<i>Capacity credit</i>	213
7.5.5	<i>Summary</i>	215
7.6	Support Mechanisms for Renewable Energy	215
7.6.1	<i>Introduction</i>	215
7.6.2	<i>Feed-in law</i>	216
7.6.3	<i>Quota system</i>	217
7.6.4	<i>Carbon tax</i>	217
7.7	Electricity Trading	218
7.7.1	<i>Introduction</i>	218
7.7.2	<i>The UK electricity supply industry (ESI)</i>	218

7.7.3	<i>Competitive wholesale markets in other countries</i>	223
7.7.4	<i>The value of renewable energy in a competitive wholesale market</i>	226
	References	229
8	The Future – Towards a Sustainable Electricity Supply System	231
8.1	Introduction	231
8.2	The Future of Wind Power	232
	8.2.1 <i>Large wind turbines</i>	232
	8.2.2 <i>Offshore wind farm development</i>	233
	8.2.3 <i>Building integrated wind turbines</i>	238
8.3	The Future of Solar Power	240
	8.3.1 <i>PV technology development</i>	240
	8.3.2 <i>Solar thermal electric systems</i>	241
8.4	The Future of Biofuels	242
8.5	The Future of Hydro and Marine Power	243
8.6	Distributed Generation and the Shape of Future Networks	244
	8.6.1 <i>Distribution network evolution</i>	244
	8.6.2 <i>Active networks</i>	245
	8.6.3 <i>Problems associated with distributed generation</i>	246
	8.6.4 <i>Options to resolve technical difficulties</i>	246
8.7	Conclusions	249
	References	250
	Appendix: Basic Electric Power Engineering Concepts	253
A.1	Introduction	253
A.2	Generators and Consumers of Energy	253
A.3	Why AC?	255
A.4	AC Waveforms	255
A.5	Response of Circuit Components to AC	256
	A.5.1 <i>Resistance</i>	257
	A.5.2 <i>Inductance</i>	258
	A.5.3 <i>Capacitance</i>	259
A.6	Phasors	260
A.7	Phasor Addition	261
A.8	Rectangular Notation	263
A.9	Reactance and Impedance	265
	A.9.1 <i>Resistance</i>	265
	A.9.2 <i>Inductance</i>	265
	A.9.3 <i>Capacitance</i>	266
	A.9.4 <i>Impedance</i>	266
A.10	Power in AC Circuits	267
A.11	Reactive Power	269
A.12	Complex Power	269
A.13	Conservation of Active and Reactive Power	271
A.14	Effects of Reactive Power Flow – Power Factor Correction	272
A.15	Three-phase AC	273
A.16	The Thévenin Equivalent Circuit	275
	Reference	276
	Index	277